

5 19 24 28 34 40 45
50 59 64 68

ELEKTOR ELECTRONICS

28 DAC VOLTAGE CONTROL
40 IC ADDRESS

THE INTERNATIONAL ELECTRONICS MAGAZINE
JUNE 1993
£2.25

DIGITAL READ-OUT FOR VHF/UHF RECEIVER

Real-time Clock for 80C32 Computer


GAL Programmer Upgrade

Inexpensive Phase Meter

Spectrum VU Meter

Electricity from
the Wind

A CW Compatible
T/R Switch

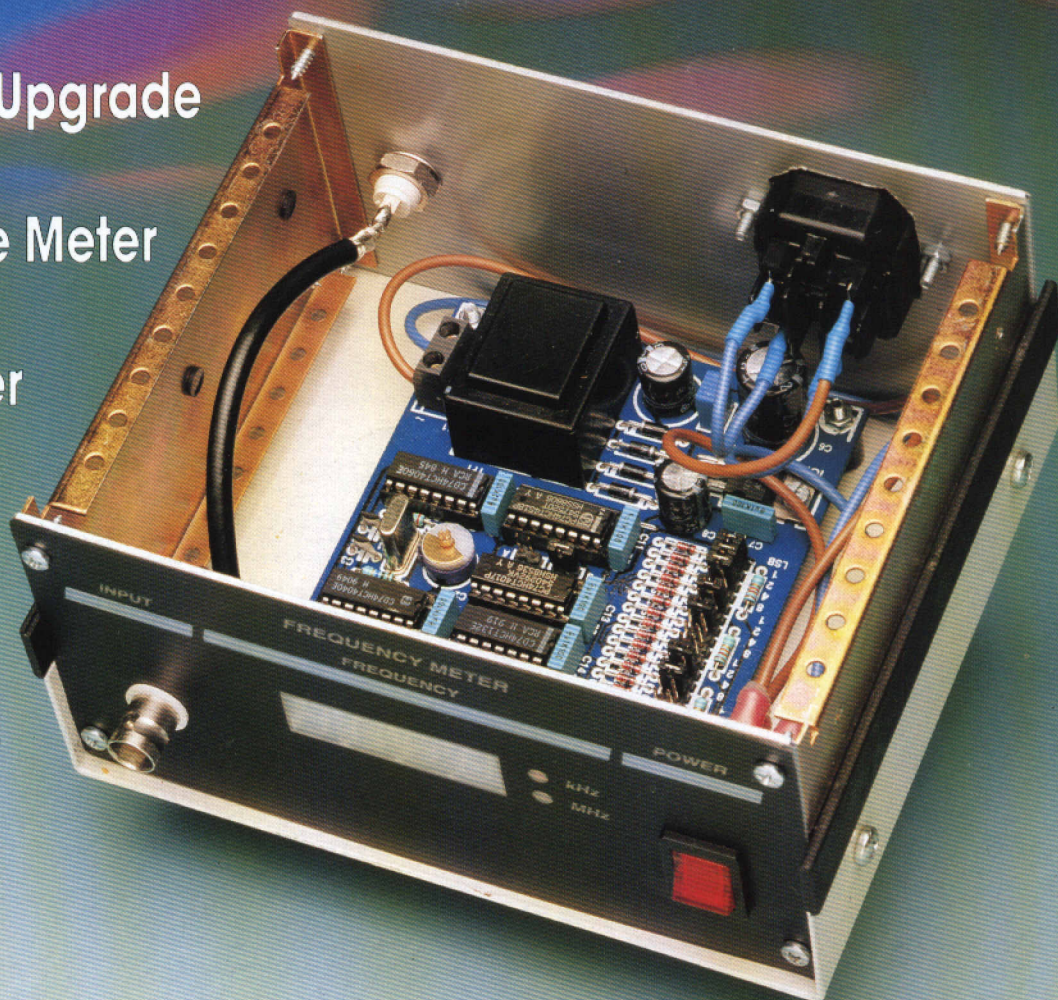

In next month's issue

- **More than 50 small construction projects** plus
- The analogue sub-system
- Active 3-way loudspeaker
- Maxi micro clock
- Four-fold DAC
- VHF-low convertor
- Camcorder audio mixer
- SFH505A: IR receiver and demodulator in one
- SMD soldering station
- EMC testing of PMR equipment
- Active probe
- Matrix keypad encoder

Front cover

The wideband VHF/UHF receiver in last month's issue is not complete without a dial to tell you the transmit frequency of the station you are listening to. Such a tuning dial is described on page 34. It takes the form of a sensitive 4-digit frequency meter with a preset option and a maximum input frequency of well over 30 MHz. It is also suitable for general use in your workshop.

Copyright © 1993 Elektor

ABC

CONSUMER PRESS

AUDIO & HI-FI

- 8 PROJECT:** Spectrum VU meter
Design by T. Giesberts

COMPONENTS

- 28 PROJECT:** GAL programmer upgrade
Design by M. Nossowitz
- 31** GAL programmer software for Amiga

COMPUTERS & MICROPROCESSORS

- 45 PROJECT:** Real-time clock for 80C32 computer
Design by W. Hackländer
- 64** 80C32 Application Notes (3)
Design by Z. Stojasavljevic

GENERAL INTEREST

- 50** Electromagnetic compatibility - Part 2
By J. Ruiters
- 40** Making sense of measurements - Part 2
By Joseph J. Carr
- 24 COURSE:** Figuring it out - Part 6: Frequencies and filters
By Owen Bishop

RADIO, TELEVISION & COMMUNICATIONS

- 34 PROJECT:** Digital read-out for VHF/UHF receiver
Design by L. Pijpers
- 56 PROJECT:** A CW compatible T/R switch
Design by Pedro Wyny, ON4AWQ
- 62** DX Television
By Keith Hamer and Garry Smith

SCIENCE & TECHNOLOGY


- 14** Electricity from the wind
By Dr K.A. Nigim

TEST & MEASUREMENT


- 19 PROJECT:** Inexpensive phase meter
Design by F. Hueber

MISCELLANEOUS INFORMATION

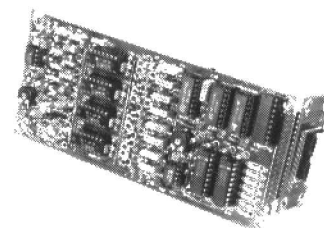
Electronics scene **5**; New books **49**; Readers' letters **58**;
Events **58**; Switchboard **59**; Product overview **68**;
Readers' services **70**; Terms of Business **72**;
Buyers' guide **74**; Index of advertisers **74**




Spectrum VU meter - p. 8

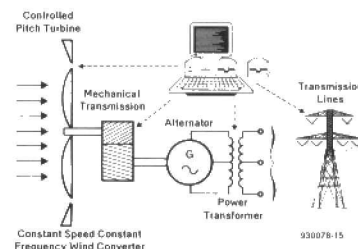

Electricity from the wind - p. 14

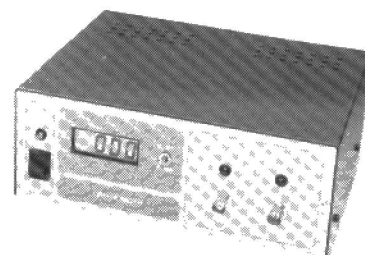

Inexpensive phase meter - p. 19

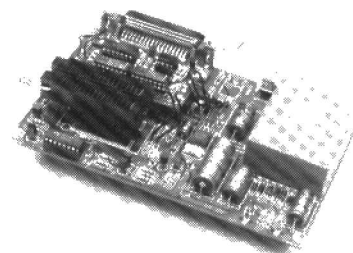

GAL programmer upgrade - p. 28

Elektor Electronics is published monthly, except in August, by Elektor Electronics (Publishing), P.O. Box 1414, Dorchester, Dorset DT2 8YH, England. The magazine is available from newsagents, bookshops, and electronics retail outlets, or on subscription at an annual (1993) post paid price of £25.00 in the United Kingdom; air speeded: £32.00 in Europe; £41.00 in Africa, the Middle East and South America; £43.00 in Australia, New Zealand and the Far East; and \$56.00 in the USA and Canada. Application to mail at Second Class Postage Rate to the USA is pending at Rahway N.J. Postmaster: Please send address corrections to Elektor Electronics, c/o Mercury Airfreight International Ltd Inc., 2323 Randolph Avenue, Avenel, New Jersey, N.J. 07001.

ELECTRONICS SCENE

COUNTDOWN TO PHONEDAY HAS STARTED

On Easter Sunday, 16 April, 1995, there will be major changes to national and international dialling codes. The changes follow extensive and lengthy consultation by the Office of Telecommunications (OfTel) with representatives of telephone users, operators and equipment manufacturers. They will create the additional codes and numbers that are needed to cater for the rapid growth of telecommunications services well into the next century, and provide capacity for new operators entering the market.

Although the changes are almost two years away, many people will already have to take them into account. For example, communications managers will have to start planning the reprogramming of telecommunications and computer equipment which store numbers in memories or bar calls to certain destinations. Then there are operators and users of security and care alarms that report to distant monitoring centres. Many alarms will need to be reprogrammed to dial the correct new code.

The changes taking place are:


- Area dialling codes will have a '1' inserted after the initial '0'. For example, Cardiff's 0222 becomes 01222 and Central London changes from 071 to 0171.
- The international dialling code changes from 010 to 00. This is a European Community requirement and internationally there are moves to make 00 the standard international dialling code.
- Five cities will be given a completely new code and their existing six-digit local number will be increased to seven digits.

Anyone wanting any information about Phoneday can phone BT's free helpline on 0800 010101.

A NEW WAY OF LOOKING AT THE WEATHER

Most high-quality weather stations are bulky, difficult to operate and, above all, expensive. Not so the Davis Instruments from ICS Electronics. With advanced microprocessors, thoughtfully designed keyboards, displays and sophisticated add-on accessories, the two Davis weather stations meet the needs of everyone.

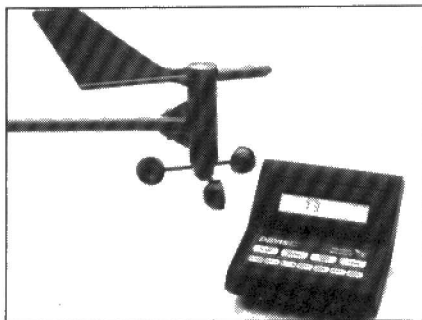The Weather Wizard II includes all the most requested features: inside and outside temperature, wind direction, wind speed and wind chill. The top-of-the-line Weather Monitor II includes all of these features plus barometric pressure and inside humidity. Both units record highs and lows and tell you the time



and date they occurred.

A rain collector can be added to both the Weather Wizard II and the Weather Monitor II, allowing you to measure daily and accumulated rainfall. An external temperature/humidity sensor can be added to the Weather Monitor II to track outside humidity and dew point.

A series of programmable alarms can be set to let you know when conditions rise above, or fall below, certain points. To protect valuable plants and crops, a gardener or farmer can set an alarm to go off when the temperature approaches freezing. A sailor, private pilot or ski lift operator can set an alarm to go off when wind speed approaches dangerous levels.

With the Weather Monitor II, a greenhouse operator or museum curator can set an alarm to go off when humidity rises or falls below optimum levels.

Information is shown on a large, well-designed LCD, which reads in either American or metric units or a combination of the two.

For those with an interest in tracking and comparing historical data, either unit can be connected to the Weatherlink data storage module. This will store data until it is transferred to an IBM (compatible) PC, where Weatherlink software will allow data to be put into graphical form, summarized and analysed.

The units are available in the UK and Europe from **ICS Electronics Ltd, Unit V, Rudford Industrial Estate, Ford, Arundel, West Sussex BN18 0BD, England. Telephone (0903) 731101; Fax (0903) 731105**, and in the USA and Canada from **Davis Instruments, 3465 Diablo Ave, Hayward, CA 94545, USA. Telephone (510) 732 7814; Fax (510) 670 0589**.

THE SETMAKERS

A new documentary titled *The Long Summer* uses photographs and information from the British Radio & Electronics Equipment Manufacturers Association's book *The Setmakers* (reviewed in the May 1991 issue of *Elektor Electronics*), which is a history of the Radio and Television industry.

The programme is on Channel 4, start-

ing on Sunday 16 May at 20.00h. The first part known as *Gathering Speed* is about the technologies in the inter-war years and features the products that define our modern age: the wireless, the internal combustion engine and the aeroplane. It is narrated by Alan Bennett and promises to be a most interesting programme for anyone who has been involved in our industry. Uncompromisingly serious but never po-faced, witty but never facile.

Copies of *The Setmakers* are available from **John O'Neill, 13 Green Curve, Banstead, Surrey SM7 1NS, England. Telephone (0737) 373545; Fax (0737) 357587**.

PATS SOFTWARE UPGRADED

Seaward Electronic Ltd has introduced a new version of its Portable Appliance Testing (PATs) software. This incorporates a number of new facilities. It is now capable of creating a database that identifies different products labelled by their serial number. This information can then be downloaded into the tester and allows an operator to visit a site and by simply entering the serial number, the instrument will then identify the product to establish which tests are appropriate and automatically conduct the testing without further user interaction.




Seaward Electronic Ltd, Bracken Hill, South West Industrial Estate, Peterlee, Co. Durham SR8 2JJ. Telephone (091) 586 3511.

SUPER POWERFLOW CONTROL OPERATING IN THE USA

The world's first electrical transmission system that controls direct and verniers powerflow has started commercial operation at the Western Area Power Administration's (WAPA) network at Kayenta Substation in Arizona. Siemens' power transmission and distribution group installed the system, which is a combination of a conventional fixed-series compensator and a controlled reactor.

This directly controlled series com-

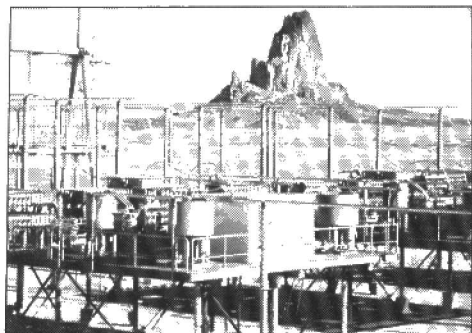

pensation scheme – called Advanced Series Compensation (ACS) – has the ability to control the compensation degree of the transmission line continuously and to achieve direct control of the transmission line's impedance. Unlike conventional series compensators, this technique provides flexible and direct control of the powerflow in transmission systems. The WAPA system operates in a 230 kV, 200-mile long transmission line close to Monument Valley.

Siemens AG, Power Transmission and Distribution Group, P.O. Box 3220, D-8520 Erlangen, Germany.

IPRE RADIO AND AUDIO PRIZE WINNER

Chuhar Singh, from Birmingham, is the first winner of a new annual award: the Incorporated Practitioners in Radio and Electronics (IPRE) Radio and Audio Prize. The award has been created by the IPRE to recognize the candidate achieving the best results in the City and Guilds of London Institute (CGLI) Electronics Servicing Course 224 – Practical Tests Radio and Audio option, administered by the Electronics Examination Board.

The IPRE – a specialist division of the Institution of Electronics and Electrical

Incorporated Engineers (IEEIE) – caters for the professional interests of those engaged in the field of electronics servicing. IPRE members, who work mainly in manufacturing, retailing, rental and servicing organizations, are offered recognition of their qualifications and experience and the use of appropriate designatory letters.

Married, with two children, Chuhar, who lives in Edgbaston, Birmingham, is employed by the West Midlands Fire Service. He was born in India, but received no formal education until the age of 13 when he moved to the UK.



IEEIE, Savoy Hill House, Savoy Hill, London WC2R 0BS. Telephone 071 836 3357; Fax 071 497 9006.

FAST GANG PROGRAMMER

Ice Technology's Speedmaster 8000 takes under five seconds to download, program and verify eight 64Kx8 EPROMs using fast programming algorithms. Larger devices are programmed in proportionate times, for example, eight 2MEPROMs take only 36 seconds.

The Micromaster 1000 is a universal programmer that can program memory devices and programmable logic as well as microcontrollers. It is designed to fill

a gap in the market for a low-cost professional solution to chip programming, particularly for microcontrollers which often require separate adapters.

For address and telephone number of Ice Technology see inside back cover.

NEW ALARM CONTROL UNITS

Autona's microprocessor-based panels in the 2000 Series provide all the necessary functions required for controlling security systems from the most basic to the advanced multi-sensor installations found in commercial applications.

The two new models differ only in the method of switching: keyswitch or keypad operation. The keypad version permits the use of pass codes with 2–12 digits to be set by the user.

The units are free of 'gimmicky' facilities (as sometimes found in today's consumer electronic equipment) so that they can be operated by all members of the family without the need for extensive familiarization.

Autona Ltd, 51 Poppy Road, Princes Risborough HP27 9DB, England. Telephone (08444) 5740; Fax (08444) 7102.

CHOOSING SOFTWARE WITH CONFIDENCE

ERA Technology has introduced a new service designed to help organizations of all types with the development or procurement of software.

Launched under the banner 'Software with Confidence', the service aims to provide assistance at any point in the development, procurement or implementation phases. This can include full-scale crisis management support, where the rapid analysis of problems and their

Produced and published by **ELEKTOR ELECTRONICS (Publishing)**

Editor/publisher: Len Seymour
Technical Editor: J. Buiting

Editorial & Administrative Offices:
P.O. Box 1414
DORCHESTER DT2 8YH
England

Telephone: (0305) 250 995 (National)
or +44 305 250 995 (International)
Fax: (0305) 250 996 (National)
or +44 305 250 996 (International)

U.K. Advertising Office:
3 Crescent Terrace
CHELTENHAM GL50 3PE
Telephone: (0242) 510 760
Fax: (0242) 226 626

International Advertising Office:
Elektuur BV
P.O. Box 75
6190 AB BEEK
The Netherlands
Telephone: +31 46 38 94 44
Fax: +31 46 37 01 61

Subscriptions:

World Wide Subscription Service Ltd.
Unit 4, Gibbs Reed Farm
Pashley Road
TICEHURST TN5 7HE
Telephone: (0580) 200 657 (National)
or +44 580 200 657 (International)
Fax: (0580) 200 616 (National)
or +44 580 200 616 (International)

Head Office:

P.O. Box 75
6190 AB BEEK
The Netherlands
Telephone: +31 46 38 94 44
Telex: 56617 (elekt nl)
Fax: +31 46 37 01 61
Managing Director: M.M.J. Landman

Distribution:

SEYMOUR
1270 London Road
LONDON SW16 4DH

Printed in the Netherlands by NDB, Zoeterwoude

Overseas editions:

FRANCE
Elektor sarl
Les Trois Tilleuls
B.P. 59; 59850 NIEPPE
Editors: D.R.S. Meyer; G.C.P. Raedersdorf
GERMANY
Elektor Verlag GmbH
Stüsterfeld Straße 25
5100 AACHEN
Editor: E.J.A. Krempelsauer
GREECE
Elektor EPE
Kariskaki 14
16673 Voula—ATHENA
Editor: E. Xanthoulis
HUNGARY
Elektor Elektronikai folyóirat
1015 Budapest
Batthyány u. 13
Editor: Lakatos András
INDIA
Elektor Electronics PVT Ltd
Chhotani Building
52C, Proctor Road, Grant Road (E)
BOMBAY 400 007
Editor: C.R. Chandarana

ISRAEL

Elektoreal
P.O. Box 41096
TEL AVIV 61410
Publisher: M. Avraham
NETHERLANDS
Elektuur BV
Peter Treckpoelstraat 2–4
6191 VK BEEK
Editor: P.E.L. Kersemakers

PORTUGAL

Ferreira & Bento Lda.
R.D. Estefani, 32-1^{oo}
1000 LISBOA

Editor: Jeremias Sequeira

SPAIN

Resistor Electronica Aplicada
Calle Maudes 15 Entlo C.
28003 MADRID

Editor: Agustin Gonzales Buelta

SWEDEN

Electronic Press AB
Box 5505
14105 HUDDINGE
Editor: Bill Cedrum

causes and the formulation of expeditious recovery strategies may be required.

With the ten-fold increase in the performance of computers that has been occurring every five years, and costs that have been steadily reducing, many more companies are embarking upon the process of replacing old labour-intensive practices with computer-based systems. But as this trend gathers pace, it is becoming increasingly apparent that the advances made in microelectronics and computer hardware have not been matched

by equivalent improvements in software.

Furthermore, companies attempting to remedy this situation with their own software development programmes are finding that the projects tend to overrun both the intended timescale and budgets. The result, all too frequently, is a major disruption or severe operational difficulties.


ERA's software-with-confidence service includes rigorous systems analysis, advice on the use of appropriate computer languages, guidance on the organizing

of software development teams, selection of a suitable external software house where necessary, the production of methodologies for checking software for compliance with specifications and the formulation of training programmes for operators.

ERA is an independently funded organization and has no alliance with softwarehouses or suppliers. Advice given is, therefore, completely impartial.

ERA Technology Ltd, Cleeve Road, Leatherhead KT22 7SA, England. Telephone (0372) 374151; Fax (0372) 374496.

EUTELSAT RADIO LINE-UP

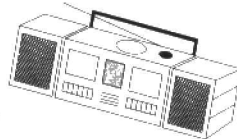

Channel	Tr.	Freq.	Audio / Language	Beam
EUTELSAT II-F1 - 13°E				
BBC World Service	25V	10.987	7.38 - English	Widebeam
BBC World Service	25V	10.987	7.56 - other langs	Widebeam
Deutsche Welle	27V	11.163	7.02 - German, 7.20 - European langs 8.10 - other langs	Widebeam
Radio 10 Gold	34H	11.678	7.92/8.10 - Dutch	Superbeam
Radio Contact	34H	11.638	7.02 - French 7.92 - Flemish	Superbeam
Radio Free Europe	21H	11.095	7.74 - Czech, 7.92 - Baltic langs 8.10 - Polish	Superbeam
RFI	26V	11.080	6.60 - French	Widebeam
World Radio Network	32H	11.554	7.74 - mixed	Superbeam
VOA	27V	11.163	7.92 - European langs	Widebeam
VOA Europe	27V	11.163	7.38/7.56 - English	Widebeam
EUTELSAT II-F2 - 10°E				
Cadena Dial	27V	11.178	7.56 - Spanish	Widebeam
Cadena SER Los 40 Principales	27V	11.178	7.38 - Spanish	Widebeam
Cadena Convencional	27V	11.178	7.74 - Spanish	Widebeam
EFE Radio	22H	11.149	7.02 - Spanish	Widebeam
EFE Radio	22H	11.149	7.20 - Spanish	Widebeam
Radio Exterior	22H	11.149	7.56 - Spanish	Widebeam
RNE	22H	11.149	7.38 - Spanish	Widebeam
Radio Liberty	38V	11.617	7.02 - Russian 7.20 - Ukrainian	Widebeam
Radio Free Europe	38V	11.617	8.10 - Bulgarian	Widebeam
Show Radio	37V	11.575	7.02/7.20 - Turkish	Widebeam
EUTELSAT II-F3 - 16°E				
Croatian Radio	20H	10.987	7.02 - Serbo-Croat	Superbeam
Egypt Radio	27V	11.178	7.02 - Arabic	Widebeam
Middle East Programme	27V	11.178	7.38 - Arabic	Widebeam
No. 1 FM	38V	11.617	7.74 - Turkish	Widebeam
Radio Renancencia	37V	11.575	7.38/7.56 - Portuguese	Widebeam
Radio Tunis International	39V	11.658	7.02 - French	Widebeam
Radio Tunis International	39V	11.658	7.20 - Arabic	Widebeam
RDP Antena 1	37V	11.575	6.60 - Portuguese 8.10/8.22 - Portuguese	Widebeam
RDP Internacional	37V	11.575	8.46 - Portuguese	Widebeam
RFM	37V	11.575	7.74/7.92 - Portuguese	Widebeam
Voice of the Arab World	27V	11.178	7.20 - Arabic	Widebeam
EUTELSAT II-F4 - 7°E				
Radio Tek	27V	11.163	7.02/7.20 - Turkish	Widebeam
RIK I Radio	22H	11.144	6.60 - Greek	Widebeam
Radio Belgrade	34H	11.638	7.02 - Serbo-Croat	Widebeam

VOC/2/93-2

For details of the radio information on EUTELSAT 24 hours a day, call 0161 271 2338 and receive news by phone or fax.

NB: This information is subject to change at the discretion of EUTELSAT's customers

NEW FROM MAPLIN

The **Talking Digital Multimeter** provides additional safety and convenience when working on mains or high voltage equipment, or in conditions where positioning of the test probe makes a meter reading difficult or impossible. A 3-position switch selects off, single or auto. In single mode, an announcement is made only when a 'talk button' on the positive probe is pressed, or when there is a change in range in manual mode or change of function. In auto mode, an announcement is made whenever a new reading is captured.



The **64K Electronic Organizer and Diary** has a qwerty style keyboard and a large, 8-line dot matrix display (256 characters) with 5x7 font. The memory can store about 1400 names or 850 appointments, and names and telephone numbers can be recalled by direct, sequential and repeat data search methods. There is also an appointment reminder with calendar alarm interface, anniversary feature (reminds of special events), home data and time format, daily alarm for three daily events or routines, world time, weather data and useful information for 128 major cities, 'secret' feature (up to eight characters) for security protection of telephone data, and many more. **Maplin Electronics, P.O. Box 3, Rayleigh Essex SS6 8LR, England. Telephone (0702) 554 161; Fax (0702) 553 935.**

Courtesy European Telecommunications Satellite Organization

SPECTRUM VU METER

Design by T. Giesberts

Making an audio signal visible on a display is something that appeals to many audio & hi-fi enthusiasts. Most commercial audio equipment is now provided with a display in the form of one or more light bars that move in rhythm with the music. The proposed VU meter offers seven or eight bars that each serve a certain part of the audio spectrum.


A VU meter used to be a moving-coil meter that indicated the drive power of, for instance, a tape recorder in 'Volume Units'. Modern equipment is normally provided with a VU meter consisting of a bar of small LEDs per channel.

The VU meter described is intended primarily for use with an amplifier and does not only show the strength of the incoming or outgoing signal, but also its spectral distribution. The sound spectrum is divided into seven or eight bands, each of whose strengths is shown on a 10-LED bar. All these LEDs do not present a construction problem, because use is made of two 5×7 or 5×8 matrix displays that are mounted one above the other. These displays are available in various sizes, from 18×26 mm to 61×72 mm.

Design considerations

The audio input signal is fed to a variable amplifier and then to seven filters (Fig. 1). The eighth filter shown is for use only with large displays that have eight LED bars. The lowest filter is a low-pass section, the five (or six in case of a large display) following ones are band-pass sections, and the highest is a high-pass section. To obtain a good split of the audio spectrum and yet keep the number of components in the filters to a minimum, the cut-off frequencies and Q factors have been chosen to give -10 dB transfer points of adjacent frequencies. That may seem a lot, but it should be borne in mind that the resolution of the display is 3 dB per step at the top and as much as 9 dB per step at the bottom.

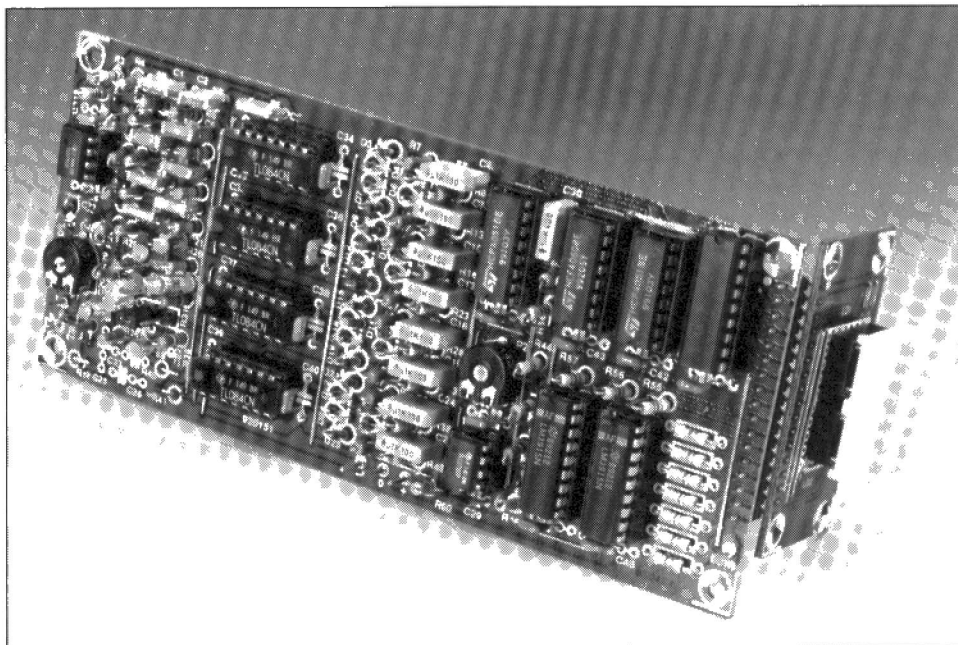To get an even distribution of the audio range of 20 Hz to 20 kHz, the central frequencies of the band-pass filters have been set to 130 Hz, 340 Hz, 880 Hz, 2.3 kHz, and 6 kHz. With a Q factor of 3, the filters interconnect just about at



their -10 dB points.

The cut-off frequency of the low-pass filter is set to 50 Hz and that of the high-pass section to 15 kHz. For small displays, these filters are third-order Butterworth types that fit in well with the band-pass sections, but for large displays their behaviour becomes more of a Chebishev nature.

The filter responses are shown in Fig. 2.

The filter outputs are passed to peak detectors. These are rather more complex than in Fig. 1, but that will be reverted to in the circuit description.

The seven (eight) direct voltages are fed to a multiplexer that passes one of them via buffer-amplifiers to a double comparator-buffer formed by two LED driver ICs. These quasi-series connected ICs enable a range of some 50 dB to be displayed.

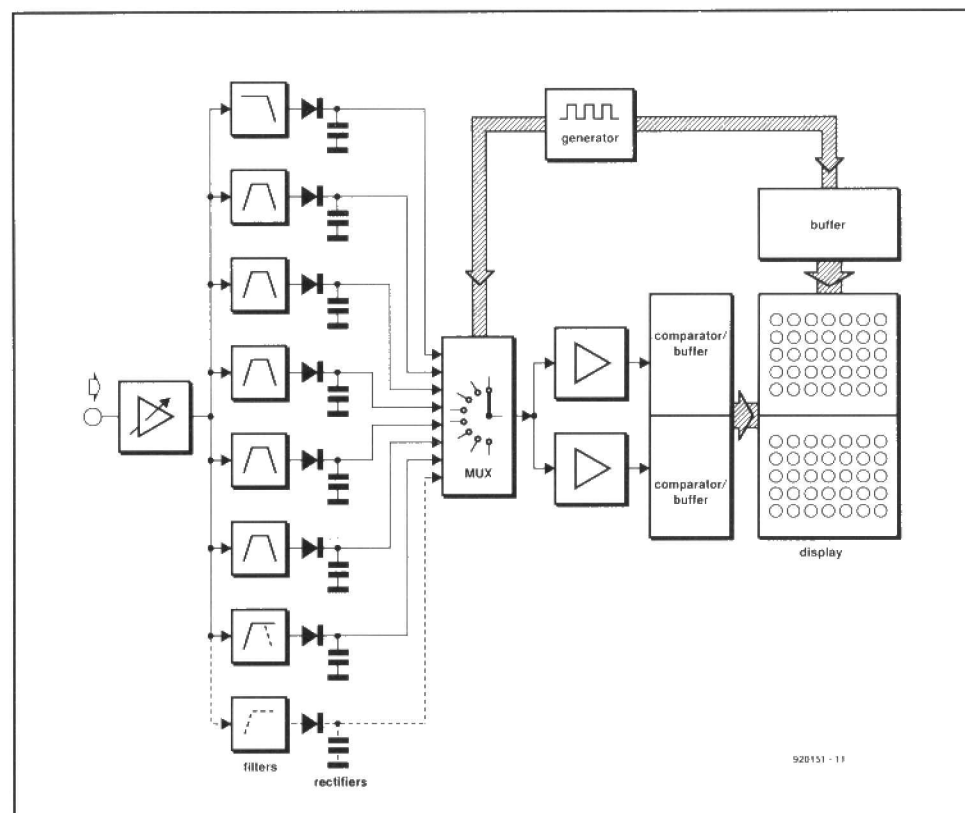


Fig. 1. Block schematic of the VU meter.

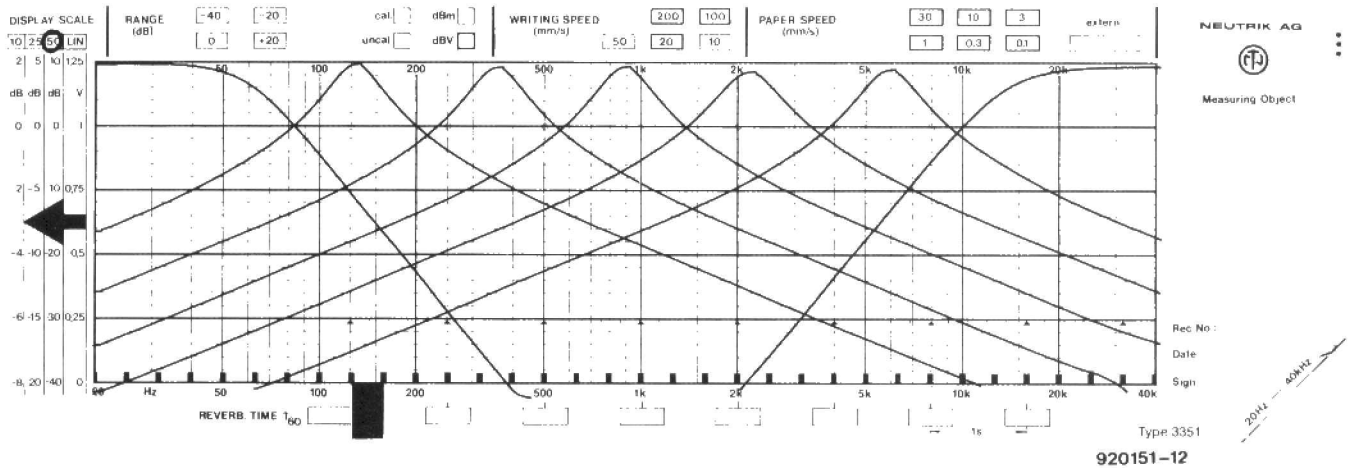


Fig. 2. Response curves of the low-pass, high-pass and band-pass filters when a seven-bar display is used.

A frequency generator provides the clock that switches the multiplexer to each successive direct voltage. At the same time, this signal actuates the LED bar associated with that direct voltage via a number of buffer stages, so that this bar displays only the level monitored at that instant.

The circuit

The audio input is applied to K_1 (see Fig. 4) and from there to IC_1 via P_1 , which enables it to be attenuated as required. The amplifier has a gain of about 16 dB. The output of IC_1 is fed to the seven or eight filter sections. The multiple feedback band-pass filters are formed by IC_{2a} , IC_{3d} , IC_{3a} , IC_{4d} , and IC_{4a} . As already mentioned, their Q factor is 3.

The third-order low-pass filter, which has a cut-off frequency of 50 Hz, is based on IC_{2d} .

The third-order high-pass filter, which has a cut-off frequency of 15 kHz, is based on IC_{5d} .

If a 10×8 LED matrix is used, the eighth filter needed is based on IC_{5a} . In that case, the high-pass filter based on IC_{5d} is converted to a band-pass section (whence the duplicated component indications; in the C_{20} position a resistor is then used). Table 1 lists all the component values in case eight filters are used.

The rectifiers are pseudo-active types to ensure proper coverage of the display range of 50 dB. In the prototype, standard passive rectifiers, even Schottky types, gave serious deviations (in some case, a 30 dB signal was attenuated to no less than 12 dB by the rectifier). The design finally chosen consists of a passive rectifier, consisting of a diode (D_5 , D_8 , D_{11} , D_{14} , D_{17} , D_{20} , D_{23}), a capacitor (C_4 , C_7 , C_{10} , C_{13} , C_{16} , C_{19} , C_{24}) and a discharge resistor (R_8 , R_{13} , R_{18} , R_{23} , R_{28} , R_{33} , and R_{38}), coupled with an active compensating

device (IC_{2c} , IC_{2b} , IC_{3c} , IC_{3b} , IC_{4c} , IC_{4b} , and IC_{5c}).

The active devices compensate the forward bias of the associated diodes as well as the discharge of the capacitors through the diodes when these conduct.

Since each of the ICs, connected in a voltage follower configuration, has negative feedback through two anti-parallel diodes, its output will always be larger by the forward bias of one of the diodes (D_3 , D_6 , D_9 , D_{12} , D_{15} , D_{18} , D_{21}) than the input. That bias depends to some extent on the current, which here is determined by the load resistor (R_7 , R_{12} , R_{17} , R_{22} , R_{27} , R_{32} , R_{37}). The diodes mentioned above are of a type that is identical to the rectifier. The type of the other diode in the feedback loop is not so important.

When the input is small, the drop across D_3 , D_6 , and so on, may be increased by reducing the value of R_7 , R_{12} ,

and so on.

Outputs Q_3 , Q_4 and Q_5 of oscillator-divider IC_8 switch multiplexer IC_6 at a frequency of about 400 Hz, so that at all times one of the output voltages of the rectifiers is connected to the comparator and drive section, IC_9 , IC_{11} , IC_{12} .

The same three Q outputs of IC_8 are also linked to binary-to-decimal converter (BDC) IC_7 . This converter ensures (via a number of buffers contained in IC_{10}) that the LED bar associated with the direct voltage output of the multiplexer at that instant is powered.

When all LEDs of a small display with seven bars light, the average current drawn is 263 mA.

The multiplexer is linked to IC_{11} and IC_{12} via two opamps, IC_{9a} and IC_{9b} . The first serves as a buffer for IC_{11} , while the second not only buffers the signal to IC_{12} , but also amplifies it $\times 32$.

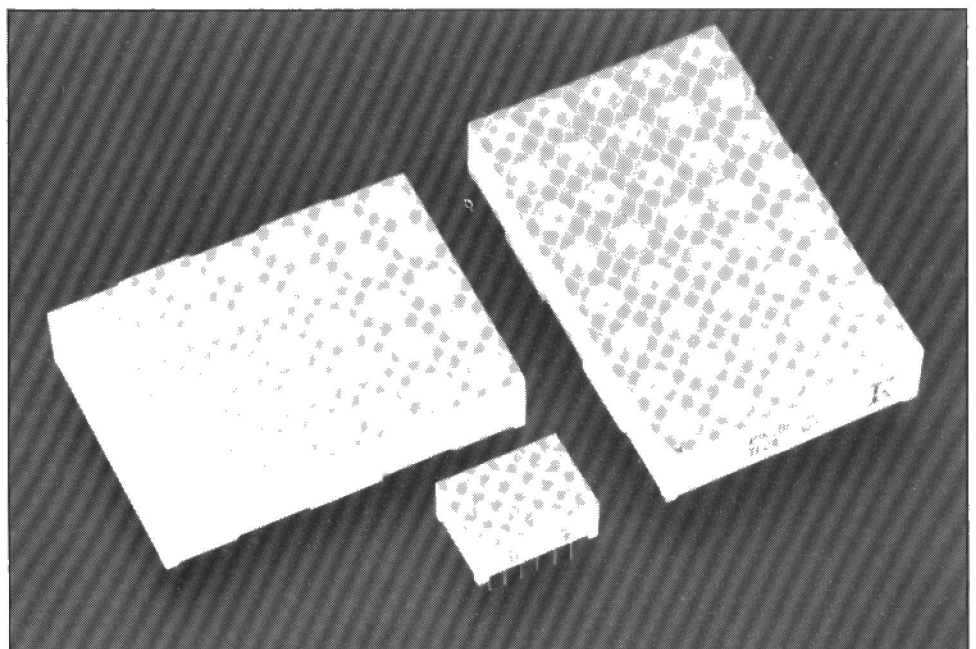


Fig. 3. The displays are available in a variety of sizes.

Circuits IC₁₁ and IC₁₂ drive the rows of the display. Each of them contains a 10-step comparator, a variable reference source and a drive circuit for the ten LEDs. Since at the underside of the display larger steps are required than at the top, most outputs of IC₁₂ are not

used. In that way, the steps on the display are (in dB): 0, -3, -6, -9, -15, -21, -27, -33, -41, and -50.

Resistors R₄₈-R₅₇ serve not so much as current limiters (the outputs of the LM3915s are current sources), but rather as dissipation limiters for the drive trans-

sistors contained in IC₁₁ and IC₁₂.

The power supply needs to provide a stabilized, symmetrical voltage; the positive supply line must be able to deliver a current of at least 330 mA, and the negative line one of about 35 mA.

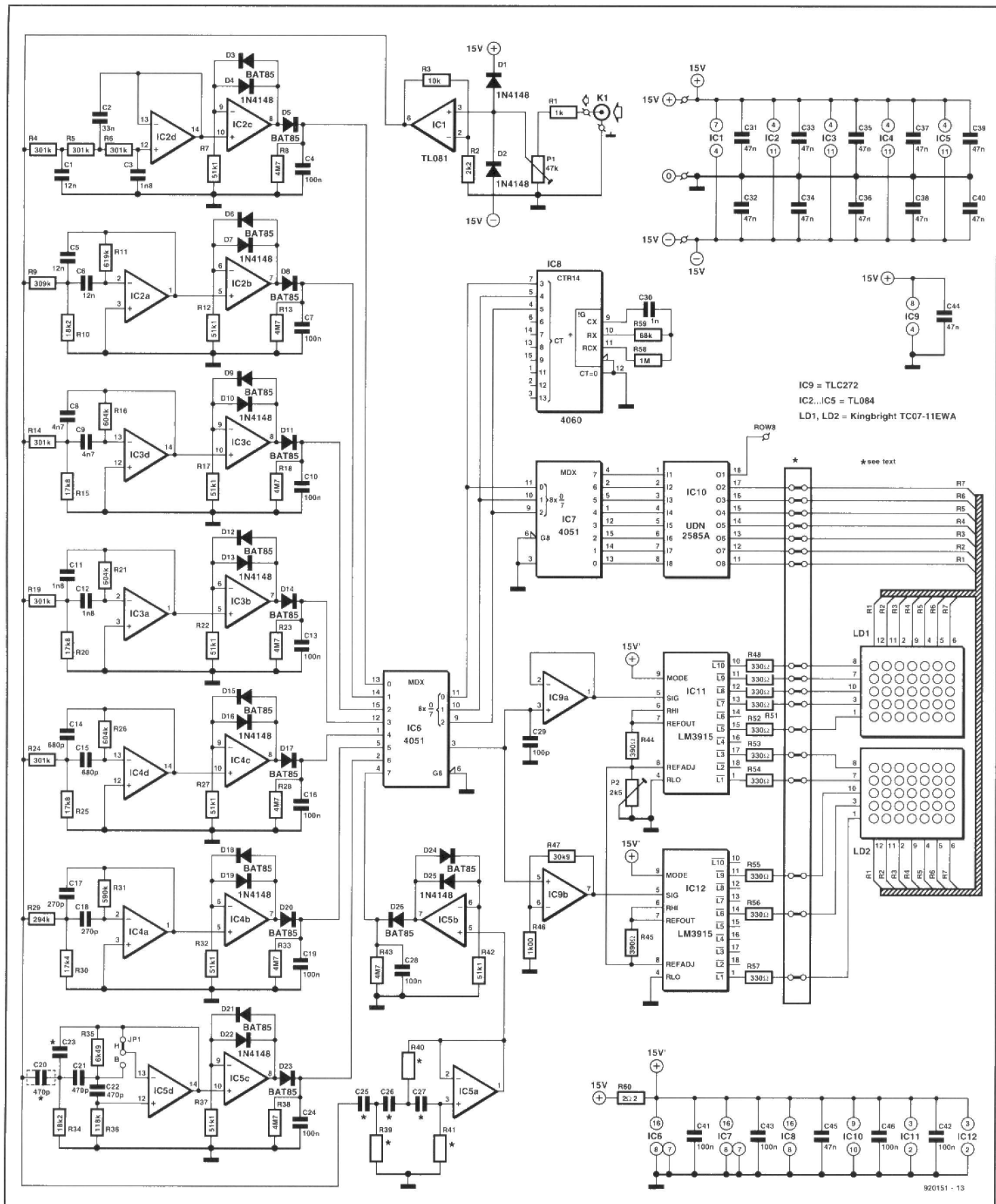


Fig. 4. Circuit diagram of the VU meter.

Construction

The VU meter is most conveniently built on the printed-circuit board shown in Fig. 5. Start with cutting off the display section if that is to be located elsewhere. Then, all components can be fitted. Note that most resistors and all diodes should be mounted upright. The 270 pF, 470 pF and 680 pF capacitors must be polystyrene types to prevent too high damping of the filters. These capacitors must also be mounted upright.

Once the boards have been completed, they must be interlinked by an angled header (see photograph on p. 8) or 17

discrete, short wires.

The power for the meter may be drawn from the equipment into which it is built, but, owing to the current requirement on the positive line, it is best to build a small, separate supply.

If a larger display is used than shown on the PCB, it must be connected to the board via suitable connectors or half IC sockets. The display section of the board is then useless.

When a small display is used, jumper JP₁ on the board must be placed in position 'H'. Resistors R₄₁ and R₄₃ must be replaced by a wire bridge.

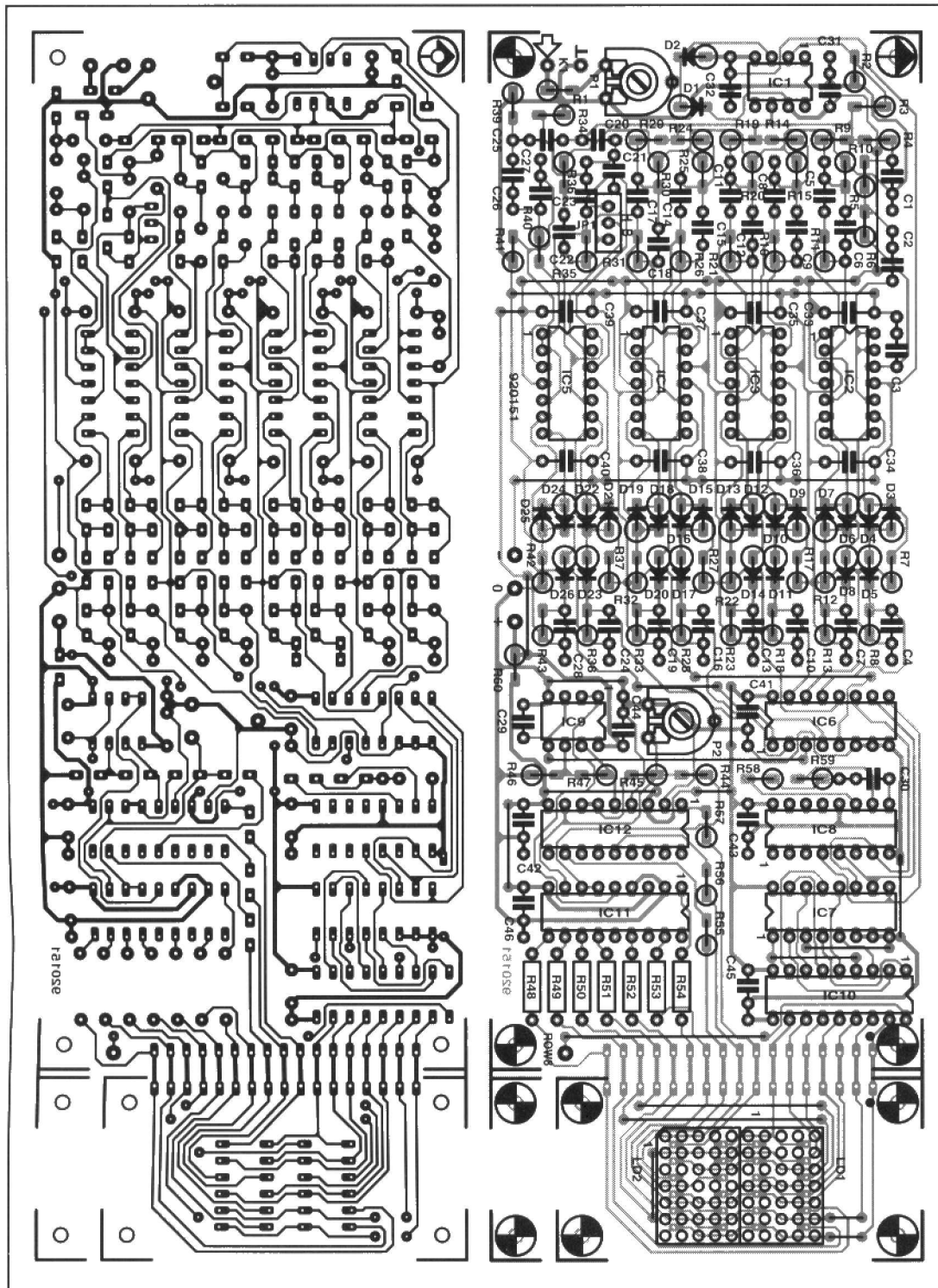


Fig. 4. The printed-circuit board for the VU meter.

PARTS LIST

Resistors:

R1=1 kΩ
R2=2.2 kΩ
R3=10 kΩ
R4, R5, R6, R14, R19, R24=301 kΩ, 1%
R7, R12, R17, R22, R27, R32, R37=51.1 kΩ, 1%
R8, R13, R18, R23, R28, R33, R38=4.7 MΩ
R9=309 kΩ, 1%
R10, R34=18.2 kΩ, 1%
R11=619 kΩ, 1%
R15, R20, R25=17.8 kΩ, 1%
R16, R21, R26=604 kΩ, 1%
R29=294 kΩ, 1%
R30=17.4 kΩ, 1%
R31=590 kΩ, 1%
R35=6.49 kΩ, 1%
R36=118 kΩ, 1%
R44, R45=390 Ω
R46=1.0 kΩ, 1%
R47=30.9 kΩ, 1%
R48-R57=330 Ω
R58=1 MΩ
R59=68 kΩ
R60=2.2 Ω
P1=47 kΩ preset
P2=2.5 kΩ preset

Capacitors:

C1, C5, C6=12 nF
C2=33 nF
C3, C11, C12=1.8 nF
C4, C7, C10, C13, C16, C19, C24=100 nF
C8, C9=4.7 nF
C14, C15=680 pF*
C17, C18=270 pF*
C20, C21, C22=470 pF*
C29=100 pF
C30=1 nF
C31-C40, C44=47 nF, ceramic
C41, C42, C43, C45, C46=100 nF, ceramic
*polystyrene, axial

Semiconductors:

D1, D2, D4, D7, D10, D13, D16, D19, D22=1N4148
D3, D5, D6, D8, D9, D11, D12, D14, D15, D17, D18, D20, D21, D23=BAT85
IC1=TL081
IC2-IC5=TL084
IC6, IC7=4051
IC8=4060
IC9=TLC272
IC10=UDN2585A
IC11, IC12=LM3915

Miscellaneous:

JP1=terminal strip with 3-way jump lead
K1=audio socket
LD1, LD2=display with 5×7 matrix, e.g., Kingbright Type TC07-11EWA (larger types: TC20-11EWA; 5×8: TC24-11EWA
PCB Type 920151 (see p. 70)

Filter	f_c or f_s	Component values
IC _{3d}	57 Hz	R4=267 k Ω ; R5, R6=249 k Ω ; C1=22 nF; C2=120 nF; C3=1 nF
IC _{2a}	113 Hz	R9=274 k Ω ; R10=11.8 k Ω ; R11=549 k Ω ; C5, C6=18 nF
IC _{3d}	255 Hz	R14=324 k Ω ; R15=13.7 k Ω ; R16=649 k Ω ; C8, C9=6.8 nF
IC _{3a}	577 Hz	R19=294 k Ω ; R20=12.4 k Ω ; R21=590 k Ω ; C11, C12=3.3 nF
IC _{4d}	1030 Hz	R24=287 k Ω ; R25=12.1 k Ω ; R26=576 k Ω ; C14, C15=1.5 nF
IC _{4a}	2940 Hz	R29=280 k Ω ; R30=12.1 k Ω ; R31=562 k Ω ; C17, C18=680 pF (polystyrene)
IC _{5d}	6650 Hz	C20=309 k Ω ; R34=13.3 k Ω ; R35=619 k Ω ; R36=wire bridge; C22=not used; C21, C23=270 pF (polystyrene) Place JP1 in position B
IC _{5a}	13600 Hz	R39=11.8 k Ω ; R40=2.37 k Ω ; R41=294 k Ω ; C25-C27=470 pF (polystyrene)
IC _{5b}		R42=51.1 k Ω ; R43=4.7 M Ω ; C28=100 nF;

Table 1. Component values and frequencies for eight filter sections.


Calibration

Connect the meter to a point in the amplifier where a strong signal is present; this is normally the loudspeaker terminal in an output amplifier. Make sure that the amplifier is fully driven. Turn P_1 so that IC₁ is just not overdriven. If an oscilloscope is not available, connect a multimeter, set to the 10 V a.c. range, to the output of IC₁. If this is an inexpensive digital multimeter, use a low-frequency input signal, say, a couple of hundred hertz. Turn P_1 slowly till the meter reads 9.5 V r.m.s. Then, using an input signal at a frequency in the centre of the pass-band, say, 130 Hz or 340 Hz, adjust P_2 until the entire associated LED bar just lights. ■

YOUR PERSONAL UNIVERSAL PROGRAMMER

Superpro is a low cost programmer which can easily be attached to your PC for use in R & D. It comes with its own half card for high speed communication so you can still use your parallel port.

Superpro comes from California so you can be sure the latest devices will be supported. In fact the software is updated on an almost monthly basis. The extensive device list covers most popular logic and memory families such as Amd's Mach series as well as the popular Altera range EP310 to EP1810. Support is also included for popular gals such as 16V8 and 20V8 from a variety of manufacturers. Standard 24, 28, 32 and 40 pin e (e) proms are also catered for in the 40 pin universal ZIF socket. An added bonus is the ability to program a range of microcontrollers. PLCC devices can be programmed with special adaptors.

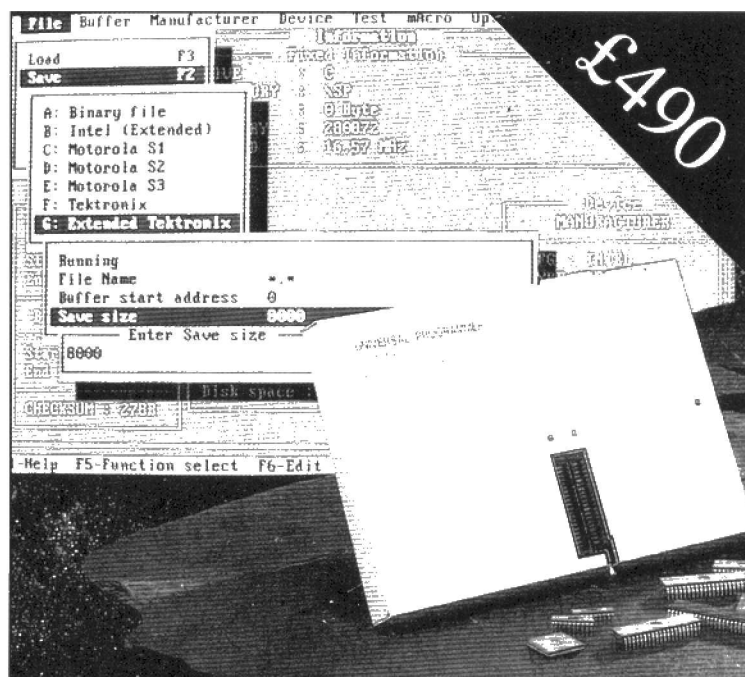

So before spending thousands of pounds on a new stand alone programmer why not have a look at Superpro for a ten day trial period?

LLOYD RESEARCH LTD

Tel: 0489 574040 for a device list

SCIENCE & TECHNOLOGY

Electricity from the wind

By Dr K.A. Nigim

Since the early 1890s, man has pioneered the technique of converting wind power into useful electricity. The development of engineering skills and the steady consumption of energy has speeded the development of the farm windmill into aerodynamically shaped turbines.

From the twenties, power from the wind was the main source of energy supply to rural areas worldwide. The modest reliability and social acceptability of the wind spinners encouraged researchers as well as environmentalists to seek ways to upgrade and increase the produced energy.

The energy crisis of the seventies revived the interest in wind power, and dozens of small wind machine manufacturers have started research into the means of increasing the generated capacity by introducing larger turbines and new designs.

Now, there are 45 companies worldwide specialized in manufacturing wind energy generators (WEGs) ranging from 100 W windmills (to charge 12 V batteries) to 4 MW windmills for direct connection to the national electricity network.

Types of windmill

Practically, windmills are classified into two categories:

1. horizontal axis wind turbines (HAWT);
2. vertical axis wind turbines (VAWT).

Both categories are shown in Fig. 1. There are several shapes, each having its own merits and requiring certain strengths of wind speed to start spinning.

There are as many as 31 types of turbine, all serving to convert the kinetic energy of the moving air to an energy associated with a mechanical motion, which in turn is converted into electricity by an electrical generator.

Each turbine model will have the capability of producing electrical power, P_w as given by the equation

$$P_w = K_w \cdot C_p \cdot R^2 \cdot V^3,$$

where

K_w is constant = $0.5\pi \cdot A_d$ (air density);
 C_p is power coefficient, whose value depends on the shape of the turbine used; for example, it is equal to 0.45 for a two-bladed turbine as shown in Fig. 2;
 R is the radius of the area swept by the blades;
 V is the free stream wind speed.

This equation gives the value of the

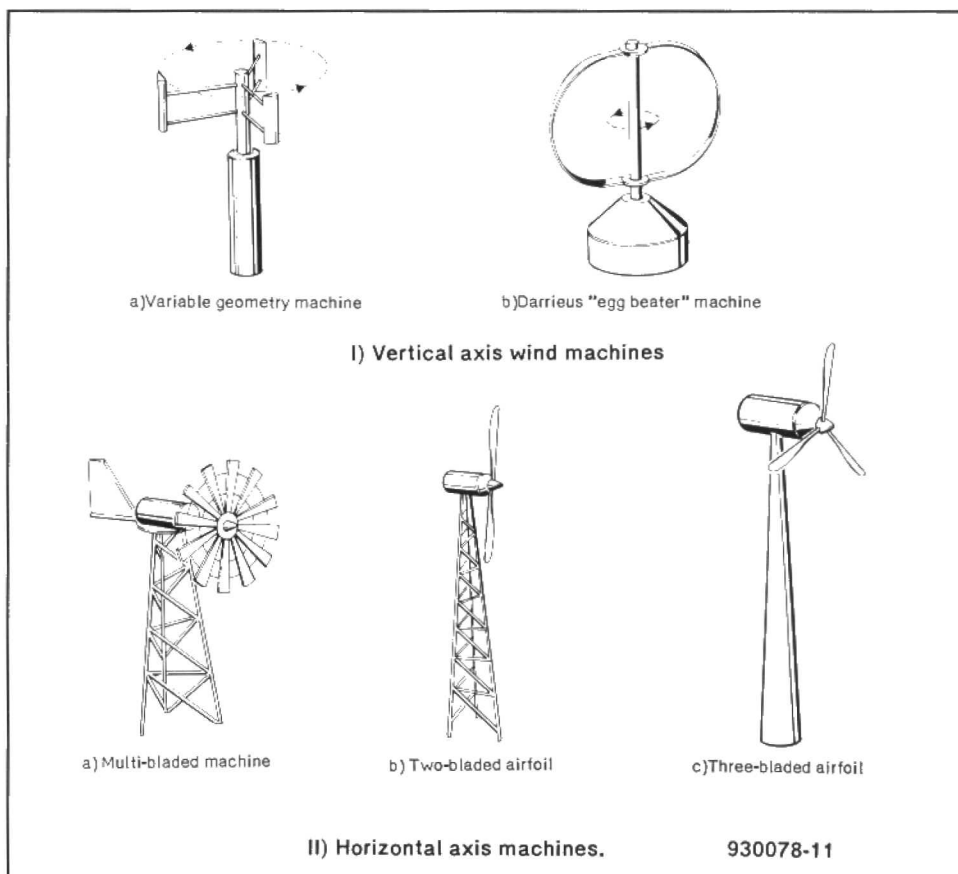


Fig. 1. Vertical axis and horizontal axis wind machines.

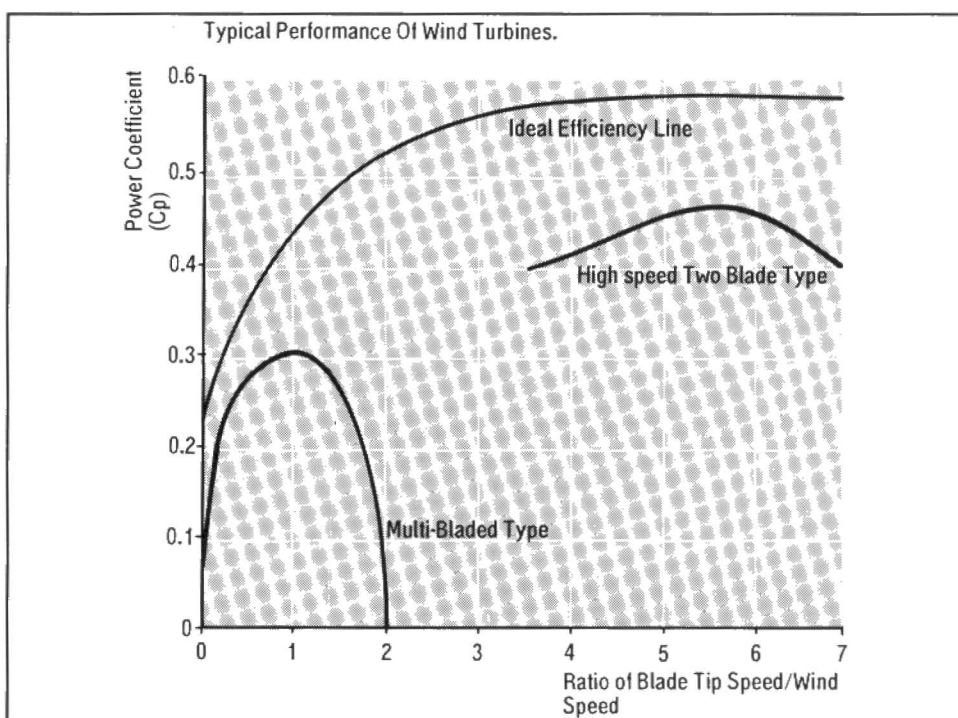


Fig. 2. Typical performance curves of wind turbines.

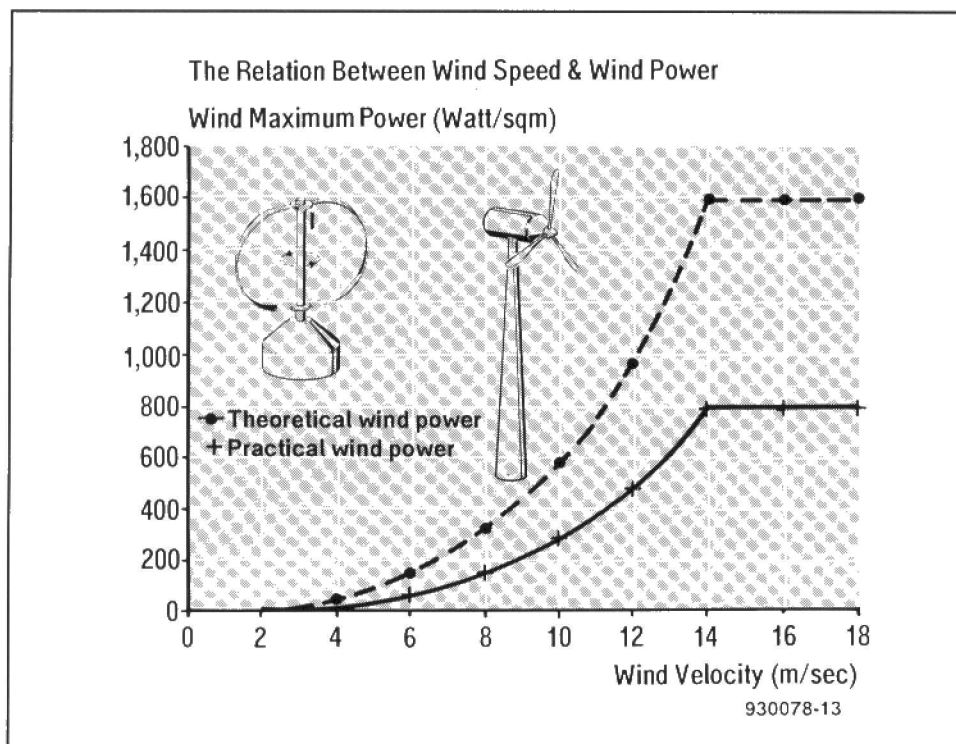


Fig. 3. Relation between wind speed and wind power.

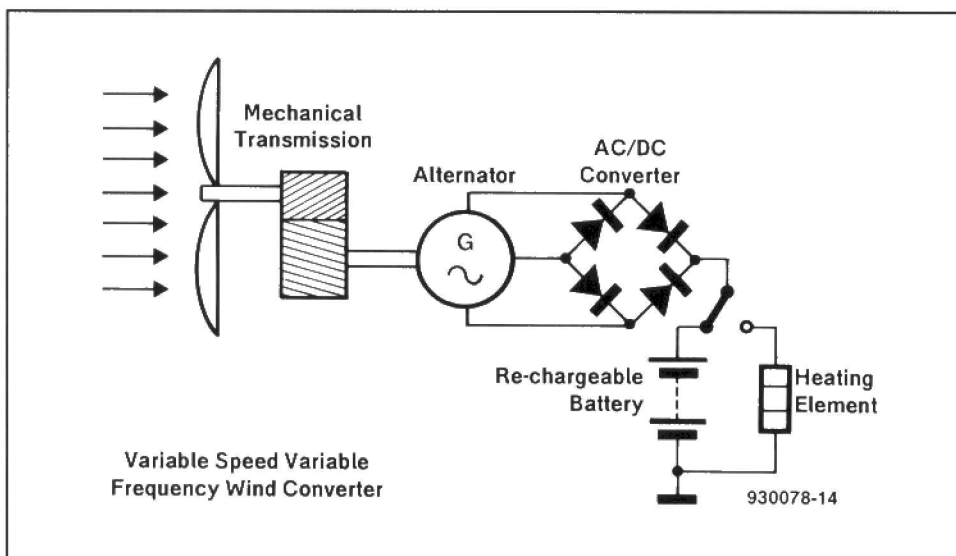


Fig. 4. Variable speed, variable frequency wind convertor.

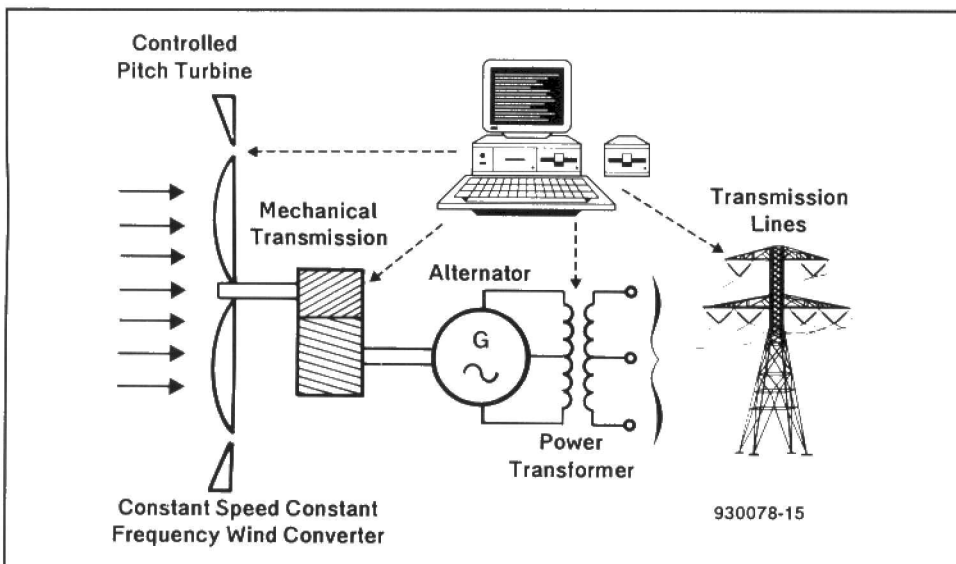


Fig. 5. Constant speed, constant frequency wind convertor.

maximum attainable power from a turbine. Owing to aerodynamic factors and other mechanical restraints, the power extracted is much smaller. A well-designed windmill achieves outputs that are 50–70% of the maximum theoretical power.

The dependence of power upon the cubic value of wind speed, as shown in Fig. 3, tends to limit the useful energy that can be extracted at low speeds. This fact presents a serious drawback to the use of wind converters in low wind-speed areas. On the other hand, gales are not welcome either, since they impose a danger to the mechanical parts of the wind turbines.

To overcome the unsteady nature of wind speeds, wind turbines are planted in groups located strategically around the selected site, which is known as a wind farm. In this way, a continuous supply of power may reasonably be expected at all times.

Wind power to electricity

Horizontal and vertical axis wind turbines with rotor diameters of 60–100 m (200–300 ft), feeding electricity into the national grid systems, are now in operation at many sites in Europe and the USA. The various schemes for interconnecting the generated electricity with power lines or for the supply of isolated communities can be classified into three groups:

- variable speed, variable frequency (VSVF);
- constant speed, constant frequency (CSCF);
- variable speed, constant frequency (VSCF).

VSVF generation

In this group, the generated output power is of variable voltage and frequency, so that the quality of the produced electricity is not suitable for household energy supply. The turbine is coupled either to an alternator or to a DC generator and supplies energy to insensitive loads such as heaters.

One practical realization of this group is to use a 12 V permanent magnet alternator to charge a battery. Figure 4 shows a schematic of the essential parts needed to convert wind power to a useful DC battery charger. Windmills in this group are of relatively simple design.


CSCF generation

The usual approach to provide a constant frequency alternating electric power is to drive the generator at constant shaft speed, thus producing output power at constant frequency. This is a must for trading in electricity with the public and other generating companies.

In most constant-speed drive systems, a control mechanism is necessary to control the speed of the rotating shaft. One way to regulate fluctuation of the shaft speed is to use a hydraulically operated pitch controller to adjust the pitch of the turbine blades so that the input power is held fairly constant.

The technology and degree of refine-

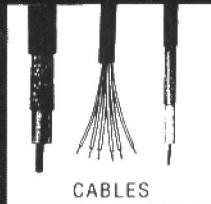Call us now! We have the widest range of components available - At competitive prices!




CABLES




CAPACITORS




VIDEO HEADS

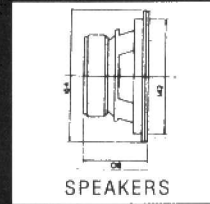

SPEAKERS

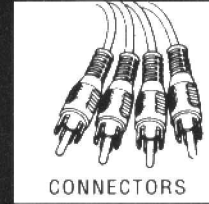

CONNECTORS

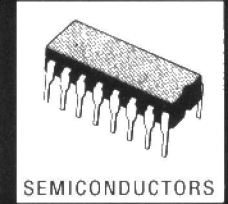

SEMICONDUCTORS

CRICKLEWOOD
ELECTRONICS

Cricklewood Electronics Ltd, 40 Cricklewood Broadway, London NW2 3ET.
Telephone: 081 452 0161 Faxsimile: 081 208 1441

All Major Credit Cards Accepted



ment involved in this scheme add to the initial costs of the windmill and it is, therefore, considered only for large wind turbines. Electricity is produced with two types of electrical machine as shown in Fig. 5. The electrical section is the standard type without the use of any power electronic devices.

VSCF generation

VSCF generating systems are those that have no pitch control mechanism fitted. Such a system is defined as an assembly of rotating electrical machinery, assisted by power equipment that is capable of converting the variable speed of the rotating mechanical energy into standard electrical energy of constant frequency, meeting the generating companies' trading rules.

There are various successfully operating schemes that use standard electrical machinery whose output is controlled by power electronic devices that are controlled by microprocessors. Figure 6 shows a schematic diagram of a system widely used all over the world.

The future

Already there is 324 MW of wind turbine generating capacity in the European Community. The greatest share of this is contributed by Denmark, which produces 1% of its electricity demand from the wind, with a target of increasing this to 20% by the turn of the century.

The Netherlands has similar plans. Enthusiasts in the UK, the area in the EC most exposed to wind, want to erect wind farms across the country and even out at sea to produce pollution-free electricity.

In the USA, special tax breaks have assisted in the creation of vast areas of the Californian desert to be planted with two and three bladed wind turbines. However, the technology used in many of these erected prototypes was not good enough and, although the windmills are still running, very little electricity is produced economically.

The experience of harnessing the wind is well shared by many developed countries. Geographic and demographic conditions pre-

vent many developing countries from installing a country-wide national grid for electricity distribution. The availability of windy sites is, therefore, greatly appreciated. Small-scale, isolated wind turbines are erected in the nearest suitable place. Integration between wind converters and conventional diesel engines is proving to be an economical solution to the need of continuous electricity demand.

Owing to the small size and/or the remote location of such power stations, the generating costs are markedly higher than the cost in interconnected national networks.

The present cost of electricity produced by wind generators in good wind sites is 2 to 3 times as high as that produced by conventional power stations. However, electricity from the wind is an environment-friendly energy source in spite of the noise the turbines produce during a breezy night.

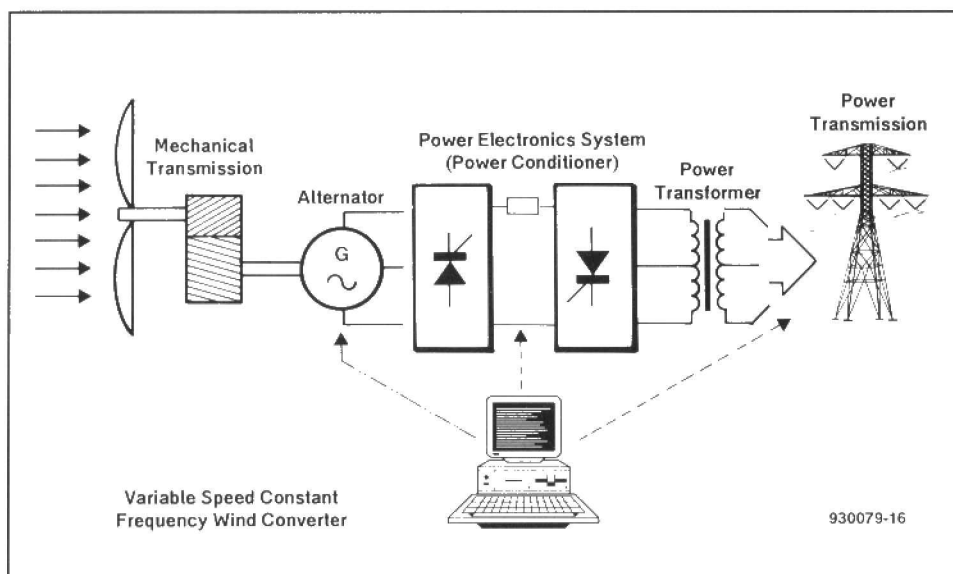


Fig. 6. Variable speed, constant frequency wind converter

INEXPENSIVE PHASE METER

Design by F. Hueber

The phase meter presented is based on just two CMOS ICs and a liquid-crystal display (LCD) to make it affordable with even the tightest budget.

The block schematic of the phase meter is shown in Fig. 1. Two amplifiers convert the input signal into a rectangular voltage that controls an edge-sensitive SR bistable (flip-flop). The average output of the bistable – between zero and the supply voltage – is directly proportional to the phase shift (0–360°). The measurement whose phase shift with respect to the reference signal at input B is to be determined is applied to input A. Every time the reference signal starts the positive half of its period, the leading edge of signal 1 sets the bistable. The bistable is reset when the phase-shifted signal at A starts the positive half of its period. In this way, the output of the bistable remains high longer the more the phase shift, that is, the average output voltage, increases. This is shown by timing diagrams 1 and 2 in Fig. 1.

Timing diagram 3 shows the situation when the phase shift is 0° or a multiple of 360°. In those cases, it may happen that sometimes the leading edge of input A occurs first and at other times the that of the reference signal. This will cause the output of the bistable to fluctuate between zero and the supply voltage. The meter will then give an undefined or instable reading because the average voltage cannot be exactly zero (0°) or the supply voltage (360°). This is one of the (small) prices to be paid for simplicity.

Another is that when the input signals are removed when the bistable is set, the meter reading remains at 360°. This error may be obviated by first removing the reference signal (B) and then the signal from A.

Circuit description

The two input channels are virtually identical—see Fig. 2. Only capacitors C_1 , C_7 and C_9 differ from their counterparts in the other channel. These capacitors serve to synchronize the phase pattern in the two channels.

Since the two channels are near-identical, channel B only will be discussed.

The signal—input at B—is applied to the circuit via C_1 , shunted by calibration capacitor C_9 , which prevents direct voltage being applied to the meter. Resistor R_2 and diodes D_1 and D_2 provide protec-

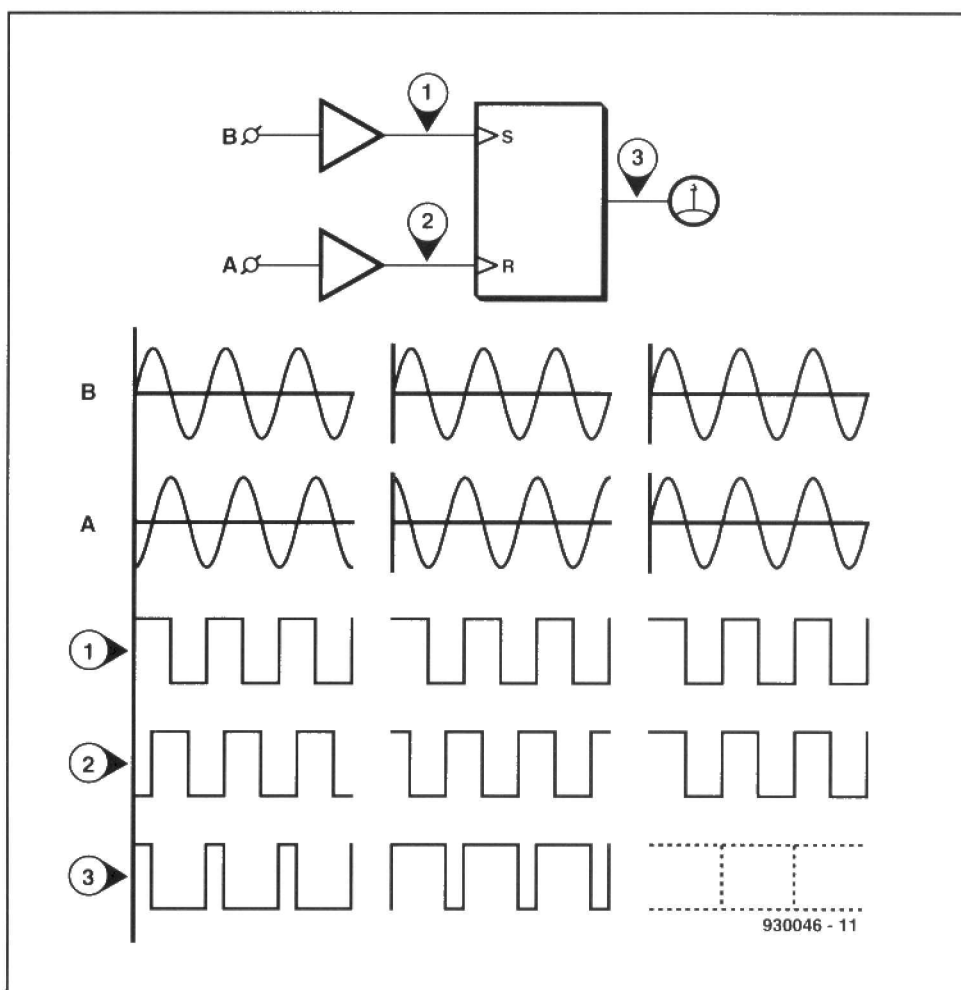
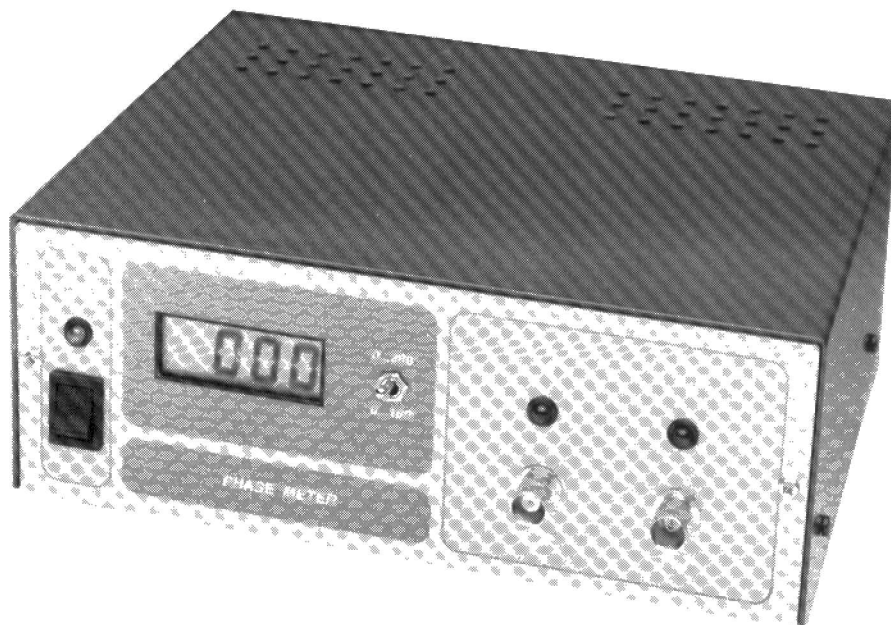


Fig. 1. The principle of the phase meter is quite simple.

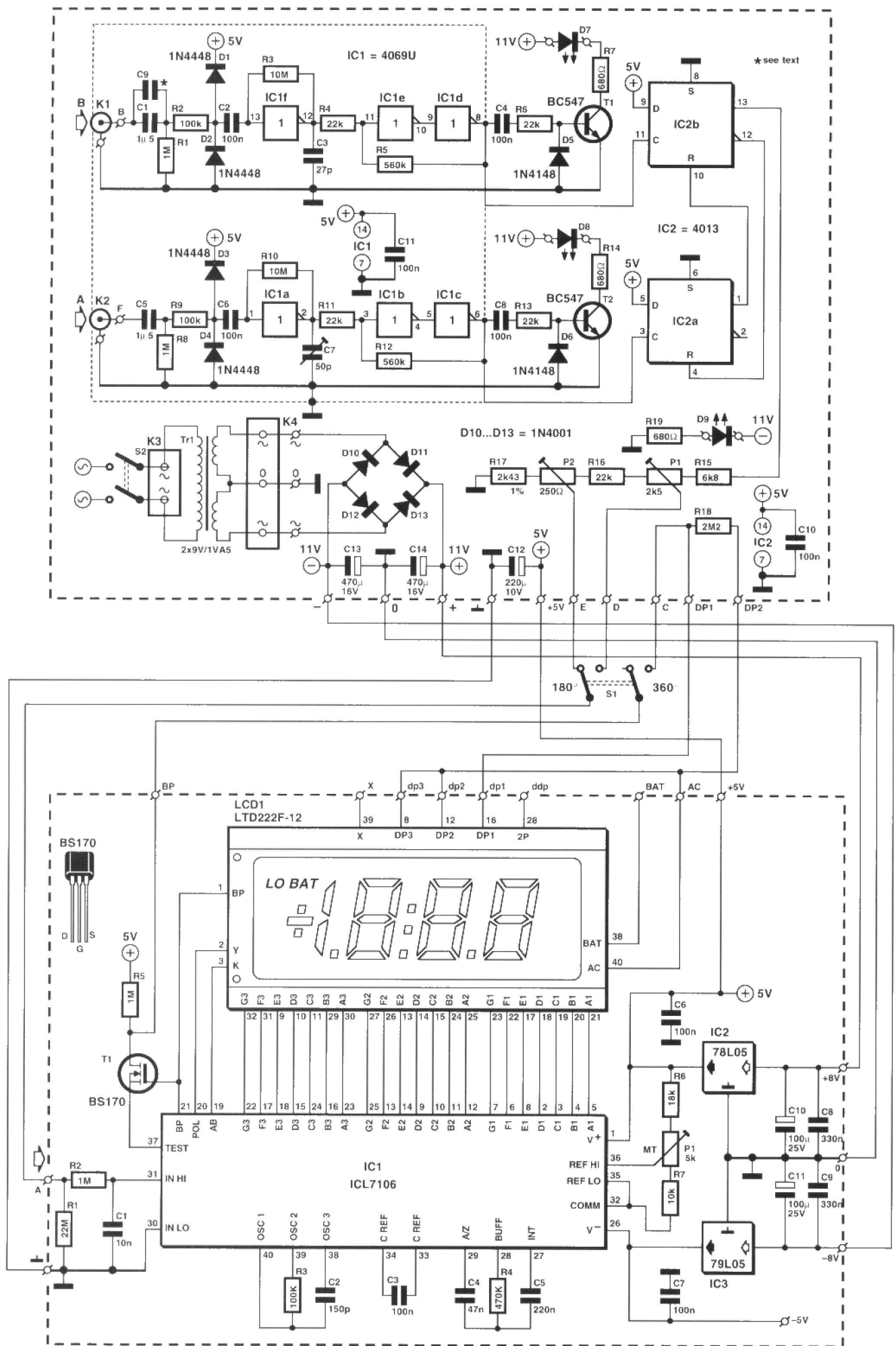


Fig. 2. Circuit diagram of the complete phase meter.

tion against too high alternating voltages at the input.

The signal is then applied to inverter IC_{1f} , which is not buffered, so it can be converted into a linear amplifier. In fact, IC_{1f} is arranged as an inverting amplifier, whose amplification is set to about $\times 10$ by R_2 and R_3 . This arrangement is not immediately recognizable owing to the protection diodes. Capacitor C_2 prevents any direct voltage generated by the protection circuit reaching IC_{1f} .

In contrast to that of a standard opamp, the input impedance of IC_{1f} is not easily determined. This is because of the protection circuit (which has a lower impedance at high voltages) and also since the inverter is a less ideal amplifier than an opamp. The input impedance varies between 200 k Ω and 300 k Ω , which is in most cases high enough to prevent loading of the circuit on test.

The amplifier is followed by a Schmitt trigger that converts the amplified signal to a neat rectangular signal. The trigger is formed by two series-connected inverters, IC_{1d} and IC_{1c} that have been provided with a measurement coupling via R_4 and R_5 .

The signal is subsequently applied to bistable IC_{2b} directly and to T_1 via C_3 and R_6 . The transistor is switched on briefly at each leading edge by the charging current through C_4 and this causes D_7 to light. This indicates that the signal is suitable for driving the bistable. If the LED goes out or flickers, the signal is too small or something else prevents the Schmitt trigger from regular toggling.

As already stated, the difference between the two channels is confined to a couple of capacitors that enable the phase behaviour in the two channels to be identical, or nearly so, over as large a frequency range as possible. This is particularly important at the extremes of the range, because where the frequency response

starts to roll off, phase shift ensues. This does no harm as long as the shift is the same in both channels and this is ensured by the calibration points.

The lower cut-off point is determined by the input circuit. Since the value of capacitors normally has a greater tolerance (usually 20%) than that of resistors, capacitors are used for calibrating. To that end, C_1 may be shunted by C_9 , which compensates small differences in value between C_1 and C_5 (C_1 and C_5 are compared and the smaller is fitted as C_1).

The upper cut-off point is determined primarily by parasitic capacitances in the inverters, but also by the small differences in the switching thresholds of the Schmitt triggers (bear in mind that the resistors have a tolerance of about 5%). The latter effect is particularly noticeable at high frequencies. The overall effect is compensated by C_3 and C_7 .

The SR bistable is not a standard component, but is composed of two D-type bistables with reset input, IC_{2a} and IC_{2b} . The D-bistables are interconnected in such a manner that every time one of them is set (the D inputs are permanently high), the other is reset. Just as the usual edge-triggered SR bistable, the present one has a non-permitted state and this occurs when two leading edges appear simultaneously. In that state, it is impossible to say whether the circuit interprets this as a set or a reset. This is the cause of the fact that, in theory, the meter has no stable null and cannot stably indicate multiples of 360° (which the meter 'sees' as 0°). This sounds worse than what happens in practice, because a few tenths of a degree are sufficient to give a stable display. Unreliable display of the phase shift occurs mainly when the frequency of the input signal is not stable (jitter).

The phase angle is displayed by an LCD that was also used for the 'inductance/capacitance meter' published last year¹. This shows, by means of filter R_7 - C_1 , the average value of the output voltage of the bistable.

Owing to the sensitivity of the DVM module and the fact that two meter ranges are required, the output voltage must be lowered to a suitable level. This is done with the aid of potential divider R_{15} - R_{17} - P_1 - P_2 . From that divider, the signal is applied to the meter via one contact of range switch S_1 . The other contact of this switch switches the decimal point for the least significant figure: the point is off when it is connected to the backplane signal (AC) via R_{18} ; it is on when it is connected to inverted backplane signal (BP).

The power supply uses the voltage regulators in the DVM module. Thus, the output of the mains transformer is taken from the transformer board to the phase meter where it is rectified and buffered and then applied to the regulators in the DVM module, which hold the

voltage steady at ± 5 V. That voltage is then returned to the phase meter board. Note that the regulators can easily cope with the 11 V unregulated input, although the connections on the DVM module state 8 V.

Since the circuit draws only a small current, it is also possible to power it by two 9-V batteries. That saves a transformer and some other components. To reduce the current even further, high-efficiency LEDs should be used. The series resistors must then be increased to 3.9 k Ω .

Construction

The printed circuit board for the phase meter and transformer is shown in Fig. 4. This board may be cut into two if, for instance, the transformer is not used. Even if the board is used as shown, it is advisable, because of the weight of the transformer, to use eight screws to fasten it. This results in a rather more rigid construction.

The input circuits must be screened along the dashed lines. The four soldering pins at the corners make this an easy operation. The lid should not be fitted until the calibration has been carried out (possible placing of C_9). It is advisable to drill a hole in the lid through which C_7 can be adjusted. Because of the screen, it is best to connect the screened wires to K_1 and K_2 at the underside of the board. This must be done, of course, before the board is fitted into the enclosure.

The values of capacitors C_1 and C_5 must be checked with a capacitance meter. The larger value should be used in the C_5 position. The difference between the two values is compensated by C_9 . To start with, make the value of this capacitor the same as the difference; the optimum value can be determined during the calibration.

The PCB for the meter module is shown in Fig. 5. Start with placing the wire bridges, because at a later stage that may be next to impossible. Place IC_1 in a low-profile socket, so that the display neatly fits over it. In case this proves troublesome, insert an extra terminal strip into the terminal strip of the display, so that the LCD sits slightly higher.

Because of the intricate routing of the supply lines, it is advisable to check them thoroughly and to measure the voltage at various positions after the supply has been switched on.

Strictly speaking, the LEDs should not light when the supply is switched on, but the sensitive input channels may well pick up some noise, which is then processed as 'input'. This property may be used to advantage by touching the live input terminal with a finger. If the input channels function correctly, the associated LED should light. With S_1 in position 180°, the decimal point before the

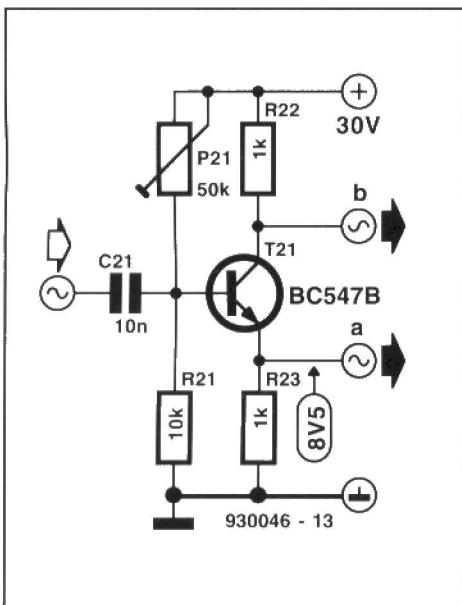


Fig. 3. Auxiliary circuit for calibrating the phase meter.

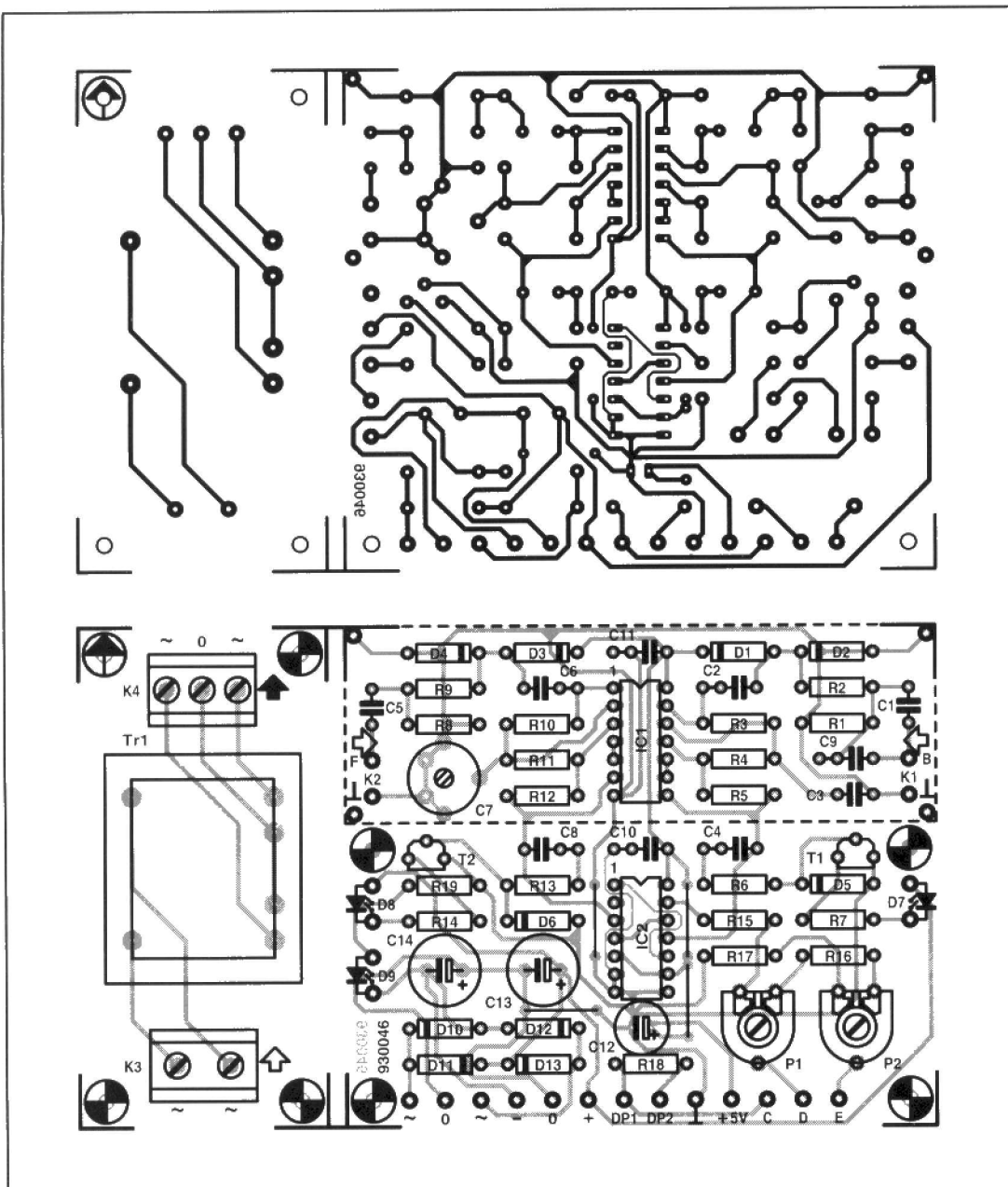


Fig. 4. Printed-circuit board for the phase meter and power supply. If necessary, the board is easily cut into two.

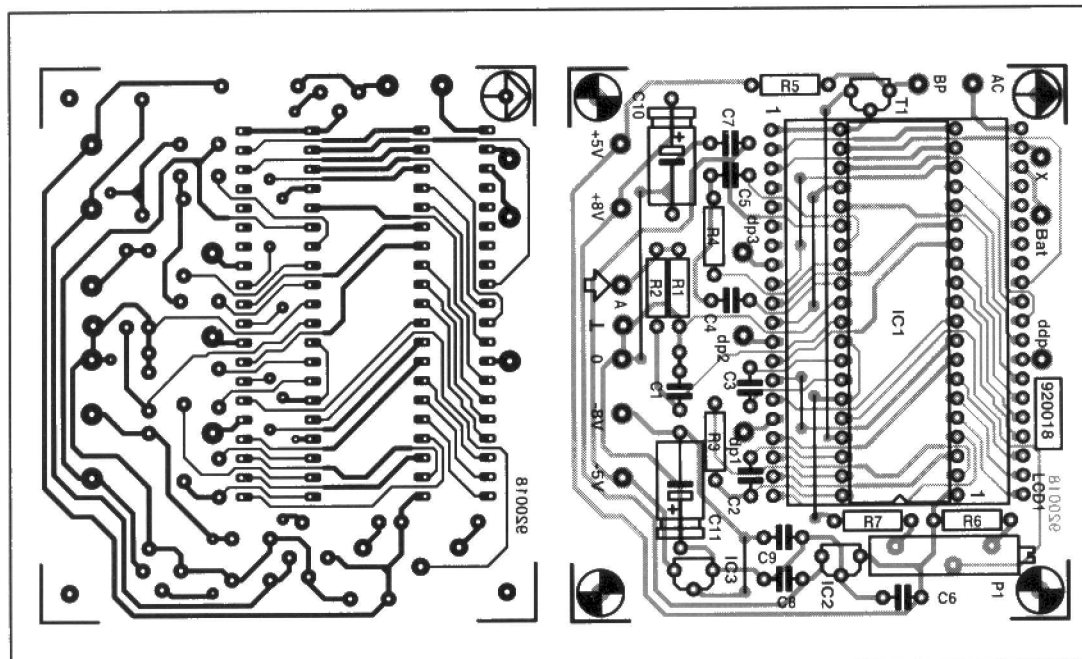


Fig. 5. Printed-circuit board for the meter module.

PARTS LIST

(Phase Meter)

Resistors:

R1, R8 = 1 MΩ
R2, R9 = 100 kΩ
R3, R10 = 10 MΩ
R4, R6, R11, R13, R16 = 22 kΩ
R5, R12 = 560 kΩ
R7, R14, R19 = 680 Ω
R15 = 6.8 kΩ
R17 = 2.43 kΩ, 1%
R18 = 2.2 MΩ
P1 = 2.5 kΩ preset
P2 = 250 Ω preset

Capacitors:

C1, C5 = 1.5 μF, MKT
C2, C4, C6, C8, C10, C11 = 100 nF
C3 = 27 pF
C7 = 50 pF trimmer
C9 = see text
C12 = 220 μF, 10 V, radial
C13, C14 = 470 μF, 16 V, radial

Semiconductors:

D1–D4 = 1N4448 or 1N4148
D5, D6 = 1N4148
D7–D9 = LED, red
D10–D13 = 1N4001
T1, T2 = BC547
IC1 = 4069U
IC2 = 4013

Miscellaneous:

K1, K2 = BNC plug
K3 = 2-way terminal block, pitch 7.5 mm
K4 = 3-way terminal block, pitch 5 mm
S1 = DPCO switch
S2 = double pole mains switch
Tr1 = mains transformer, 2×9 V, 1.5 A
Enclosure 210×80×160 mm (8 1/4×3 1/2×6 5/16 in)
PCB Type 930046 (p. 70)
Front panel foil 930046-F (p. 70)

(Meter module)

Resistors:

R1 = 22 MΩ
R2, R5 = 1 MΩ
R3 = 100 kΩ
R4 = 470 kΩ
R6 = 18 kΩ
R7 = 10 kΩ
P1 = 10-turn preset, 5 kΩ

Capacitors:

C1 = 10 nF
C2 = 150 pF
C3, C6, C7 = 100 nF
C4 = 47 nF
C8, C9 = 330 nF
C10, C11 = 100 μF, 25 V, radial

Semiconductors:

T1 = BS170
IC1 = ICL7106
IC2 = 78L05
IC3 = 79L05

Miscellaneous:

LCD1 = 3 1/2 digit LCD
40-pin low profile IC socket
2×20-way terminal strip
PCB Type 920018 (see p. 70)

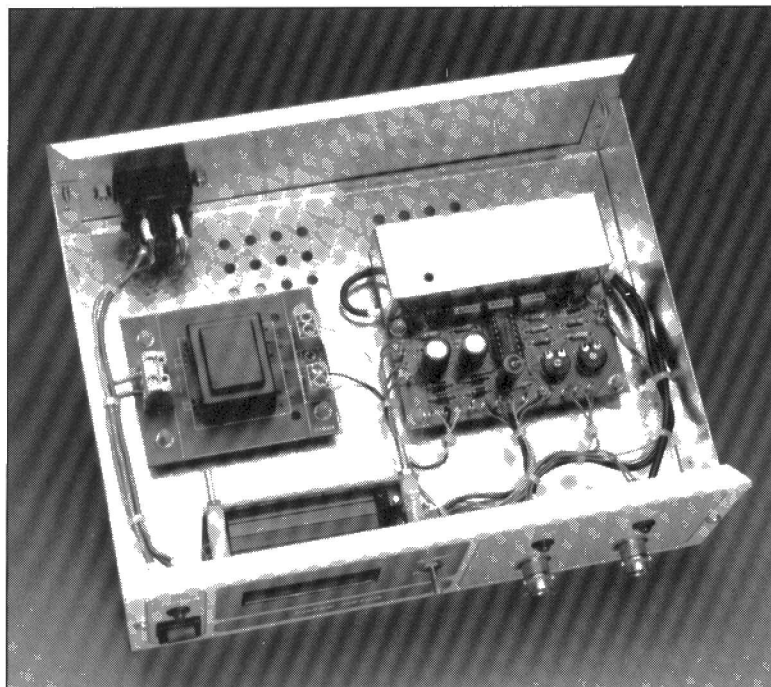


Fig. 6. Inside view of the completed phase meter.

last digit of the display should light. With a signal at input A (and input B short-circuited), the meter should read 0° . With a signal at input B (and input A short-circuited) and S_1 in position 360° , adjust P_1 until the meter reads 360° .

Preset P_2 (180° range) may be adjusted in a number of ways, but at all times with a 1000 Hz signal. One way is to use the 360° range as reference and to shift the signal by about 180° with the aid of an RC network. The preset is then adjusted until the meter readings in the 180° range and the 360° range are the same.


Another way is to use a signal source that can provide an output signal and its inverse (which is the same as one that is shifted by 180°). Again, adjust P_2 until the meter reads 180° .

A third method makes use of the auxiliary circuit in Fig. 3, which provides two signals that are one another's inverse. Adjust P_{21} in such a manner that the two signals look identical (or nearly so) on an oscilloscope. If an oscilloscope is not available, set P_2 to obtain an emitter voltage of 8.5 V. An input signal of 100 mV is fine. With the auxiliary circuit connected to the phase meter, adjust P_2 for a meter reading of 180° .

To determine the optimum value of C_3 and to adjust C_7 , either a signal source with inverted outputs or the circuit of Fig. 3 is required.

Start with lowering the frequency to between 100 Hz and 50 Hz. If everything is all right, the indicated phase angle (S_1 in position 180°) should not change by more than a few tenths of a degree. If it is more, the value of C_3 must be made a little lower or higher (this has to be tried out). Do the same with a frequency of 30 Hz. Then, adjust C_7 until the meter reads 180° again. If C_7 cannot be made

Fig. 7. The front panel foil for the phase meter is available through our Readers' services (see page 70).

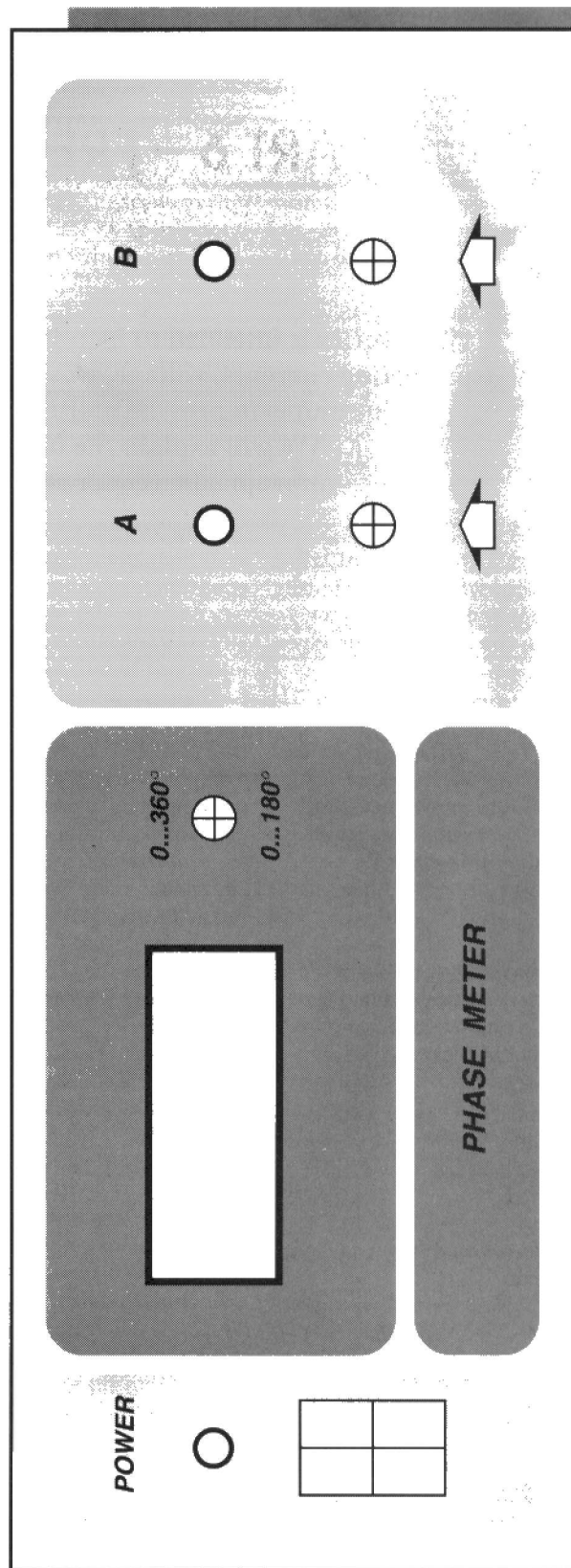

small enough, the value of C_3 must be increased slightly. If C_7 cannot be made large enough, shunt C_3 with a small, say, 27 pF, capacitor.

Finally, carry out these tests at a few different frequencies to make sure that everything works all right. Readjust the relevant controls where necessary. Put the lid on the screening of the input circuits and close the enclosure. [930046]

References

1. 'Inductance-capacitance meter', *Elektor Electronics*, March, April 1992.

FIGURING IT OUT

PART 6 – FREQUENCIES AND FILTERS

By Owen Bishop

This series is intended to help you with the quantitative aspects of electronic design: predicting currents, voltage, waveforms, and other aspects of the behaviour of circuits.

Our aim is to provide more than just a collection of rule-of-thumb formulas.

We will explain the underlying electronic theory and, whenever appropriate, render some insights into the mathematics involved.

In Part 5 we looked at what happens when an alternating pd is applied to an inductor. In Fig. 43, the applied pd is given by

$$U = U_0 \cos \omega t, \quad [\text{Eq. 31}]$$

where U_0 is the peak pd and ω is the angular frequency (more about this in a moment). We then showed that the current through the inductor is given by

$$I = I_0 \sin \omega t. \quad [\text{Eq. 32}]$$

We compared these equations to demonstrate the facts that I has the same frequency as U , but lags behind U by $\pi/2$ radian.

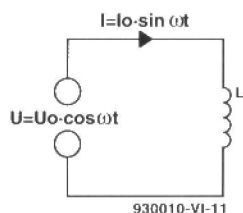


Fig. 43

First to clarify the quantity ω . This is related to frequency by the equation

$$\omega = 2\pi f,$$

where ω is in radian per second. Equation 31 could equally well be written as $U = U_0 \cos 2\pi ft$. In many instances, particularly when dealing with audio circuits, f is a more convenient quantity to use. However, it is often easier to deal with the single symbol ω than the multiple $2\pi f$ when integrating or differentiating, so we shall use either way of expressing frequency, depending on circumstances.

During the discussion of the

equations above, we derived an equation for I , in which

$$I = (U/\omega L) \sin \omega t.$$

At the time we said that the expression in brackets represents the peak value, I_0 , of a sinusoidally varying current, immediately replacing the expression by I_0 to produce Eq. 32. Now we will take time to look at this bracketed expression more closely. The expression gives the value of the peak current as

$$I_0 = U_0/\omega L.$$

This has the same form as the well-known equation for resistance:

$$I = U/R$$

and demonstrates that ωL is the equivalent of resistance. It is the **inductive reactance** of the inductor and has the symbol X_L :

$$X_L = \omega L. \quad [\text{Eq. 33}]$$

Like resistance, inductive reactance is one of the elements of the total **impedance** of a circuit and is expressed in ohm (Ω). Equation 33 shows that inductive reactance is proportional to inductance, as would be expected. The equation also shows that, unlike resistance, it is proportional to frequency: as the frequency increases, so does the inductive reactance.

Example: calculate the reactance of a coil, $L = 0.1$ mH, given a signal of (a) 100 Hz; (b) 1 MHz.

$$(a) \omega = 2\pi f = 200\pi = 628 \text{ rad s}^{-1}.$$

$$X_L = 628 \times 0.1 \times 10^{-3} = 0.0628 \Omega.$$

$$(b) \omega = 2\pi \times 10^6 = 6.28 \times 10^6 \text{ rad s}^{-1}.$$

$$X_L = 6.28 \times 10^6 \times 0.1 \times 10^{-3} = 628 \Omega.$$

Capacitive reactance

In Part 5 we also showed that, if a capacitor is being charged with a sinusoidally varying pd (Fig. 44), the current flowing into the capacitor is:

$$I = C(dU/dt).$$

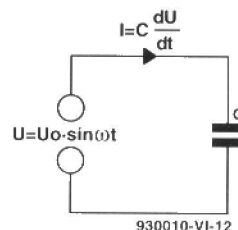


Fig. 44

Differentiating $U_0 \sin \omega t$ as one of the standard differentials, we find:

$$I = C(\omega U_0 \cos \omega t).$$

As C , ω and U_0 are all constants, we can replace their product with a single constant. The equation for current is, in fact, a cosine equation, where the single constant is I_0 , the peak current. In other words,

$$I_0 = \omega C U_0.$$

The argument follows the same lines as that above, leading to the conclusion that the **capacitive reactance** is given by

$$X_C = 1/\omega C. \quad [\text{Eq. 34}]$$

Equation 34 shows that X_C has features that are the opposite of those of X_L . It is **inversely** proportional to both capacitance and frequency. The higher the frequency, the lower the capacitive reactance. This is another example of a pair of duals.

Example: calculate the reac-

tance of a capacitor, $10 \mu\text{F}$, given a signal of (a) 100 Hz, (b) 1 MHz.

$$(a) \omega = 628 \text{ rad s}^{-1}, \text{ as above.}$$

$$X_C = 1/(628 \times 10 \times 10^{-6}) = 159 \Omega.$$

$$(b) \omega = 6.28 \times 10^6$$

$$X_C = 1/(6.28 \times 10^6 \times 10 \times 10^{-6}) = 0.0159 \Omega.$$

Total impedance

The calculations above are for purely inductive and purely capacitive circuits, as illustrated by Fig. 43 and 44. Now, to examine what happens in a circuit in which all three elements are present in series, as in Fig. 45.

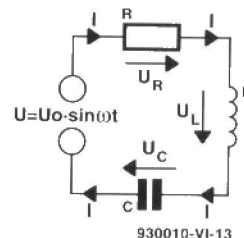


Fig. 45

Two facts are clear:

(a) The instantaneous current, i , through each of L , C , R , and the source is the same. If it were not, it would imply that current was leaking out of, or into, the circuit at some point.

(b) KVL applies to the instantaneous pds. The equation for the loop is:

$$U = U_R + U_L + U_C.$$

There are several ways of analysing the changing pds and currents in the circuit. Techniques using complex numbers or differential equations will be considered in a later issue. Here we adopt an approach that relies on geometry. The dif-

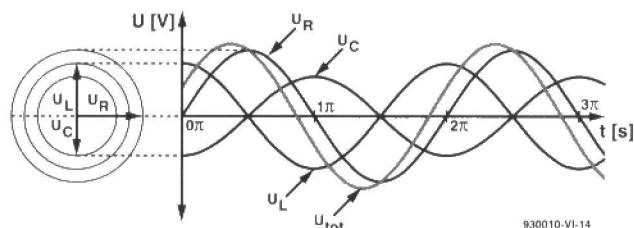


Fig. 46

difficulty with analysing this circuit is that the changing pds are usually not in phase with each other. The graphs of Fig. 46 show their relationships, with U_L leading U_R by $\pi/2$ and U_C lagging U_R by the same amount.

The current is in phase with U_R , since the pd across a resistor and the current through it are always in phase. The three vectors on the left represent the pds at the instant corresponding to the extreme left of the graph. The relative lengths of the vectors depend on the impedances found in a particular circuit at a given frequency. Their relative directions, however, are always as shown in the figure.

Comparison with the graph shows that these vectors represent **peak** pds. As time passes, that is, as we move toward the right-hand end of the graph, we can imagine this array of vectors rotating anticlockwise (with angular velocity ω), each vector remaining the same length and the angles between them remaining unchanged. The pds peak in order: U_L , then U_R , and finally U_C . This can be seen by examining the curves in Fig. 46. Since the three vectors retain their relative magnitude and keep in phase with each other, we can add them for the position shown on the left of Fig. 46, knowing that rotation does not affect the result.

Figure 47 shows the pds added by vector addition. The first step is to add U_L and U_C , which is easy because they lie in exactly opposite direction (U_C is negative). Call their resultant the **reactance voltage**, U_X . This leaves us just two vectors, U_R and

U_X , which are summed by drawing the diagonal of the vector rectangle. Since the vectors represent peak pds, the length of U represents the peak pd of the source. U_R is in phase with the current (as always), so it is clear from Fig. 47 that U is **not** in phase with I . This is the effect of the action of the capacitor and inductor. The **phase angle**, ϕ , in this example is positive (a lead) but, if U_C had been greater than U_L , it would have been negative (a lag).

Looking again at Fig. 46, it can be seen that U_R is the dominant pd in this particular circuit. U_L and U_C are very similar in magnitude and, since they are out of phase with each other (leading and lagging U_R by 90°) they almost cancel each other out. The U_{tot} curve in Fig. 46 is plotted by summing the point values calculated for the other three curves. Its peak value is slightly greater than that of U_R , and it leads U_R by a small phase angle, both features confirming the results of Fig. 47.

Since all the quantities are represented geometrically, it is easy to discover the equations that relate them. Figure 48 is the key diagram for all such calculations. In this diagram, the vectors represent impedances, not pds. Because the current is the same for all elements, a diagram of impedance vectors has the same proportions and angles as a diagram of pd vectors. The difference is just a matter of scale. In Fig. 48 the relative lengths of vectors differ from those in Fig. 47, which represent a circuit with different values of R , L , and C .

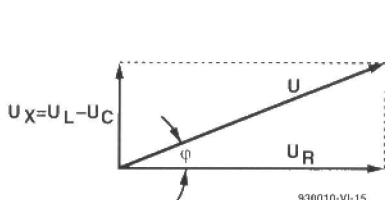


Fig. 47

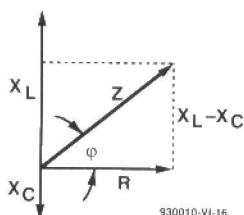


Fig. 48

Given the values of R , L , and C , the first step is to calculate X_L and X_C , using equations 33 and 34. Then we can draw a sketch of the vectors (as in Fig. 48) and find:

1. The **total impedance**, Z : apply the Pythagoras theorem to the triangle enclosed by the vectors R , $(X_L - X_C)$, and their resultant Z .

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad [\text{Eq. 35}]$$

2. The **phase angle**, ϕ .

$$\phi = \tan^{-1}[(X_L - X_C)/R] \quad [\text{Eq. 36}]$$

Note that since the calculations depend solely on the **proportions** of the rectangle, not on its absolute dimensions, the equations are independent of the magnitudes of the pds or the current. The circuit behaves the same, irrespective of the magnitude of the signal.

Example. Given $R=100\ \Omega$, $L=100\text{ mH}$, and $C=22\ \mu\text{F}$, connected in series, calculate their total impedance and the phase angle when the signal frequency is 500 Hz.

$$\omega = 2\pi f = 1000\pi = 3141.6\text{ rad s}^{-1};$$

$$R = 100\ \Omega;$$

$$X_L = 3141.6 \times 100 \times 10^{-3} = 314.16\ \Omega;$$

$$X_C = 1/(3141.6 \times 22 \times 10^{-6}) = 1/0.069115 = 14.469\ \Omega;$$

$$X_L - X_C = 299.69\ \Omega.$$

$$\therefore Z = \sqrt{(100^2 + 299.1^2)} = 315.4\ \Omega;$$

$$\phi = \tan^{-1} 299.1/100 = 1.25\text{ rad}.$$

What about j?

If you are reading this article in conjunction with an electrical or electronics textbook, you may have found that the text quotes the reactance of an inductor as $j\omega L$ and that of the capacitor as $-j/\omega C$. The symbol j is used when expressing complex numbers and this will be explained in a future issue. For the moment, take $+j$ to indicate that inductive reactance leads the current, and $-j$ to indicate that capacitive reactance lags it. At present we are using the geometrical technique in which lead and lag are clear from the sketch of the vectors.

Sinusoidal or not?

All the discussions so far have assumed that the source pd or the current varies in time according to a sine (or cosine) function. What happens if the waveform is not sinusoidal? What about

square waves or sawtooth waves, for example? As we shall see later in the series, all periodic waves can be treated as if they were the sum of a number of sine waves of various amplitudes with related frequencies. For example, the sawtooth wave of Fig. 49 is the sum of a sequence of terms which goes like this:

$$y = 3\pi - 6\sin t - 3\sin 2t - 2\sin 3t - \dots - (6/n)\sin nt$$

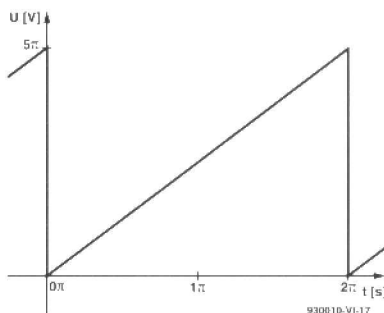


Fig. 49

The greater the number of terms summed, the more accurately the curve comes to look like a sawtooth wave. If we want to know how a circuit will behave with a sawtooth input, we analyse the waveform into its sinusoidal components, and calculate the impedances and phase angles for each component separately, as above. Then we sum the results. This may involve a lot of calculations, but it can be done, especially with the aid of a computer.

Simpler circuits

Equations 35 and 36 cater for circuits in which all three kinds of impedance are present. If one source of impedance is absent, or so small that it can be ignored, we use the same two equations putting the absent impedance equal to zero. Consider the network of Fig. 50.

Since L equals zero (assuming that the self-inductance of the connecting wires and the leads of the capacitor is so small

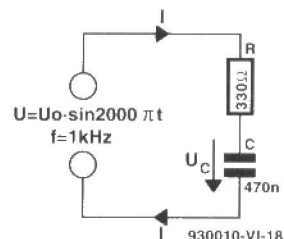


Fig. 50

that it can be ignored), the equations simplify to

$$Z = \sqrt{R^2 + X_C^2};$$

$$\phi = \tan^{-1} -X_C/R.$$

Given the values shown in Fig. 50:

$$\omega = 2000\pi = 6283.2 \text{ rad s}^{-1};$$

$$X_C = 1/(6283.2 \times 470 \times 10^{-9}) = 338.6 \Omega.$$

$$\therefore Z = \sqrt{(330^2 + 338.6^2)} = 472.8 \Omega.$$

$$\phi = \tan^{-1}(-338.6/330) = -0.80 \text{ rad}.$$

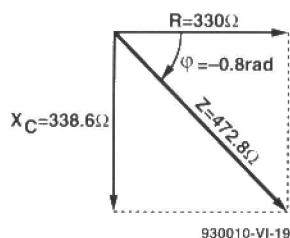


Fig. 51

Figure 51 shows the vectors. The current lags 0.80 rad (about 45°) behind the pd. Since the same current flows through all components, the impedance vectors are proportional to the pd vectors. Thus, Z is proportional to the total pd applied to the network at any instant. The pd across the capacitor is proportional to X_C , and it can be seen that this pd lags about 45° behind the pd applied to the network.

We can also calculate the peak value of the alternating signal across the capacitor. Consider Fig. 50 to be that of a potential divider circuit. The current through R and C are equal (of course, no current actually passes through C , but current flowing to one plate is matched by current flowing from the other). Thus, the pd developed across R and across C is proportional to their impedances. The pd across C is calculated as for a potential divider. Taking pds at their peak values:

$$U_C = U(X_C/Z) = U(338.6/472.8) = 0.716U_0,$$

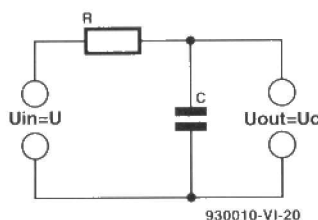


Fig. 52

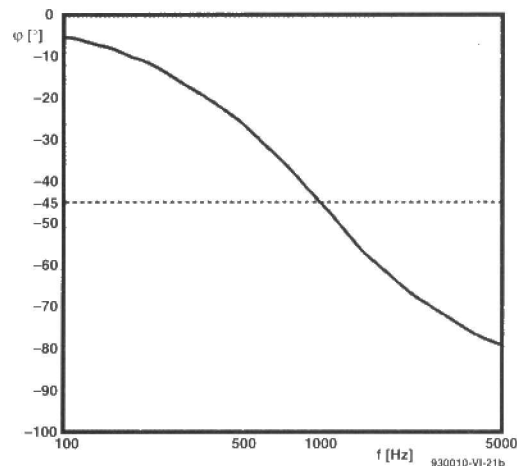
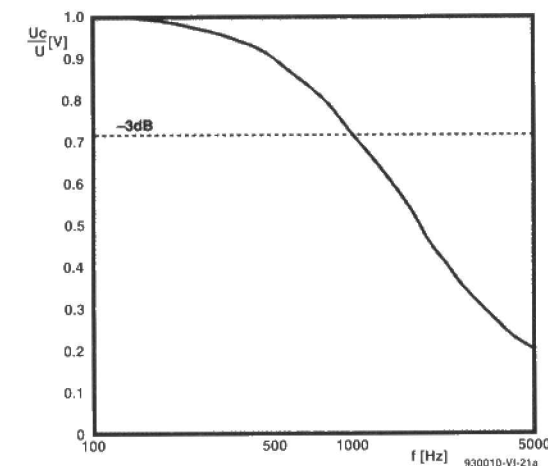


Fig. 53

or

$$U_C/U = 0.716.$$

Redraw Fig. 50 as in Fig. 52; call the total pd the **input pd**, U_{in} ; and call the pd across the capacitor the **output pd**, U_{out} . U_{out} is about 0.7 of U_{in} . The network attenuated the signal by roughly 0.3. The calculation assumes that the current drawn from the network by any load is insignificant.

Frequency dependence

The calculations for Fig. 50 can be repeated for lower and higher frequencies and graphs plotted to relate phase lag and signal attenuation to frequency. As these graphs show (Fig. 53), phase lag approaches zero at low frequency and approaches -90° at high frequencies. Remember that here we are considering the angle between U and U_C (or between Z and X_C), not the angle between U and U_R . Attenuation approaches zero at low frequencies and gradually becomes more important at high frequencies. In fact, this network is a **low-pass filter**. The frequency chosen for the worked example (1000 Hz) is very close to what is known as the -3 dB point. This is the frequency (1026 Hz for the specified component values) at which the output is 0.707 of the input (equivalent to a power attenuation of -3 dB or 50%), and the phase lag is exactly 45°. It is the frequency at which X_C is equal to R , giving us the approximately 45° triangle of Fig. 51. We can find a formula for this frequency by equating R and X_C :

$$R = X_C = 1/\omega C = 1/2\pi f C.$$

Rearranging gives:

$$f = 1/2\pi RC.$$

Example. Find the -3 dB point for a low-pass filter in which $R = 150 \Omega$ and $C = 2.2 \mu\text{F}$.

$$f = 1/(2\pi \times 150 \times 2.2 \times 10^{-6}) = 482 \text{ Hz}.$$

Other filters

The filter of Fig. 52 is converted to a high-pass filter simply by interchanging the resistor and capacitor. The vector diagram remains unchanged, but U_{out} is now the pd across the resistor. Thus, output **leads** input by 45° when R and X_C are equal and by greater or lesser amounts when the frequency is lower or higher. The -3 dB point or **cut-off frequency** is calculated as for the low-pass filter.

A high-pass filter may also be constructed by substituting an inductor for the capacitor in Fig. 52. The -3 dB point of such a filter occurs when $R = X_L$, so that at that point $f = 1/2\pi RL$.

A resistor, inductor and capacitor may be combined in a filter network such as that in Fig. 54. The output is the pd across the resistor. It is left to the reader to calculate U_{out} for a num-

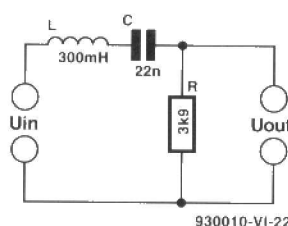


Fig. 54

ber of different frequencies in the range 100 Hz to 10 kHz, to observe the response, and say what type of filter this is. (Answer next month).

Test yourself


1. Calculate the angular velocity ω for a signal of frequency 350 Hz.
2. What is the reactance of a 33 μH inductor at (a) 50 Hz, (b) 10 MHz?
3. What is the reactance of a 120 μF capacitor at (a) 2 Hz, (b) 10 kHz?
4. Draw the vector diagram for the circuit of Fig. 47, given that $R = 680 \Omega$, $L = 0.3 \text{ H}$, $C = 1 \mu\text{F}$, and the signal frequency is 250 Hz.
5. Calculate the cut-off frequency for a low-pass filter in which $R = 12 \text{ k}\Omega$ and $C = 2.2 \mu\text{F}$.
6. Given a 10 k Ω resistor, what value capacitor is needed to form high-pass filter with its -3 dB point at 500 kHz?

Answers will be given in next month's instalment.

Answers to Test yourself (Part 5)

1. $U = L(-0.5) = -0.05 \text{ V}$. A constant back e.m.f. in the direction opposing the reduction of current.
2. $U = 0.2 \times -2e^{-2} = 7.33 \text{ mA}$.
3. $I = 10000 \times |t^2 \beta_0| = 0.09 \text{ A}$. The constant of integration C/L cancels out when we evaluate the definite integral.

GAL PROGRAMMER UPGRADE

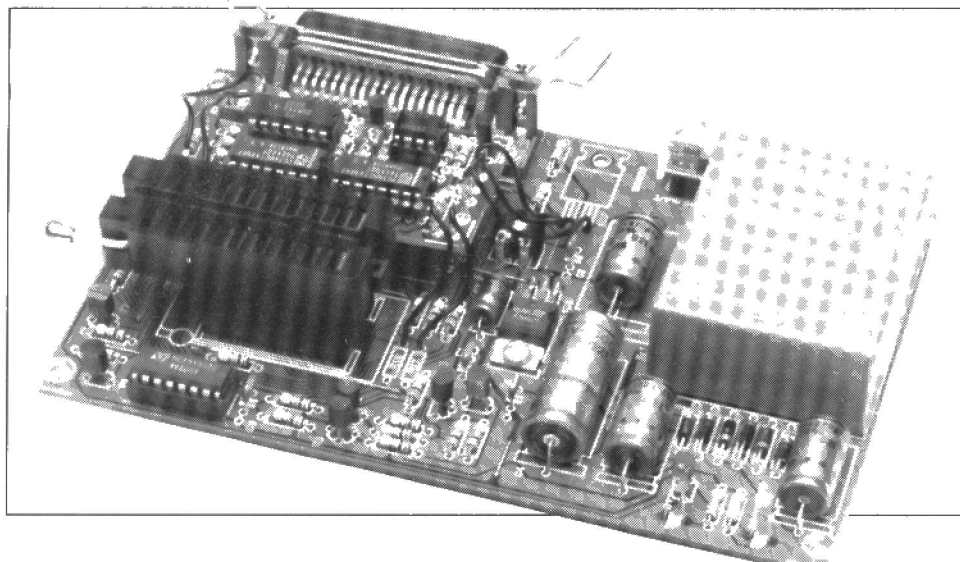

Judging from the response to an *Elektor Electronics* article last year describing a low-cost GAL programmer, it looks like many of you have recognized the power of GALs, and have started programming these interesting devices. This article answers many readers' requests for a hardware extension plus upgraded software that allows more GAL types, including the industry standard 22V10, to be programmed.

Design by M. Nosswitz

AFTER some research into the programming algorithms of a number of relatively new GALs, the designer found out that only very small modifications were required to the original GAL programmer (Ref. 1) to enable it to handle even more GAL types.

The differences in GAL programming algorithms often concern the programming voltage and the signal timing. Hence, the two main programmer upgrades are (1) a variable programming voltage source and (2) modifications to the control software to implement the (complex) timing of the programming signals, and the variable programming voltage. The software automatically adapts to the GAL type in question, hence changes to the programming algorithms are transparent to the user.

In addition to GAL types 16V8(A) and 20V8(A), the upgraded GAL programmer is also capable of handling the B versions of these GALs, the 22V10, 20RA10 and the GAL6001. Programming the 6001 takes about one minute, which, admittedly, is not fast, but still useful. As regards the programming ability of different GAL brands (a subject on which we have received many letters), please do remem-

ber that the GAL programmer can only handle GALs manufactured by **Lattice, National Semiconductor** and **SGS/Thomson**.

Hardware extension

Everyone who has successfully built the original GAL programmer should be encouraged to upgrade it with the present hardware extension. The circuit diagram shows that the extension is relatively simple. Circuits IC1 and IC2 (Type 4094s) together form an 8-bit shift register. The output of IC2 drives IC3, a digital-to-analogue converter (DAC) Type ZN426. The DAC supplies an output voltage between 0.63 V and 1.92 V, which is programmable in steps of 20 mV. The DAC output voltage is applied to IC4, a Type CA3140 BiFET opamp, which replaces the LM317 voltage regulator originally fitted in the circuit. Apart from removing the LM317 from the board, the voltage divider around it has to be changed also. Resistor R27 (270 Ω) is changed into 22 k Ω , and R26 (2.7k Ω) into 1.8k Ω . Finally, preset P1 (1 k Ω) is

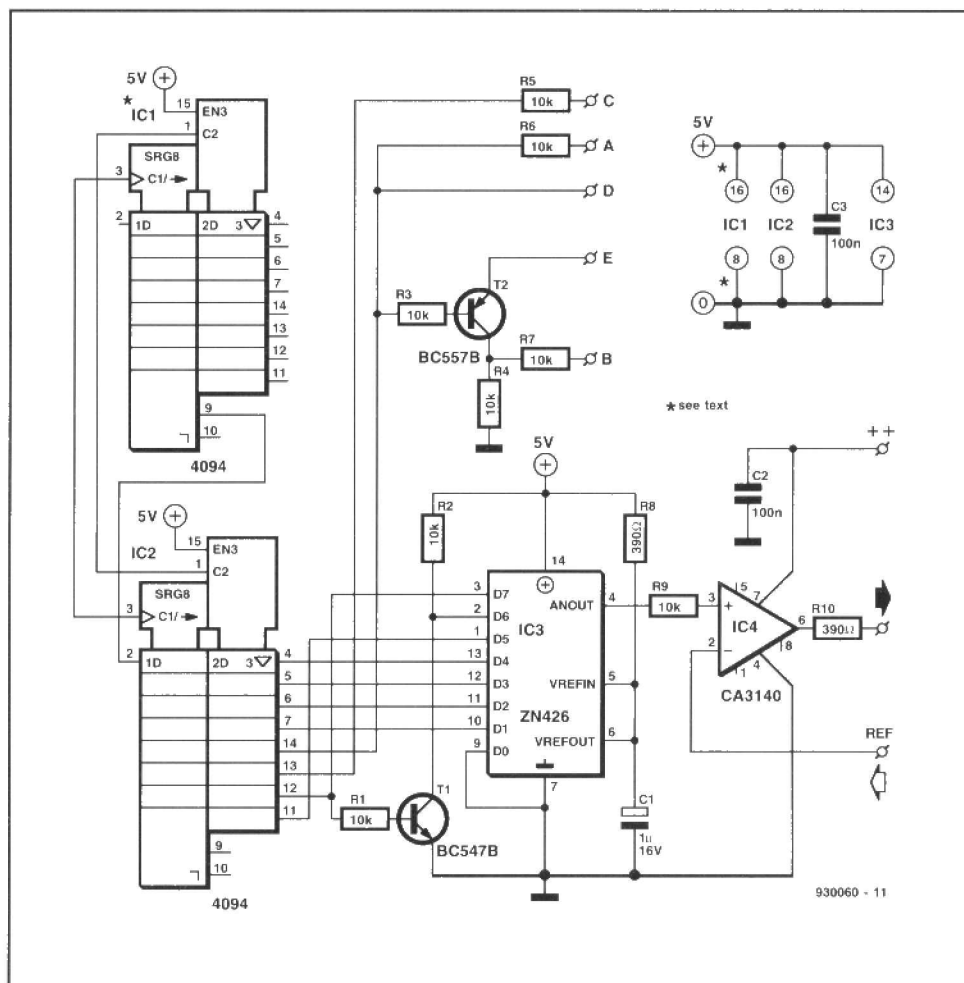


Fig. 1. Circuit diagram of the GAL programmer extension.

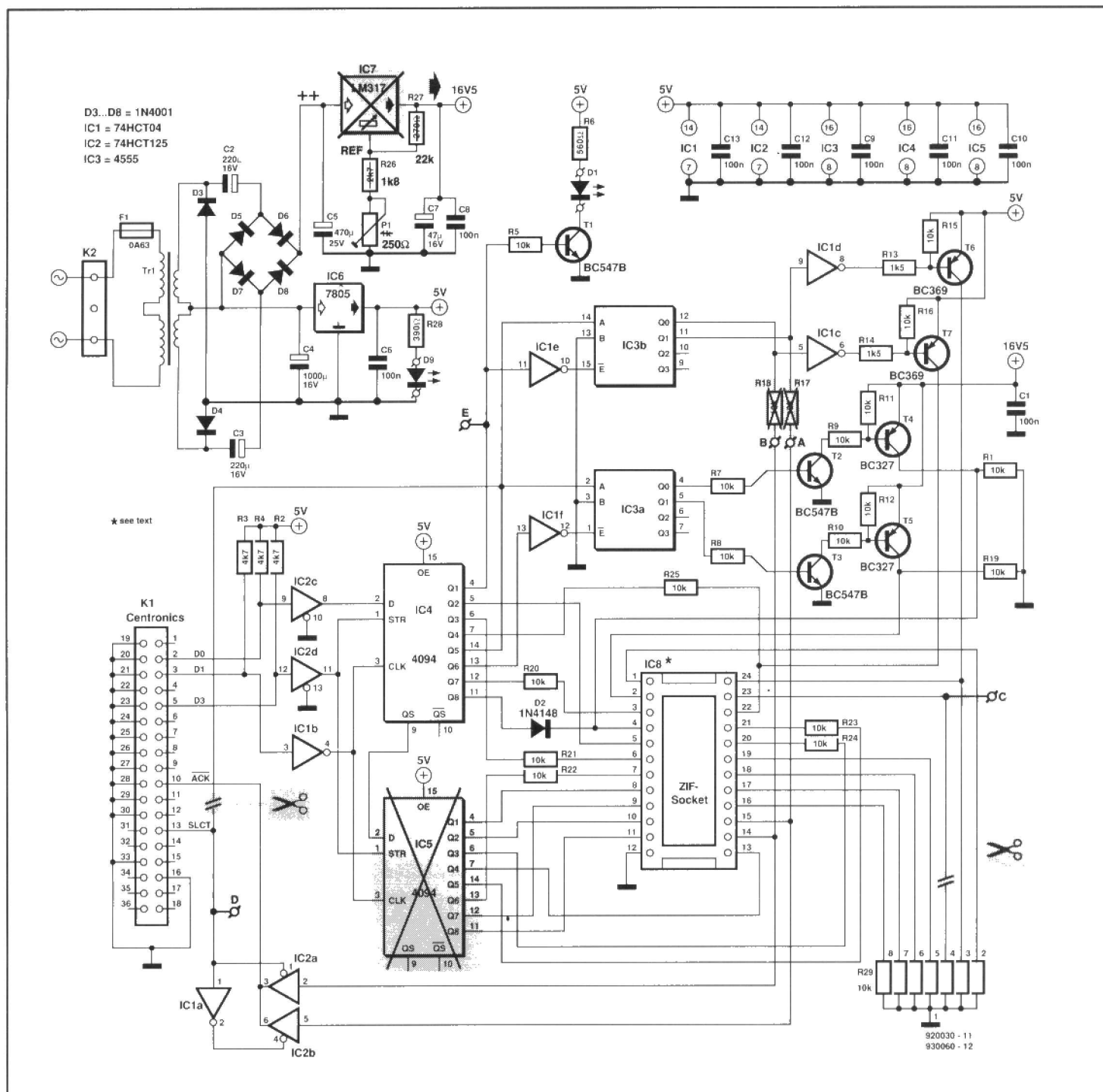


Fig. 2. This diagram shows where the original GAL programmer has to be modified to enable the extension to be integrated.

changed into 250 Ω (or 220 Ω). The opamp ensures a programming voltage range from 8 V to 23.75 V. For the sake of clarity, Fig. 2 shows the original circuit diagram with the modifications in shaded blocks.

The small board that contains the additional circuitry is fitted as an extension on to the main board. IC5 (a 4094) is removed from the main board, and replaced by the (extended) pins of the socket for IC1 on the extension board. This IC takes over the function of IC5 on the main board, and at the same time provides the connection of the supply voltage. IC2 on the extension board becomes the third element in the shift register consisting of IC4

on the main board, and IC1 and IC2 on the extension board. The third element is required to copy and latch the control word that represents the variable programming voltage. Furthermore, a number of output signals of IC2, marked A through E, are sent into the circuit. These signals are under software control, and, therefore, of little interest to the user.

Construction

As already mentioned, the extension board is plugged into the empty socket in position IC5 on the main board. The track layout and component overlay of the extension board are given in Fig. 3.

IC1 on the extension board is mounted into two IC pin rows with extra long pins, or a wire-wrap socket. The long pins are pushed through the holes in the extension board, soldered at the track side, and inserted into the socket in position IC5 on the GAL programmer main board. First, however, the extension board has to be populated. Fit eight solder pins where the wires between the extension board and the main board are to be connected. Once the extension board is complete, you can proceed with the modifications to the main board.

Remove IC7 from the main board, and solder three lengths of insulated wire in the open PCB holes. Next, re-

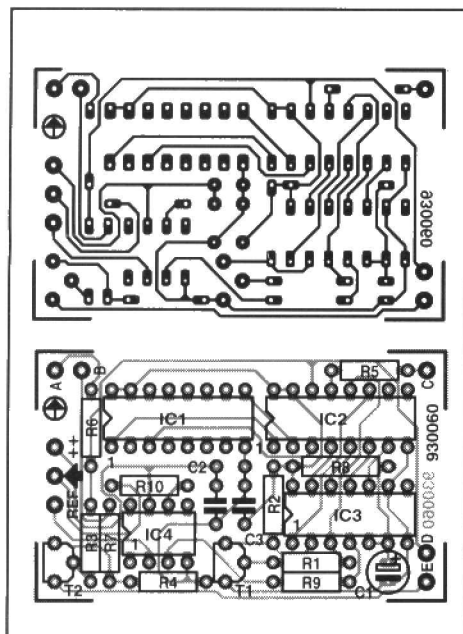


Fig. 3. Track layout (mirror image) and component overlay of the extension board.

COMPONENTS LIST

Resistors:

8	10 k Ω	R1-R7;R9
2	390 Ω	R8;R10

Capacitors:

1	1 μ F 16V tantalum	C1
2	100nF ceramic	C2;C3

Semiconductors:

1	BC547B	T1
1	BC557B	T2
2	4094	IC1;IC2
1	ZN426	IC3
1	CA3140	IC4

Miscellaneous:

- 1 DIL-16 wire-wrap socket, or two 8-way IC pin strips with long pins
- 1 Printed circuit board, order code 930060 (see page 70)
- 1 Software on disk, order code 1701 or 1881 (see page 70)

move resistors R17 and R18 from the board, and solder two wires into the holes nearest R23 and R24. The next job is a little more difficult: pin 4 of array R29 has to be disconnected from the PCB, and a short wire is inserted into the hole. If you find it difficult to actually pull the array pin out of the PCB hole, you may also cut it off (using a pair of precision pliers), and pull the remaining wire out of the PCB hole (while heating it with the solder iron, of course). Next, remove the wire link between R5 and R13, and fit a wire into the hole near R2/R5. The last wire is connected to the side of R5 that is close to the wire link you have just removed.

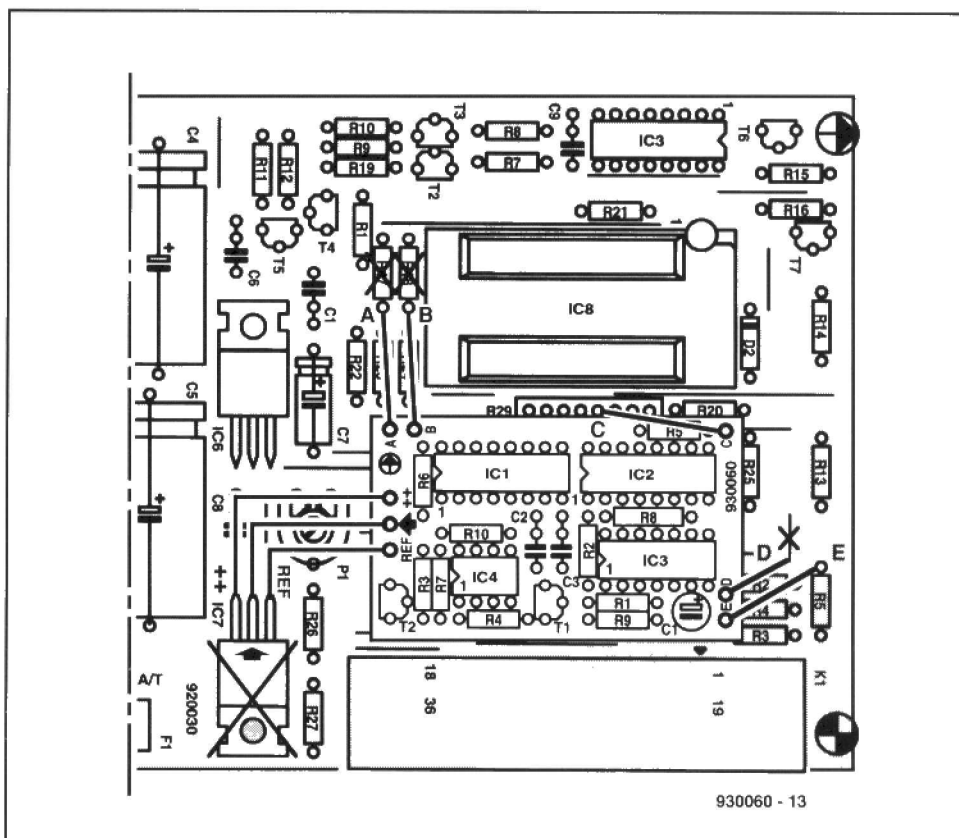


Fig. 4. This diagram tells you which components have to be changed on the main board, which wire link is removed, and where the eight wires are connected.

Replace resistor R27 by a 22-k Ω type, resistor R26 by a 1.8-k Ω type, and preset P1 by a 250- Ω (or 220- Ω) type.

After plugging the extension board on to the main board, connect the eight wires to the appropriate solder pins. The drawing in Fig. 4 shows which components must be removed, and which connections are to be made.

That concludes the modification work, and only leaves preset P1 to be adjusted, which requires the use of the new GAL programmer software (ver-

sion 6.65 or later). Once you have the program running on your PC, type a colon (:) followed by a carriage return. Next, measure the voltage at pin 2 of the ZIF socket, and adjust P1 until you measure 16.5 V.

Finally, if you foresee programming GAL6001's, it may be necessary to replace the 7805 on the main board by a low-drop regulator such as the L4941BV or the L4940V5. This prevents thermal overloading of the regulator, which would cause the supply voltage to drop below about 4.75 V. In

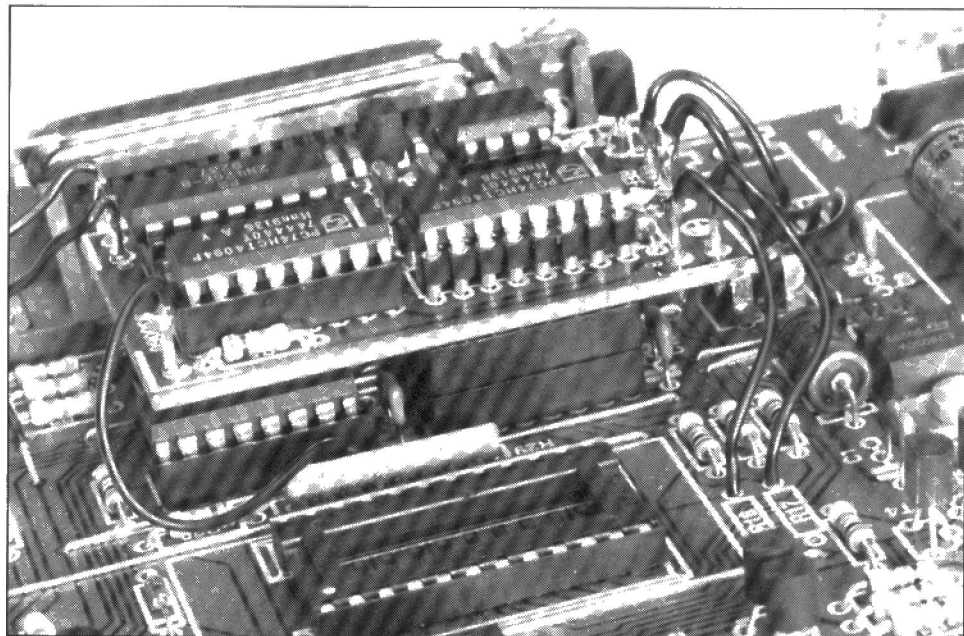


Fig. 5. Prototype of the extension board, plugged into the socket for IC5 on the main board.

some cases, this is harmful for the GAL6001.

New software

The new features of the GAL programmer call for revisions to the existing control software. From the publication date of this article, the new version (6.65) of the GAL programmer software is supplied as Readers Services item 1701, which includes National Semiconductors's Opal Jr. demonstration software. Those of you who already have Opal Jr. may order the updated GAL programmer software only as item 1881 (one disk).

Finally, the new GAL programmer software includes a modified configuration file, called GAL665.CFG. This file, and the associated comment, is shown in Fig. 6. ■

Reference:

1. GAL programmer. *Elektor Electronics* May 1992.

```
GAL665.cfg
{license number}
{user number}
$3bc Address of Centronics port for GAL data exchange
1 GAL extension board no=0 yes=1
1 Change PES (program counter) no=0 yes=1
0 Switch for general RESET (EPROM, PROM, GAL) no=0 yes=1
1 Check if GAL hardware accessible no=0 yes=1
0 Select set security bit at power-up no=0 yes=1
1 Basic GAL type selection (16V8=1, 20V8=2, 16V8A=3, 20V8A=4,
75 beep length in ms 20V8A/B=4, 22V10=5, 6001=6, 20RA10=7)
2000 error beep frequency in Hz
2000 error display time in ms
1 Background colour Text (blue)
7 Foreground colour Text (bright grey)
5 Background colour Error reports (magenta)
7 Foreground colour Error reports (bright grey)
5 Background colour Letters (magenta)
15 Foreground colour Figures (white)
7 Background colour Selection window (bright grey)
1 Foreground colour Selection window (blue)
5 Background colour Selection bar (magenta)
14 Foreground colour Selection bar (yellow)
4 Background colour Changed cells (red)
7 Foreground colour Changed cells (bright grey)
5 Top of paper margin (in lines) (printing)
8 Left margin (printing)
```


Fig. 6. GAL programmer version 6.65 configuration file listing.

GAL PROGRAMMER SOFTWARE FOR AMIGA

SOFTWARE to control the GAL programmer is now also available for the Amiga series of computers. The Amiga software consists of two programs, AmiGAL and AmiBURN, with associated (extensive) documentation files that can be printed from disk. The disk also contains an installation instruction file.

AmiGAL is a GAL logic function editor, while AmiBURN is the actual programming software. Interestingly, AmiGAL is capable of generating JEDEC files, and has a built-in Minterms (minimal terms) generator that can help you reduce complex logic equations into a form suitable for implementation with the aid of GAL cells. AmiBURN reads the files produced by AmiGAL (or any other program capable of outputting JEDEC format files), and sets up the programming conditions required for the selected GAL. Functions like making master GALs, actuating the read protection in a GAL, device copying, producing cell hard copies, and much more, are available.

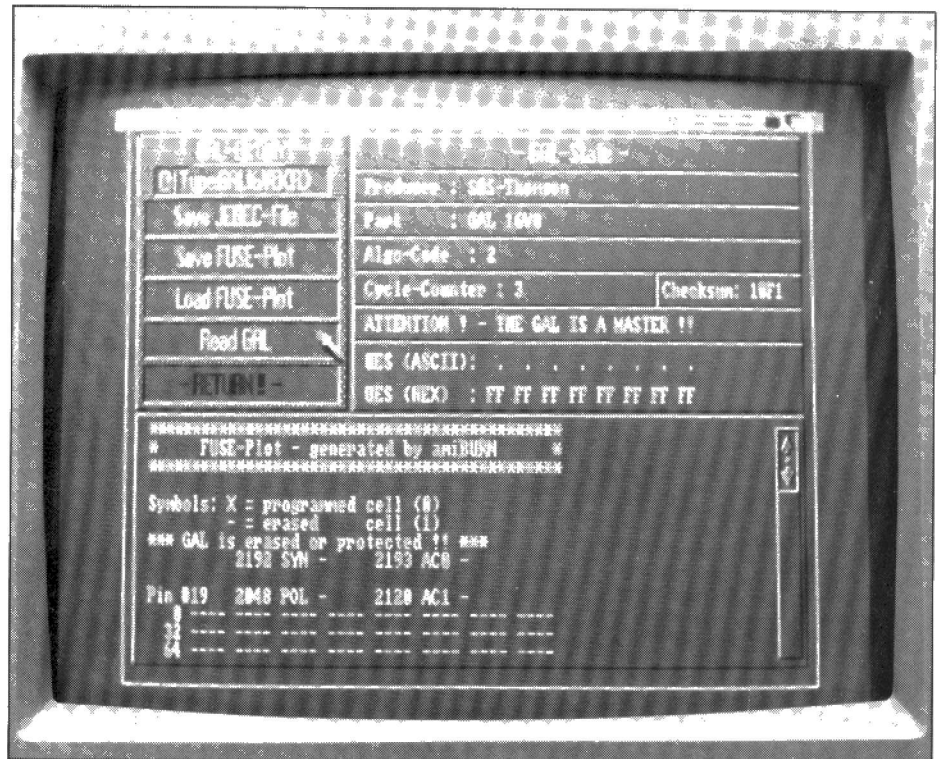AmiGAL and AmiBURN are fully menu-driven, and make full use of the Amiga's graphics power. They can be run on all types of Amiga with 512 KBytes of memory or more. Before running the software, a small hard-



ware modification is required: pins 10 and 11 of the Centronics connector must be interconnected. Fortunately, this modification still allows the programmer to be used with a PC. The

Amiga GAL programmer software may be ordered through our Readers Services as item **1841** (see page 70). ■

DIGITAL FREQUENCY READOUT FOR VHF/UHF RECEIVER

The wideband AM/FM receiver¹ described last month is not complete without a dial that tells you the transmit frequency of the station you are listening to. Such a tuning dial is described here — it takes the form of a sensitive 4-digit frequency meter with a preset option and a maximum input frequency of well over 30 MHz. Also suitable for general use in your workshop!

Design by L. Pijpers

THE circuit diagram of the frequency meter (Fig. 1) is not too complex, which is mainly by virtue of the use of an integrated counter/display driver Type ICM72117AIP1 from Harris Semiconductor. The display circuit is shown separately in Fig. 2.

The function of the ICM72117AIP1 is changed from a counter only into a frequency meter by IC5 and IC6a. The timebase consists of a crystal oscillator, X1-IC2, and a divider chain, IC2, IC3 and IC5. The input signal arrives at divider IC4 via a transistor preamplifier, T1. The digitized and scaled down input signal is applied to the counter IC input (pin 8) via gate IC6a, which functions as an electronic switch. IC6a is enabled during the gate time (measurement period) by pin 12 of IC5. Diodes D1-D16 serve to give to the counter a certain preset value — this will be reverted to below.

The time base pulse that controls the closing of IC6a must be accurately

times to ensure the correct gate time for the counter. The timing diagram of the timebase generator, IC5, is shown in Fig. 3. The numbers 0-9 at the left of the diagram represent the Q outputs of IC5. As indicated, these outputs go high successively on each pulse applied to the clock (CLK) input. The CO (carry out) output of IC5 is high when one of the outputs Q0-Q4 is high also. The CO output is low during the rest of the time, i.e., when one of the outputs Q5-Q9 is high. This means that the CO output supplies a symmetrical rectangular signal whose frequency equals $\frac{1}{10}$ th that of the input clock signal. When the CO output of IC5 is high, IC6a is enabled, so that the count pulses arriving via T1 and IC4 are fed to the count (CNT) input of IC1. The number of pulses counted during the gate time is stored in a 4-digit counter contained in IC1.

When the gate time has elapsed, the count value is fed to the 4-digit LED

display. This happens when output Q5 of IC5 goes high, whereupon IC6a supplies a 'low' to the store input of IC1.

The counter memory is cleared (reset to zero) at the start of every count cycle by a logic 'high' on Q7 of IC5, which is fed to the RESET\ input via inverter IC6b. The counter preset value defined with the aid of diodes D1-D16 is loaded into the counter when output Q8 of IC5 pulls the 'load counter' (LC) input of IC1 logic 'high'.

The input of the frequency meter is connected to prescaler output 'F' or 'G' of the Philips TV tuner in the VHF/UHF receiver. To refresh your memory, this tuner output supplies the local oscillator (LO) frequency divided by 256. The signal level is about 1 V_{pp}, which is too small to drive the digital frequency meter directly. Furthermore, the signal edges are not steep enough. These problems are resolved by the circuit around transistor T1, which acts as a preamplifier and signal shaper that turns the prescaler output signal into a neat rectangular wave with a level of 5 V_{pp}, suitable for driving the clock input of counter IC4.

IC4 divides its input signal by 2⁷, which gives a total LO frequency scale factor of 2¹⁵ (2⁸×2⁷). This means that the highest frequency at pin 13 of IC6a is about 30 kHz.

To obtain a readout in megahertz (10⁶ Hz), a timebase of 1×10⁻⁶ s is required, which means that the period of the gate signal is 2×10⁻⁶ s, or 0.5 MHz. This is achieved with the aid of dividers contained in IC2, IC3a and IC3b, which scale the 8-MHz clock signal generated by the oscillator in IC2 down by a factor 2¹⁹ (2³×2¹×2¹⁵). Note, however, that the timebase signal is divided by 10 in IC5 before it is available at the CO output. Although this results in a display reading that is ten times too high, it increases the counter accuracy, and is simple to correct visually by lighting the decimal point on





D13-D16

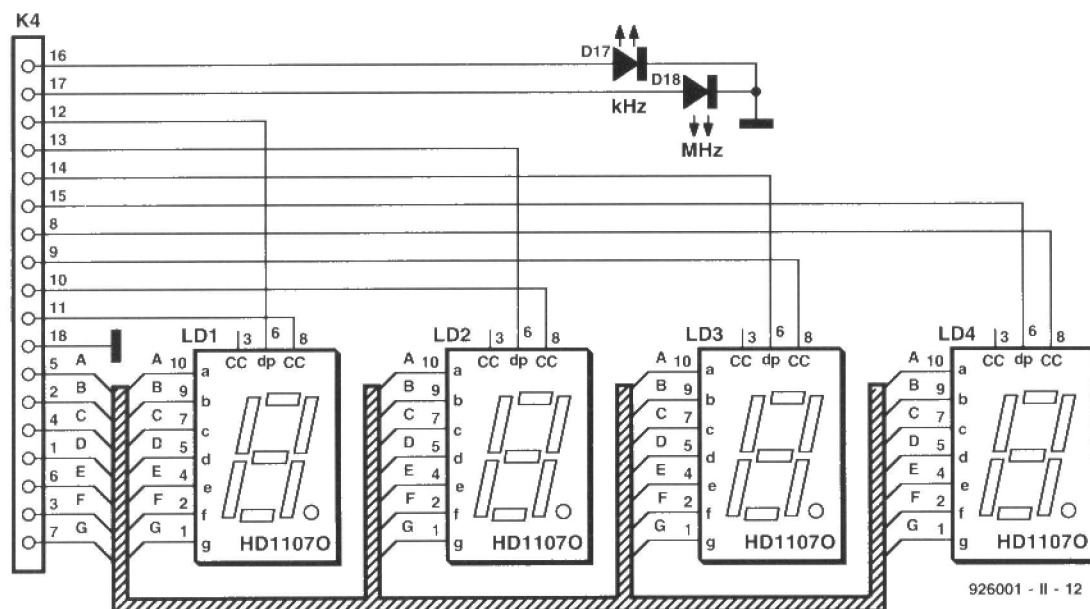


Fig. 2. Circuit diagram of the display section.

LD2	D9-D12
LD3	D5-D8
LD4 (LSD)	D1-D4

Although the four diodes associated with each digit allow a maximum preset of $2^4=16$, in practice, only the values 0 through 9 will be useful. If no jumper is fitted for a certain digit, this results in a '0', or 'no off-set'. The digit preset value is binary coded. Examples: a '3' is programmed by fitting jumpers 1 and 2, a '4' by fitting jumper 3 only, and a '7' by fitting jumpers 4, 2 and 1. Programming a

certain preset means that you have to fit the correct jumper combination for each preset. While this is straightforward with positive presets, negative presets, as required for the VHF/UHF receiver, call for a simple calculation. The instruction is simple; starting from four zeros on the display, put a '1' ahead of them (for borrowing), subtract the off-set frequency, and program the result with the aid of the diodes. So, for a LO off-set of 37.3 MHz ('373' without the decimal point), the preset value becomes

$$10000 - 373 = 9627.$$

which is programmed by fitting the preset jumpers as indicated in the circuit diagram, Fig. 1. The other jumpers are also in the positions as required for the VHF/UHF receiver: dp3 for the decimal point on LD3, the 'MHz' jumper, jumper 'A' with IC3b to set the correct timebase, and the '256' jumper with IC4 to match the $\div 256$ prescaler in the VHF/UHF tuner. The other jumpers are for tuners that have different prescaling factors.

Jumper 'C' defines the count direction (up or down). For the VHF/UHF receiver, the readout should increase with a higher LO frequency. This means that the counter must count 'UP', hence jumper 'C' must not be fitted. The 'DOWN' mode is used with receivers whose intermediate frequency is higher than the signal frequency and the local oscillator frequency.

General-purpose frequency meter

As already mentioned, the present circuit is perfect for use as a general purpose frequency meter. Since this function does not require a counter off-set, none of the diodes D1-D16 must be fitted. Also, IC3 (a dual binary counter/divider Type 74HCT4520) must be replaced with a dual decimal counter Type 74HCT4518. No modifications are required to the printed circuit board, which is suitable for both ICs. The 4518 is virtually identical to the 4520, only the signal at output Q3 is divided by 10 rather than by 16.

For frequencies from 0.01 MHz to

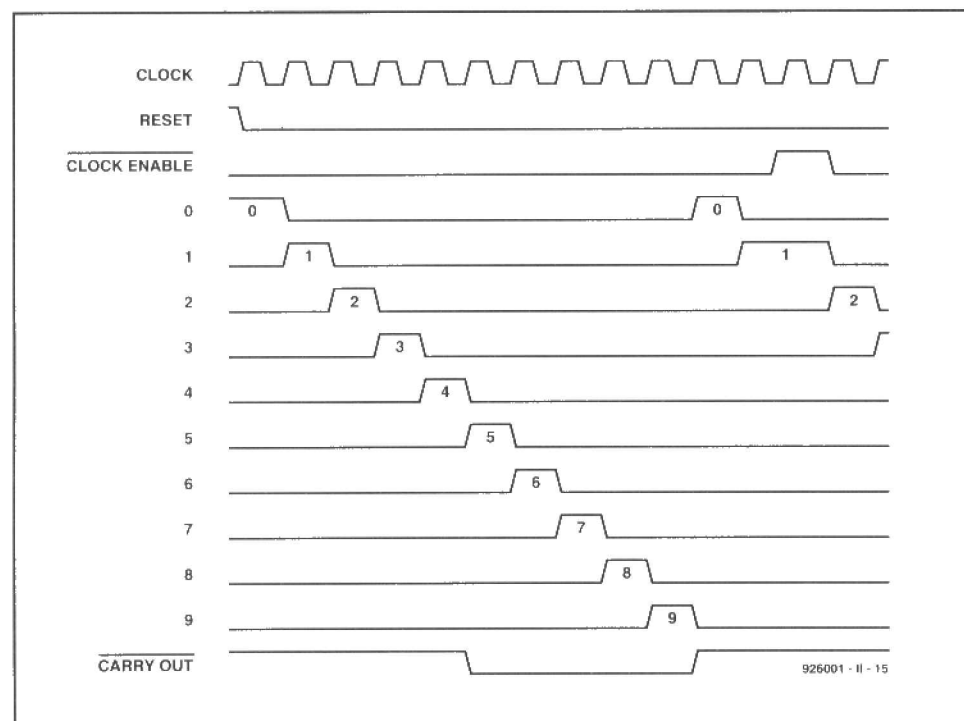


Fig. 3. Timing diagram of the counter control signals.

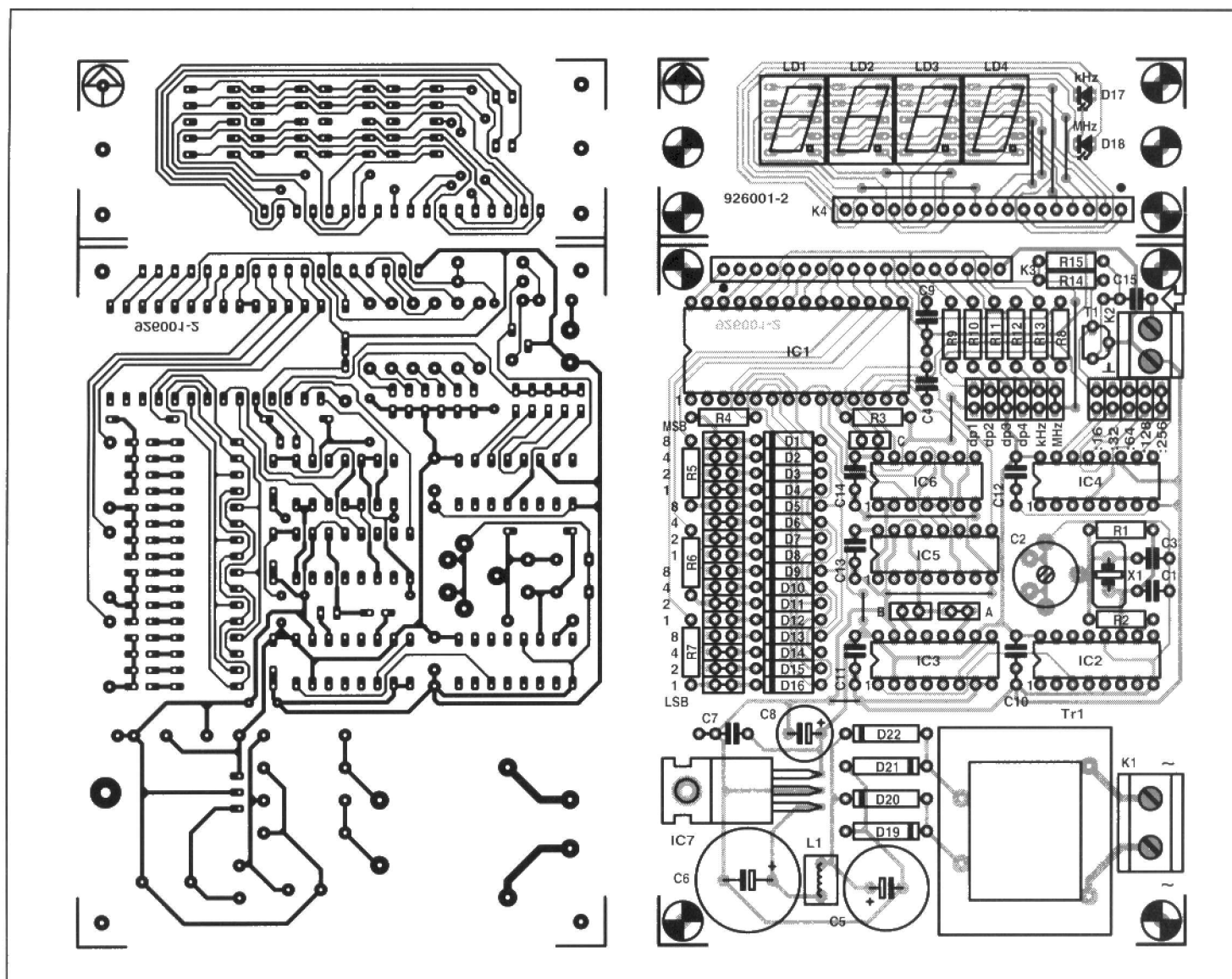


Fig. 4. Track layout (mirror image) and component mounting plan of the printed circuit board designed for the frequency meter.

COMPONENTS LIST

Resistors:

1	10M Ω	R1
1	2k Ω	R2
1	10k Ω	R3
4	12k Ω	R4-R7
4	68 Ω	R8-R11
2	220 Ω	R12;R13
1	1k Ω	R14
1	68k Ω	R15

Capacitors:

2	68pF	C1;C4
1	100pF trimmer	C2
1	10pF	C3
1	100 μ F 35V radial	C5
1	470 μ F 35V radial	C6
8	100nF	C7;C9-C15
1	100 μ F 16V radial	C8

Inductors:

1	15mH	L1
---	------	----

Semiconductors:

16	1N4148	D1-D16
2	LED, red, 3mm	D17;D18

4	1N4001	D19-D22
1	BF494	T1
1	ICM7217A-IP1*	IC1
1	74HCT4060	IC2
1	74HCT4520	IC3
1	74HCT4040	IC4
1	74HCT4017	IC5
1	74HCT132	IC6
1	7805	IC7
4	HD11070**	LD1-LD4

Miscellaneous:

1	8-MHz quartz crystal	X1
1	9V/1.5VA PCB mount mains transformer, e.g., Monacor VTR1109	Tr1
1	double-pole mains switch	S1
1	2-way PCB terminal block, pitch 7.5mm	K1
1	2-way PCB terminal block, pitch 5mm	K2
1	18-way SIL socket	K3
1	18-way SIL header, angled	K4
1	Metal enclosure 80x150x132mm,	

e.g., Telet*** LC740
1 Printed circuit board 926001-2 (see
page 70)

* Electromail (0536) 204555; fax (0536)
405555.

** ElectroValue (0784) 433603; fax:
(0784) 435216.

*** C-1 Electronics fax (+31) 45 241877.

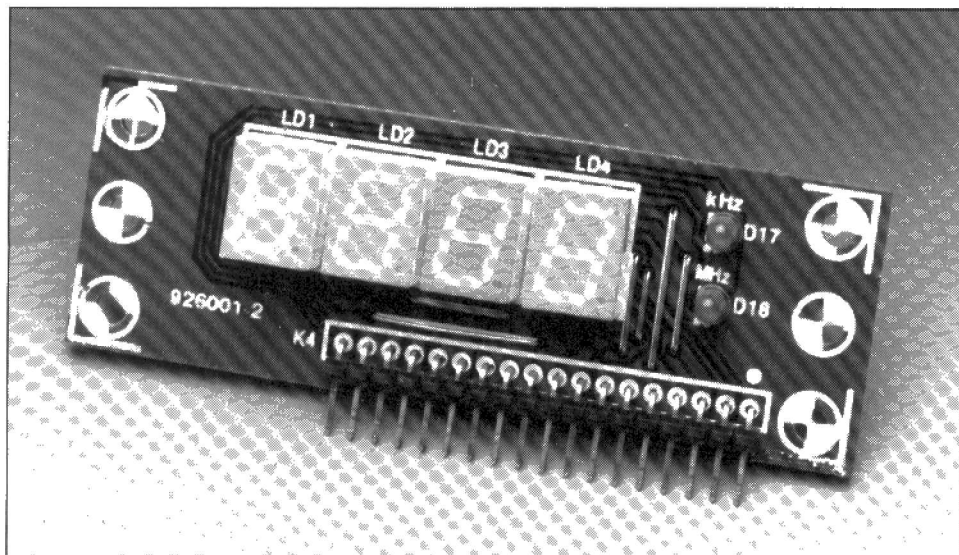


Fig. 5. Completed display board.

30 MHz, fit jumper 'A' with IC3, the ':16' jumper with IC4, the 'dp2' jumper, and the 'MHz' jumper. Depending on the maximum frequency that T1 and IC4 can handle, the highest input frequency that can be measured may be considerably higher than 30 MHz.

If you want to use the counter to measure relatively low frequencies (1 to 9999 kHz), fit jumper 'B' with IC3, and jumper ':32' with IC4. Also fit either the 'dp4' and 'kHz', or the 'dp1' and 'MHz' jumpers.

Construction

The printed circuit board designed for the frequency meter is available ready made through our Readers Services (see page 70). Those of you who have the means to make their own PCBs will find the artwork in Fig. 4. Before you start fitting parts, cut the board to separate the counter/supply section (Fig. 6) from the display section (Fig. 5).

Start the construction of the main board with the resistors, capacitors, the transformer, the crystal and the solder pins. Be sure not to damage the plastic foil trimmer (C2, near the crystal) by overheating its pins. The voltage regulator, IC7, does not need a heat-sink, and may be bolted straight on to the board. As shown by the photographs of the prototype, the display board is connected to the main board with the aid of an angled pin header and a mating socket.

The completed counter/supply board is mounted on to the bottom cover of the enclosure using PCB spacers, bolts and nuts. Great attention should be paid to the insulation of the parts, wires and terminals that are at mains potential. Also be sure to use a properly rated dual-pole mains switch.

The prototype has two 50-Ω BNC input sockets — one on the front, and

one of the rear panel. The one on the rear panel serves to connect the instrument to the VHF/UHF receiver, while the one on the front is for 'general use'. The two coax input cables are simply soldered in parallel with K2 (braids to ground; cores to C15).

If the frequency readout is used for one application only, the jumpers may be replaced by wire links. Alternatively, the jumpers may be replaced by DIP switch blocks connected to short lengths of flatcable. This allows you to switch quickly between two applications. The coax cable between the VHF/UHF receiver and the frequency meter should be kept as short as possible.

To prevent IC5 being damaged by static discharges, jumpers should not be removed or fitted with the circuit switched on. Also do not forget to discharge yourself (by touching the case) before touching any part of the circuit.

Adjusting C2 will hardly ever be required, since the error caused by a deviation from 8 MHz is negligible at a

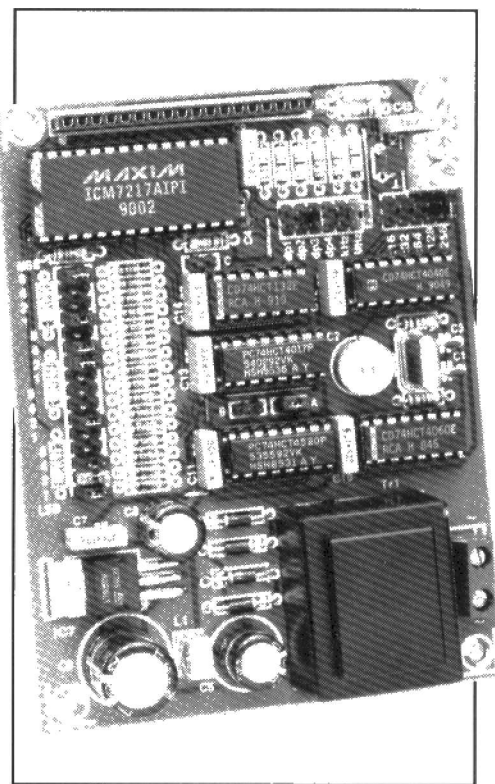


Fig. 6. Completed main board.

few kilohertz only. However, if you have the means to do so, feel free to adjust the trimmer for a clock frequency of 8 MHz exactly. Alternatively, tune the receiver to an accurately known frequency, and adjust C2 until the corresponding readout is obtained.

Reference:

1. VHF/UHF receiver, *Elektor Electronics* May 1992.

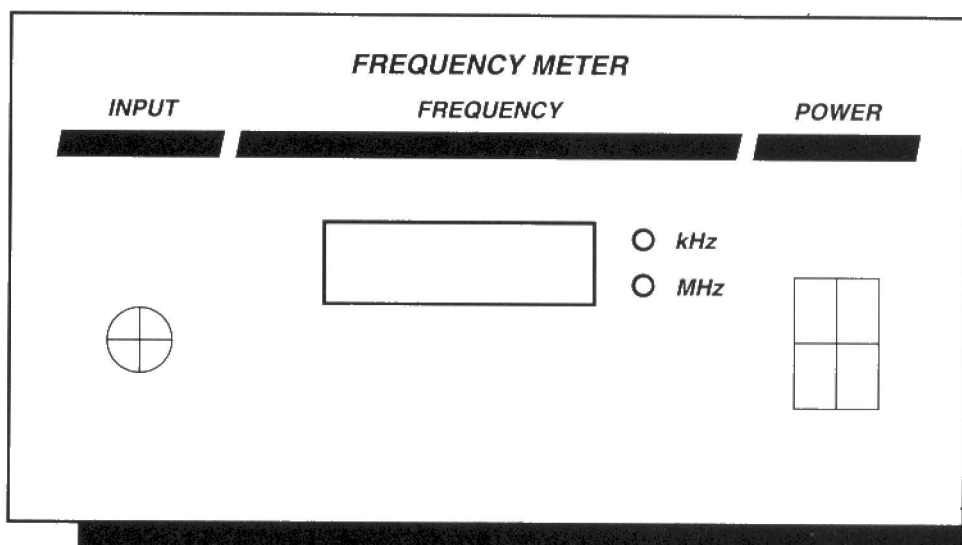


Fig. 7. Suggested front panel layout.

MAKING SENSE OF MEASUREMENTS (PART 2)

By Joseph J. Carr

In Part 1 of this two-part article we looked at the subject of measurement variation, and determined that most processes naturally vary according to the **normal distribution curve**, also known as the 'bell shaped' curve. We also discussed the ideas of precision and accuracy, and the different types of measurement (direct, indirect and null). In this final instalment we will discuss measurement errors and some of the arithmetic needed to overcome these difficulties. First, let us look at the various types of measurement error and their sources.

Theoretical error

All measurements are based on some measurement theory that predicts how a value will behave when a certain measurement procedure is applied. The measurement theory is usually based on some theoretical model of the phenomenon being measured, i.e. an intellectual construct that tells us something of how that phenomenon works. It is often the case that the theoretical model is valid only over a specified range of the phenomenon. For example, nonlinear phenomena that have a quadratic, cubic or exponential function can be treated as a straight line linear function over small, selected, sections of the range. Electronic sensor outputs often fall into this class.

Alternatively, the actual phenomenon may be terribly complex, or even chaotic, under the right conditions, so the model is therefore simplified for many practical measurements. An equation that is used as the basis for a measurement theory may be only a first order approximation of the actual situation. For example, consider the **mean arterial pressure** (MAP) that is often measured in clinical medicine and medical sciences research situations. The MAP approximation equation used by clinicians is:

$$\bar{P} = \text{Diastolic} + \frac{\text{Systolic} - \text{Diastolic}}{3} \quad [3]$$

This equation is really only an approximation (and holds true mostly for well people, not some sick people on whom it is applied) of the equation that expresses the mathematical integral of the blood pressure over a cardiac cycle. That is, the time average of the arterial pressure. The actual expression is written in the

notation of calculus, which is beyond the math abilities of many of the people who use the clinical version above:

$$\bar{P} = \frac{1}{T} \int P dt. \quad [4]$$

The approximation works well, but is subject to greater error owing to the theoretical simplification of the first equation. Incidentally, if you work your way through most of undergraduate and all of graduate school repairing medical and scientific instruments, like I did, then you will understand that it does no good to tell an irate Intensive Care Unit (ICU) nurse that the MAP reading on an instrument is correct when it differs from her calculated value. The actual measured MAP is based on the integral calculus equation (an electronic Miller integrator circuit is used), while her calculated value is based on the simplification. Because some patients lack a considerable part of the time dependent pressure curve (which is sometimes why they are in the hospital), the actual MAP will be lower than the approximation value. Sometimes heat, fire and smoke flow from the tender, loving care hands of ICU nurses!

Static errors

Static errors include a number of different sub-classes that are all related in that they are always present even in unchanging systems (thus are not dynamic errors). These errors are not functions of the time or frequency variation.

Reading errors. These errors result from misreading the display output of the sensor system. An analog meter uses a pointer to indicate the measured value. If the pointer is read at an angle other than straight on, a **parallax reading error** occurs. Another reading error is the **interpolation error**, i.e., an error made in guessing the correct value between two calibrated marks on the meter scale (Fig. 8). Still another reading error occurs if the pointer on a meter scale is too broad, and covers several marks at once.

A related error seen in digital readouts is the **last digit bobble** error. On digital displays, it is often the case that the least significant digit on the display will flip back and forth between two val-

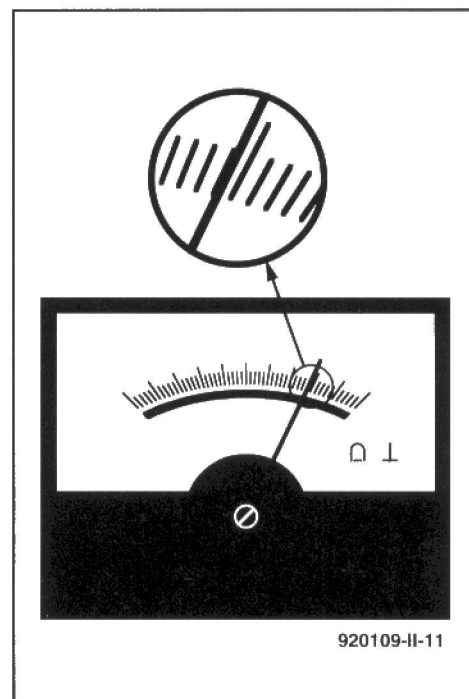


Fig. 8. Analogue meter pointers can suffer both parallax and interpolation of reading errors.

ues. For example, a digital voltmeter might read '12.24' and '12.25' alternately, depending on when you looked at it, despite the fact that absolutely no change occurred in the voltage being measured. This phenomenon occurs when the actual voltage is between the two indicated voltages. Error and uncertainty in the system will make a voltage close to 12.245 V bobble back and forth between the two permissible output states (12.24 and 12.25) on the meter. An example where 'bobble' is of significant concern is the case where some action is taken when a value changes above or below a certain amount — and the digital display bobbles above and below the critical threshold.

Environmental errors. All sensors and instruments operate in an environment, which sometimes affect the output states. Factors such as temperature (perhaps the most common error producing agent), pressure, electromagnetic fields, and radiation must be considered in some electronic sensor systems.

Characteristic errors. These static errors are still left after reading errors and environmental errors are accounted.

When the environment is well within the allowable limits and is unchanging, when there is no reading error, there will be a residual error remaining that is a function of the measurement instrument or process itself. Errors found under this category include zero offset error, gain error, processing error, linearity error, hysteresis error, repeatability error, resolution error and so forth.

Also included in the characteristic error are any design or manufacturing deficiencies that lead to error. Not all of the 'ticks' on the ruler are truly 1.0000 inch apart at all points along the ruler. While it is hoped that the errors are random, so that the overall error is small, there is always the possibility of a distinct bias or error trend in any measurement device.

For digital systems one must add to the resolution error a **quantization error** that emerges from the fact that the output data can only take on certain discrete values. For example, an 8-bit analogue-to-digital converter allows 256 different states, so a 0 to 10 V range is broken into 256 discrete values in 39.06 mV steps. A potential that is between two of these steps is assigned to one or the other according to the rounding protocol used in the measurement process. An example is the weight sensor that outputs 8.540 V, on a 10-V scale, to represent a certain weight. The actual 8-bit digitized value may represent 8.502, 8.541, or 8.580 V because of the ± 0.039 V quantization error.

Dynamic errors

Dynamic errors arise when the measurand is changing or in motion during the measurement process. Examples of dynamic errors include the inertia of mechanical indicating devices (such as analog meters) when measuring rapidly changing parameters. There are a number of limitations in electronic instrumentation that fall into this category, as you will find out by consulting any competent book on the subject.

Instrument insertion error

A fundamental rule of making engineering and scientific measurements is that **the measurement process should not significantly alter the phenomenon being measured**. Otherwise, the measurand is actually the altered situation, not the original situation that is of true interest. Examples of this error are found in many places. One such is the fact that pressure sensors tend to add volume to the system being measured, so slightly reduce the pressure indicated below the actual pressure. Similarly, a flow meter might add length, a different pipe diameter, or turbulence to a system being measured. A voltmeter with a low

impedance of its own could alter resistance ratios in an electrical circuit and produce a false reading (Fig. 9). This problem is seen when using cheap analogue volt-ohm-milliammeters (VOMs), that have a low sensitivity hence a low impedance (R_m in Fig. 9), to measure a voltage in a circuit. The meter resistance R_m is effectively shunted across the circuit resistance across which the voltage appears.

Instrument insertion errors can usually be minimized by good instrument design and good practices. No measurement device has zero effect on the system being measured, but one can reduce the error to a very small value by appropriate selection of methods and devices.

Dealing with measurement errors

Measurement error can be minimized through several methods, some of which are lumped together under the rubric 'procedure' and others under the legend 'statistics'.

Under 'procedure' one can find methods that will reduce, or even minimize, error contributions to the final result. For example, in an electrical circuit, use a voltmeter that has an extremely high input impedance compared with circuit resistances. The idea is to use an instrument (whether a voltmeter, a pressure meter or whatever) that least disturbs the thing being measured.

A way to reduce total error is to use several different instruments to measure the same parameter. In Fig. 10 we see an example where the current flow in a circuit is being measured by three different ammeters: M1, M2 and M3. Each of these instruments will produce a result that contains an error term de-correlated

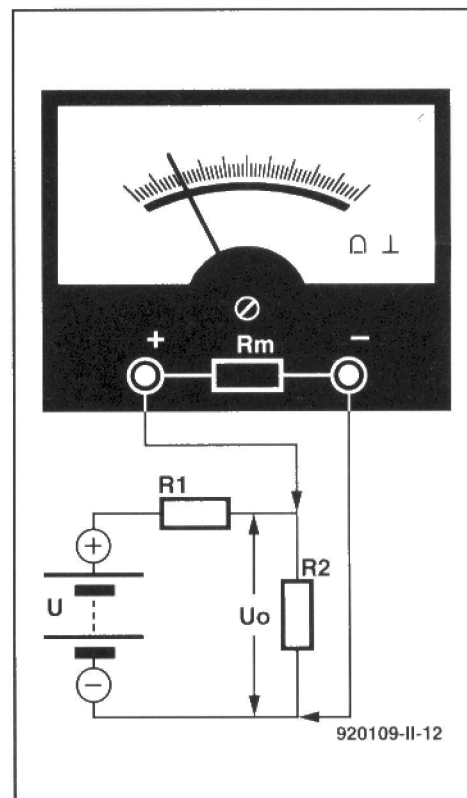


Fig. 9. If a low-impedance VOM is used to measure voltages in a circuit, it can load the circuit and produce an erroneous reading. This is an example of an instrument insertion error.

from the error of the others and not biased (unless, by selecting three identical model meters we inherit the characteristic error of that type of instrument). We can estimate the correct value of the current flow rate by taking the average of the three:

$$M_0 = \frac{M_1 + M_2 + M_3}{3} \quad [5]$$

One must be careful to either randomize

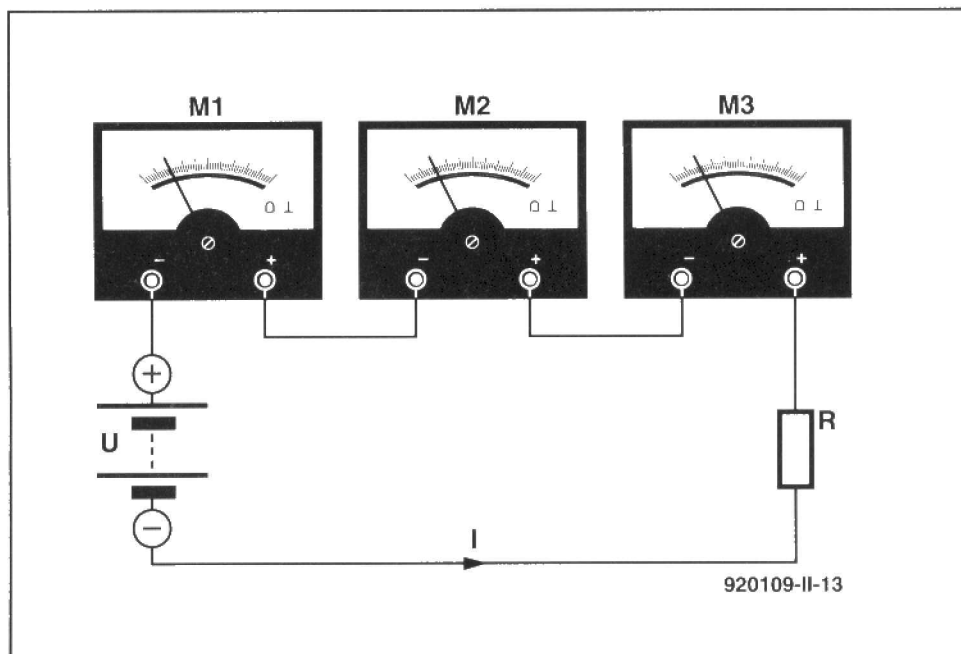


Fig. 10. Use of multiple instruments, and then averaging the results, can reduce error.

the system in cases where the sensor or instruments used tend to have large error terms biased in one direction, or calibrate the average error so that it may be subtracted from of the final result.

Error contributions analysis

An **error analysis** should be performed in order to identify and quantify all contributing sources of error in the system. A determination is then made regarding the randomness of those errors, and a **worst case analysis** is made. Under the worst case, one assumes that all of the component errors are biased in a single direction and are maximized. We then attempt to determine the consequences (to our purpose for making the measurement) if these errors line up in that manner, even if such an alignment is improbable. The worst case analysis should be done on both the positive and negative side of the nominal value. An **error budget** is then created to allocate an allowable error to each individual component of the measurement system in order to ensure that the overall error is not too high for the intended use of the system.

If errors are independent of each other, and are random rather than biased, and if they are of the same order of magnitude, then one can find the **root of the sum of the squares** (RSS) value of the errors, and use it as a composite error term in planning a measurement system. The RSS error is:

$$\epsilon_{\text{rms}} = \sqrt{\sum \epsilon_i^2} \quad [6]$$

The RSS error term is a reasonable estimate or approximation of the combined effects of the individual error components.

A collection of repetitive measurements of a phenomenon can be considered a sampled population, and treated as such. If we take N measurements (M_1 through M_n) of the same parameter, and then average them we get:

$$\bar{M} = \frac{M_1 + M_2 + M_3 + \dots + M_n}{N} \quad [7]$$

The average value obtained in Eq. [7] is the **mean arithmetic average**. This value is usually reported as the correct value for the measurement, but when taken alone does not address the issue of error. For this purpose we add a fudge factor by quoting the **standard error** of the mean, or

$$\sigma_{\bar{m}} = \frac{\sigma_m}{\sqrt{N}} \quad [8]$$

which is reported in the result as:

$$M = \bar{M} \pm \sigma_{\bar{m}} \quad [9]$$

Any measurement contains error, and this procedure allows us to estimate that error, and thereby understand the limitations of that particular measurement.

Operational definitions in measurement

Some measurement procedures suggest themselves immediately from the nature of the phenomenon being measured. In other cases, however, there is a degree of ambiguity in the process, and it must be overcome. Sometimes the ambiguity results from the fact that there are many different ways to define the phenomenon, or perhaps no way is established. In cases such as these, one might wish to resort to an **operational definition**, i.e., a procedure that will produce consistent results from measurement to measurement, or when measurements are taken by different experimenters.

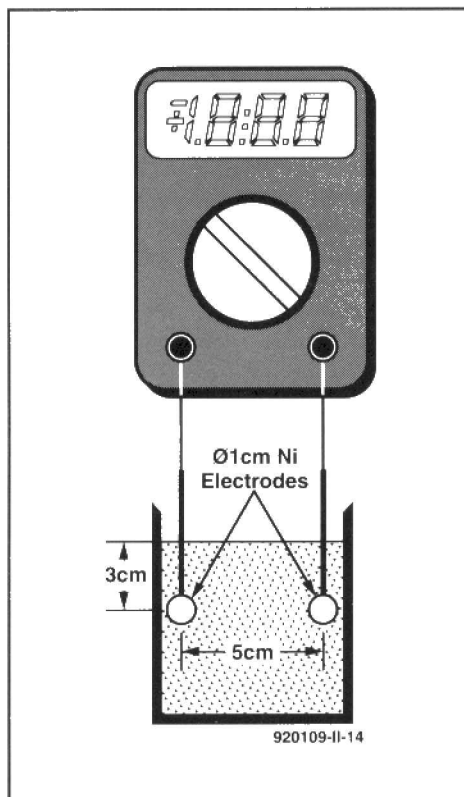


Fig. 11. Example of an 'operational definition'.

An operational definition, therefore, is a procedure that must be followed, and specifies as many factors as are needed to control the measurement so that changes can be properly attributed only to the unknown variable. The need for operational definitions (as opposed to absolute) definitions arises from the fact that things are only rarely so neat and clean as to suggest their own natural definition; ambiguity reigns. By its very definition, the operational definition does

not ask 'true' or 'false' questions, but rather it asks 'what happens under given sets of assumptions or conditions'. What an operational definition can do for you, however, is to standardize a measurement in clear and precise way so that it remains consistent across numerous trials. Operational definitions are used extensively in science and technology. When widely accepted, or promulgated by a recognized authority, they are called **standards**.

An operational definition should embrace what is measurable quantitatively, or at least in non-subjective terms. For example, in measuring the 'saltiness' of saline solution (salt water), one might taste it and render a subjective judgement such as 'weak' or 'strong'. Alternatively, one can establish an operational definition that calls for you to measure the electrical resistance of the saline under certain specified conditions:

1. immerse two 1-cm diameter circular nickel electrodes, spaced 5 cm apart and facing each other, to a depth of 3 cm into a 500-ml beaker of the test solution.
2. Bring the solution to a temperature of 4 °C.
3. Measure the electrical resistance (R) between the electrodes using a Snotz Model 1120 digital ohmmeter.
4. Find the conductance (G) by taking the reciprocal of resistance ($G = 1/R$).

You can probably come up with a better definition of the conductance of saline solution that works for some peculiar situation. Keep in mind that only rarely does a preferred definition suggest itself naturally.

The use of operational definitions results in both strengths and weaknesses. One weakness is that the definition might not be honed fine enough for the purpose at hand. Sociologists and psychologists often face this problem because of difficulties in dealing with non-linearities such as human emotions. But such problems also point to a strength. We must recognize that scientific truth is always tentative, so we must deal with uncertainties in experimentation. Sometimes, the band of uncertainty around a point of truth can be reduced by using several operational definitions in different tests of the same phenomenon. By taking different looks from different angles, we may get a more refined idea of what is actually happening.

When an operational definition becomes widely accepted, and is used throughout an industry, it may become part of a formal **standard** or test procedure. You may, for example, see a procedure listed as 'performed in accordance with NIST XXXX.XXX'¹ or 'ANSI Standard XXX'.² These notations mean that whoever made the measurement fol-

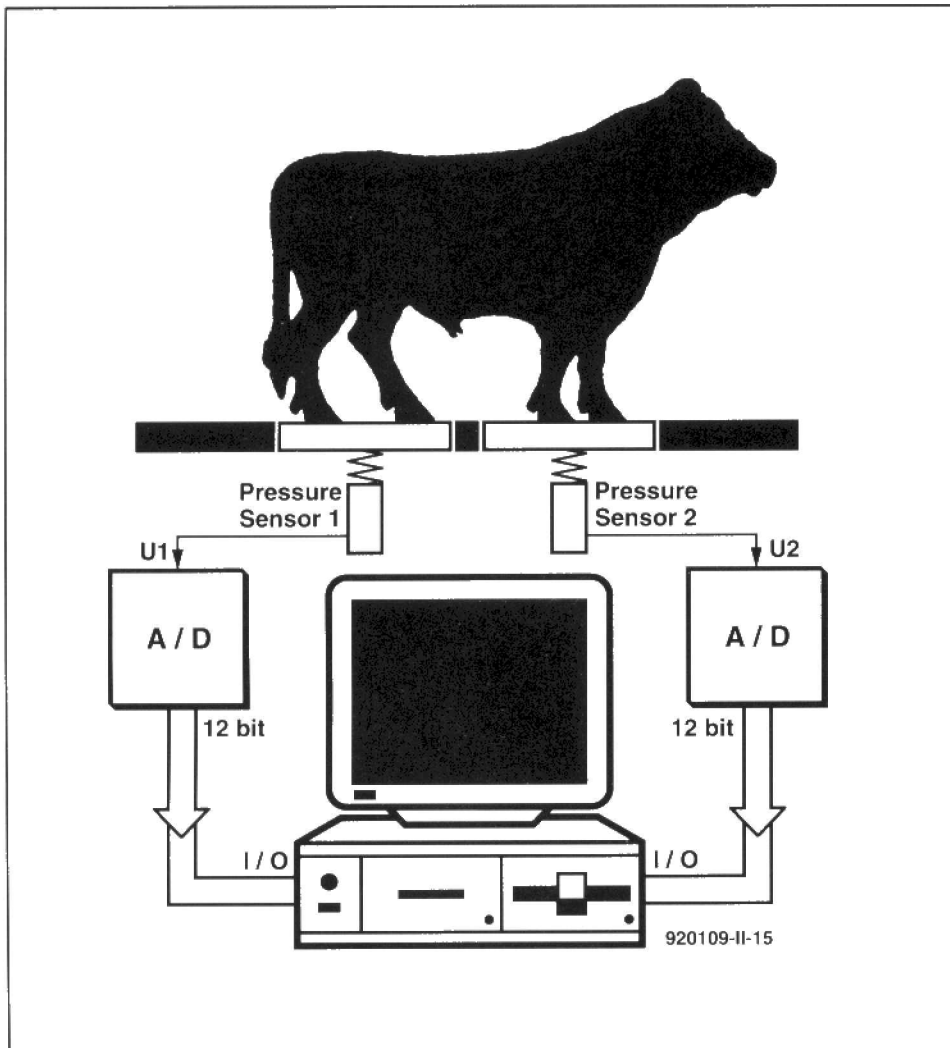


Fig. 12. Instrument for weighing a bull.

lowed one or another of a published standard.

Weighing a cow

Now let us get back to the issue of weighing a cow on an electronic scale. The main problem is that the cow will not stand still long enough to make a static measurement. As a result, it is necessary to use statistical methods to weigh the animal. Figure 12 shows the cattle scale seen by my electronically literate political aide. The animal stands on two platforms, one for the front legs and another for the rear legs, that are each connected to an electronic pressure sensor. The voltage outputs of each sensor (U_1 and U_2) are each approximately equal to half the weight of the animal. Therefore, the sum of U_1 and U_2 is proportional to the total weight of the animal.

These voltages (U_1 and U_2) are converted to binary numbers by the analogue-to-digital (A-D) converters, and input to a desktop computer. Because very fast A-D converters are now available, it is possible to take several thousand samples of the two half weights in the ten to twenty seconds the animal is held on the scale. The average of each is taken, along with the error factor, and

765 °F after 10 minutes. A test technician inserted an electronic thermometer and a timer to take the temperature measurement after exactly ten minutes; the oven was allowed to cool back to room temperature between trials. She took 20 measurements and found the mean to be 770 °F with a standard deviation of 26.2. Did this oven pass the test? The situation is shown in Fig. 13 — the answer seems to be: yes. Why? Because the error term represented by the standard error of the mean (shown as $\pm s_m$ in Fig. 13) encompasses the desired value of 765 despite the dispersion of the data. We can only claim that the test is failed if the desired value is outside these limits. ■

Notes:

1. NIST is the National Institute for Standards and Technology, formerly called National Bureau of Standards.
2. ANSI is the American National Standards Institute.

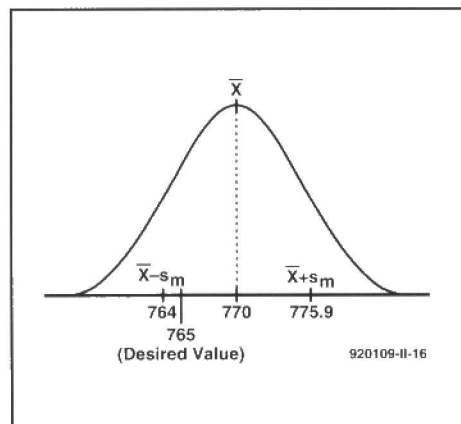


Fig. 13. Plot of oven test data showing error limits.

they are then added together. As long as the error factor is less than the desired resolution, the scale's reading is accepted.

Now let us take a look at another situation that involves ambiguous measurements.

Did it pass the test?

An adhesives curing oven is supposed to have an equilibrium temperature of

'SMARTWATCH' REAL-TIME CLOCK FOR 80C32 COMPUTER

A 'Smartwatch' real-time clock is described that provides a time/date indication and a stopwatch function on the *Elektor Electronics* 80C32 single-board computer^{1,2}.

Design by W. Hackländer

DALLAS Semiconductor's 'Smart-Watch' Type DS1216C is a real-time clock IC which is, unusually, housed in a 28-way IC socket. The device is pin compatible with 64-kBit and 256-kBit static CMOS RAMs, and is simply inserted between the RAM on the 80C32 computer and its socket. The 'intelligent socket' between the RAM and the processor contains a clock circuit, a Lithium battery and a power supply controller for the CMOS RAM. The Lithium battery contained in the DS1216C doubles as a RAM backup for the computer, which means that the existing 3.6-V battery and battery holder board may be removed from the board.

Smartwatch intelligent socket

With the exception of pins 20 and 28, the 'intelligent socket' (Fig. 1) connects all RAM pins directly to the corre-

sponding PCB holes. The DS1216C may be used with all static RAMs organized as $8\text{ k} \times 8$ or $32\text{ k} \times 8$. Its principal feature, the real-time clock, counts hundredths of a second, seconds, minutes, hours, days, months and years, and automatically updates the date information. The clock error is less than ± 1 minute per month, and the clock takes leap years into account. Both 12-hour (AM/PM) and 24-hour time indications are possible.

Communication with the clock starts with pattern recognition. This is achieved by sending 64 successive write cycles to port DQ0. The 64-bit datastream is compared with a fixed pattern (Fig. 2), which arranges the bits into eight bytes (groups of 8 bits). This results in a byte pattern as shown to the right in Fig. 2. The probability of an identical datastream intended for the RAM is smaller than 1 in 1019 instances. The 64-bit pattern is followed by 64 further read or write cycles to set

or read the clock. RAM access is disabled during these operations. Any write instruction to the RAM that activates CE\ (chip enable) and OE\ (output enable) starts the pattern recognition operation by setting up a pointer to the first of the 64 bits in the comparison register. Obviously, the next 64 write operations that enable the CPU to access the clock end up in the RAM also. Consequently, one address in the RAM should be reserved for use as a kind of scratch pad, and the clock should be accessed via this address.

The pattern recognition that selects the clock is a sequential (bit-by-bit) operation. The DS1216C compares the first write instruction with bit 0 of the 64-bit pattern register. If the bits match, the pointer is increased to bit 1, and waits for the next instruction. This continues until all 64 bits have been compared, or the first mismatch occurs, when the pointer is 'frozen', and the clock ignores all further write instructions. If a read operation occurs during the pattern recognition, the comparison is terminated, and the pointer reset.

The clock is accessible when a sequence of 64 bits received via DQ0 matches the clock selection pattern, whereupon the next 64 bits can be read from, or written to, DQ0. This is

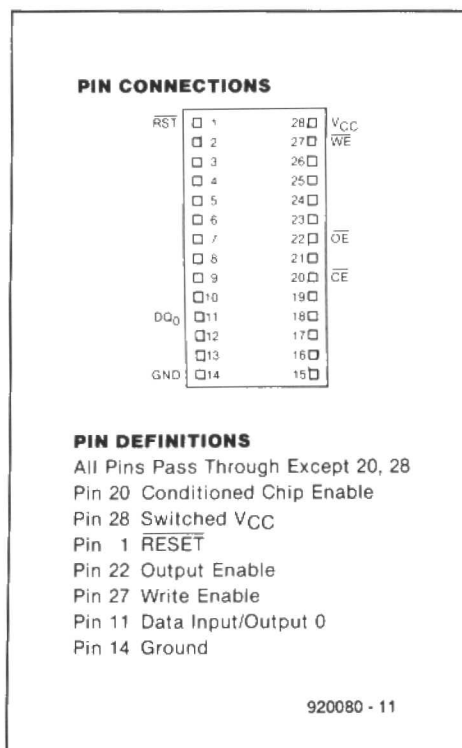


Fig. 1. DS1216C Smartwatch pin-out (courtesy Dallas Semiconductor).

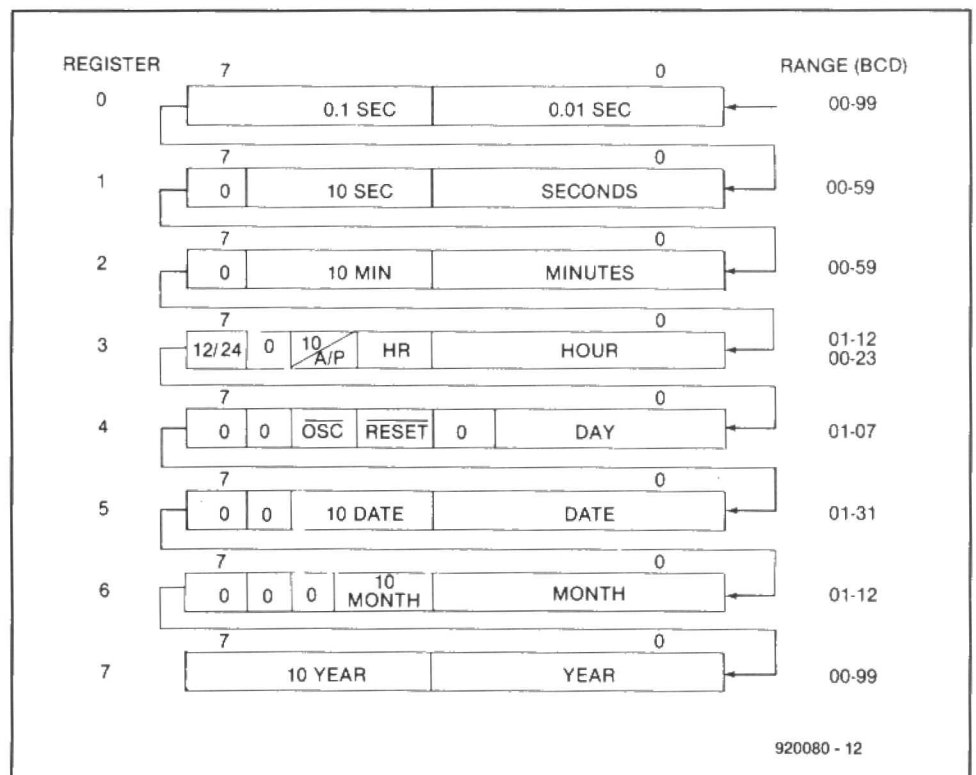


Fig. 2. Smartwatch register definition.

DS1216C SMARTWATCH software for Elektor Electronics 80C32 computer

1. Smartwatch address assignment

CLKADDR EQU 03FFFH ;Smartwatch dummy address

2. Eight registers assigned in internal RAM.

Registers for intermediate storage of data exchanged between CPU and Smartwatch. 80C32 board RAM definitions including eight RTC registers.

; RAM definitions

```

;
; ORG 030H
;
COMMAND: DS 1 ;for MON call, MUST be address 030H!
CNT1: DS 1
HEXLEN: DS 1
HEXSUM: DS 2
;
dBYTES EQU 5 ;must be 5, loop unrolling used;
;
dREG1: DS dBYTES
dACCU: DS dBYTES
;
PSWSAV: DS 1 ;used for snapshot and MON
ACCSAV: DS 1
DPLSAV: DS 1
;
; arithmetic storage
;
top EQU dREG1 ;overlay 2 bytes
next EQU dREG1+2 ;overlay 2 bytes
;
FAC1 EQU top ;overlay factors for 16*16 bit
FAC2 EQU next ;overlay
DIVI EQU FAC2 ;overlay divisor for 32/16 bit division
QUOT EQU FAC1 ;overlay quotient for 32/16 bit divis.
PROD EQU dACCU ;overlay 5 bytes (4+ ext.) for division
DIVCNT: DS 1
;
; date and clock storage
;
CLOCK: DS 4 ;Smartwatch, Time
DAY_NR: DS 1 ;Smartwatch, Day of Week (+OSC/RES-Bits)
DATE: DS 3 ;Smartwatch, Date
;
Rtop EQU $
;

```

3. Command codes assignment

Allow the courseware RAM to access Smartwatch via courseware EPROM. All relevant EMON51 codes are listed; additions are marked.

; function codes for MON calls

```

;
ccCHR EQU 001H
ccSTXT EQU 002H
ccBYTE EQU 003H
ccHEX16 EQU 004H
ccdR016 EQU 005H
ccdR032 EQU 006H
cchR016 EQU 007H
cchR032 EQU 008H
;
ccGETC EQU 010H
ccTSTC EQU 011H
ccGET16 EQU 012H
ccGET10 EQU 013H
ccGETU EQU 014H
;
ccSNAP EQU 020H
ccLTIME EQU 021H
ccSTIME EQU 022H
;
ccCLKREQ EQU 030H **** New
ccCLKRUN EQU 031H **** New
ccCLKSTP EQU 032H **** New
ccCLK_WR EQU 033H **** New
ccCLK_RD EQU 034H **** New
;
ccLINK EQU 040H
;
ccADD EQU 050H
ccSUB EQU 051H
ccMUL EQU 052H
ccDIV EQU 053H
ccABS EQU 054H
ccNEG EQU 055H
;

```

4. Embedding the above command codes into the EPROM jump table in EMON51. Refer to the program section 'main monitor service routine'. For clarity lines before and after the insertion are given also.

```

;
; .....
;
ttGETU: CJNE A,#ccGETU,ttLINK
        LJMP GETUPC
ttLINK: CJNE A,#ccLINK,ttCLKREQ
        LJMP LINK1
ttCLKREQ: CJNE A,#ccCLKREQ,ttCLKRUN
        LJMP CLKREQ
ttCLKRUN: CJNE A,#ccCLKRUN,ttCLKSTP
        LJMP CLK_ON
ttCLKSTP: CJNE A,#ccCLKSTP,ttCLKWR
        LJMP CLKOFF
ttCLKWR: CJNE A,#ccCLK_WR,ttCLK_RD
        LJMP CLKWR
ttCLKRD: CJNE A,#ccCLK_RD,ttADD
        LJMP CLKRD
ttADD: CJNE A,#ccADD,ttSUB
        LJMP rADD16
;
; .....

```

5. The actual program

This program arranges the data exchange between 8051 and the Smartwatch module. In the EMOM51 monitor, it is located between routines "snap" and "Arithmetic routines".

```

;
; ***** Routines for Smartwatch DS 1216C *****
;
; ----- Clear and switch off clock (OSC bit)
;
CLKOFF: LCALL C_REG0 ;Clear storage register
        MOV DAY_NR,#00110000B ;Oscillator off, RES passive
        SJMP CLK_WR
;
; ----- Clear and switch on clock (OSC bit)
;
CLK_ON: LCALL C_REG0 ;Clear storage register
        MOV DAY_NR,#00010000B ;Oscillator on, RES passive
;
; ----- convey data from internal RAM to clock
;
CLK_WR: LCALL C_OPEN ;convey code word
;
        MOV DPTR,#CLKADDR ;Smartwatch dummy address
        MOV R0,#CLOCK ;Pointer to storage register
        MOV R7,#8 ;8 Bytes
        MOV R6,#8 ;8 Bits
        MOV A,@R0 ;Read byte
        MOVX @DPTR,A ;Clock write pulse
        RR A ;Bit 1 --> Bit 0
        DJNZ R6,WRBIT ;8 Bits written?
        INC R0 ;Next register
        DJNZ R7,WRBYTE ;8 Bytes written?
        NOP
        RET
;
; ----- Get clock status (OSC bit)
;
CLKREQ: ACALL CLK_RD ;Read hours register
        MOV A,DAY_NR ;Fetch control register
        JB ACC.5,C_OFF ;Bit 5 set (clock off)?
;
        MOV DPTR,#C_TXT1 ;Monitor report, clock active
        LCALL STXT
        RET
;
C_OFF: MOV DPTR,#C_TXT2 ;Monitor report, clock passive
        LCALL STXT
        RET
;
C_TXT1: DB 'Smartwatch active',13,10,0
C_TXT2: DB 'Smartwatch passive',13,10,0
;
; ----- Transfer clock data to internal RAM
;
UHR_RD: LCALL C_REG0 ;Clear storage register
        LCALL C_OPEN ;Convey code word
        MOV DPTR,#CLKADDR ;Dummy address
        MOV R0,#CLOCK ;Pointer to lowest storage req.
        MOV R7,#8 ;8 Bytes
        MOV R6,#8 ;8 Bits
        MOVX A,@DPTR ;Clock read pulse
        RRC A ;Bit 0 --> C bit
        MOV A,@R0 ;Read register
        RRC A ;C bit --> bit 7
        MOV @R0,A ;Write register
        DJNZ R6,RDBIT ;8 Bits read?
        INC R0 ;Next byte
        DJNZ R7,RDBYTE ;8 Bytes read
        NOP
        RET
;
; ----- Enable access to clock (64-bit code word)
;
C_OPEN: MOV DPTR,#CLKADDR ;Dummy address
        MOVX A,@DPTR ;Initialize clock
        MOV DPTR,#C_CODE
        MOV R7,#8 ;8 Bytes
        MOV R6,#8 ;8 Bits
        CLR A
        MOVC A,@A+DPTR ;Fetch constant
        PUSH DPH ;Save string pointer (DPTR)
        PUSH DPL
        MOV DPTR,#CLKADDR ;Dummy address
        MOVX @DPTR,A ;Clock write pulse
        RR A ;Bit 1 --> Bit 0
        DJNZ R6,CDBIT ;8 Bits written?
        POP DPL ;Restore string pointer
        POP DPH
        INC DPTR ;Next constant
        DJNZ R7,CDBYTE ;8 Bytes (64 bits) transf'd?
        NOP
        RET
;
C_CODE: DB 0C5H,03AH,0A3H,05CH,0C5H,03AH,0A3H,05CH
;
; ----- Clear 8 registers in internal RAM
;
C_REG0: CLR A
        MOV R7,#8
        MOV R0,#CLOCK
        MOV @R0,A
        INC R0
        DJNZ R7,ALL_0
        NOP
        RET
;
ALL_0:

```

ELECTROMAGNETIC COMPATIBILITY (2)


From theory to practice

By J. Ruiters

As already stated in Part 1 of this two-part article, the EMC Directive must be taken into consideration when the marketing, and thus the design, specification is drawn up. This makes it far cheaper for the final product to meet the EMC guidelines than taking corrective measures in the later stages of the production process.

Although much work has been done by, for instance, the Department of Trade & Industry, The Institution of Electrical Engineers, and organizations like ERA Technology, in informing industry and all who are affected by the Directive, the practical application of EMC is still in its infancy. This is mainly because of the great variety of possible compatibility problems: after all, each design is different from the next, each product may be used in a different environment. On top of that, there are specific requirements for specific systems. Here are a few guide lines for designers.

- **Design on the basis of representative models.** In other words, use models that are characteristic of reality. Too often designers take decisions on the basis of analyses on non-valid models. If, therefore, a design decision does not yield the desired effect or result, the conclusion must be that the model used was not, or only partly, correct.
- **Always consider component properties as a function of frequency.** This rule applies to the range 0 Hz to 12 GHz. For instance, in an optoisolator common-mode signals are converted to differential-mode signals; this process, in EMC terms, is frequency-dependent. Another example is that one metre of yellow/green earth wire (as found in mains cable) represents an inductance of 1 μH (this will be reverted to later). At 10 MHz, this gives an impedance of 63 Ω , which

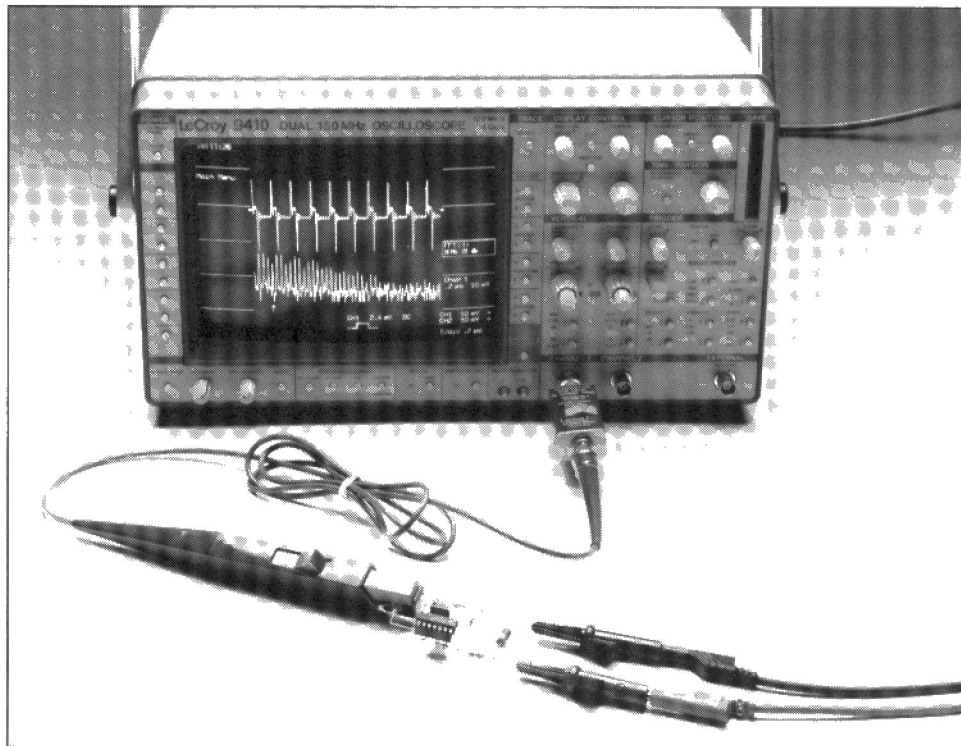

shows that much equipment cannot be made EMC approved by just 'earthing it properly'.

Figure 7 shows that the behaviour of electrolytic capacitors is strongly frequency-dependent: above about 10 kHz, an electrolytic capacitor is no longer a capacitor, but an inductor. This fact is important in decoupling power supply lines for high frequencies.

- **Think in terms of current.** It is well known that in a closed circuit current can flow even though the circuit is not connected to a voltage source. If such a circuit is placed in a varying magnetic field, a current equal to $-1/R \, d\phi/dt$ flows. This makes it clear that each measured potential difference (pd) is determined partly by the meter leads and the magnetic flux, $d\phi$, which (accidentally) is enclosed by these leads. It is, therefore, virtually impossible to conform to the EMC Directive on the basis of voltage considerations.

Even a more fundamental consideration of 'potential difference' leads to a preference of thinking in terms of current. From Maxwell's Second Law, which is applicable to each and every electromagnetic phenomenon, it follows that at frequencies that are not zero the potential difference between two points is dependent on the route along which the

electric field is integrated. Strictly speaking, therefore, potential difference has meaning only in the context of electrostatic fields. Note that Kirchhoff's Second Law ($\sum U=0$) is merely a special case of Maxwell's Second Law ($\sum U=-d\phi/dt$) and is, therefore, often not sufficiently accurate. However, Kirchhoff's First Law ($\sum I=0$) is always valid. In other words, voltage does not always have a rational physical meaning, whereas current does.

Properties of current

From what has been said, it is important to be well aware of a number of properties of current. In the first place: **currents always flow in closed circuits (loops)**. This is an important fact, because it is these loops that determine the emission and susceptibility to interference of an electronic circuit. It also explains why earthing does not always have the desired effect. After all, a current will flow to earth only if it cannot flow elsewhere. Mother earth is definitely not a bottomless pit into which we can dump all our interfering signals.

Each and every current sets up an electromagnetic field. A current-carrying conductor is always surrounded by a magnetic field (H), while as a result of the charge on the conductor an electric field (E) ensues between the conductor and its

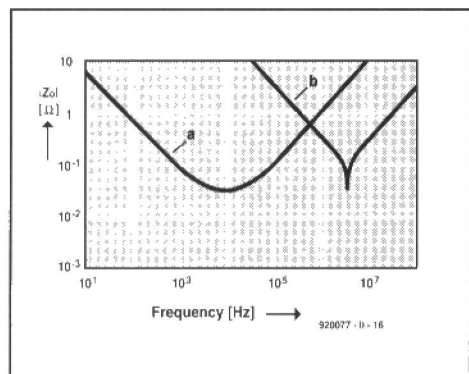


Fig. 7. Impedance as a function of frequency, (a) of a 2200 μF capacitor, and (b) of a 470 pF ceramic capacitor.

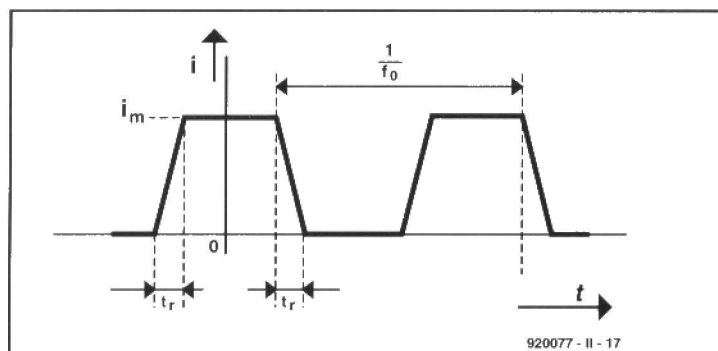


Fig. 8. True rectangular waveforms cannot be attained; the usual shape is trapezoidal as shown (slightly exaggerated).

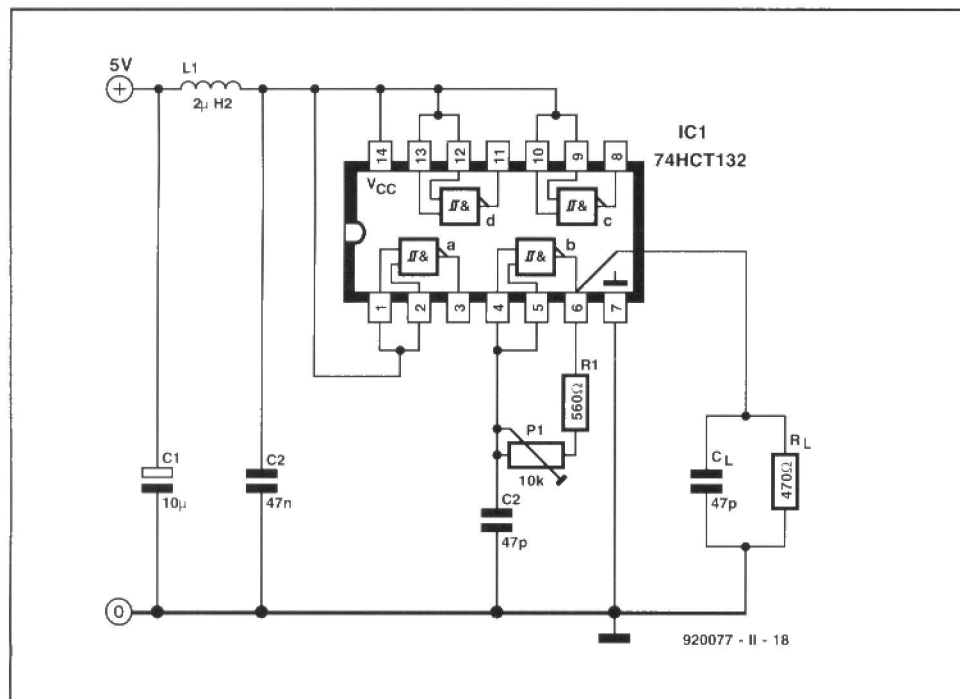


Fig. 9. In this digital oscillator, several currents have been measured. The measurement set-up is as shown in the introductory photograph.

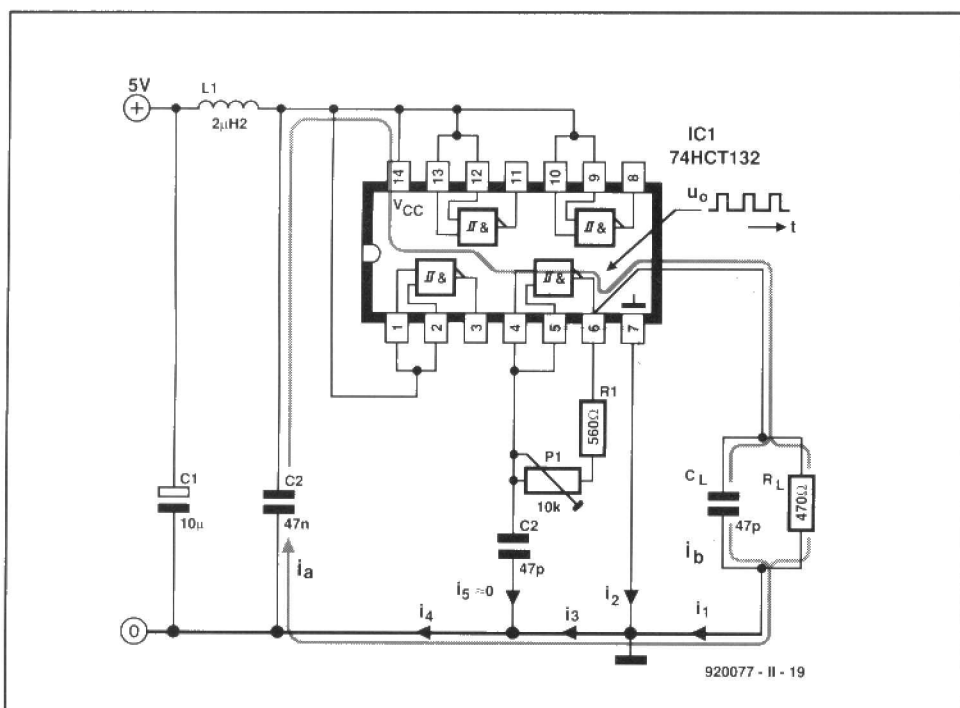


Fig. 10. The radiation of the oscillator is determined by currents i_a and i_b .

environment. The electromagnetic field causes the conductor to have not only resistance, but also several parasitic properties, such as inductance (1 nH mm^{-1}) and capacitance (read: coupling) to its ambience. The electromagnetic fields cause couplings over (electrically) short distances: cross talk.

To be able to predict the electrical behaviour of a design on the basis of a (low-frequency) network model (the CAD drawing, for instance), these field effects must be taken into account by adding to the model the correct parasitic components and sources. *E*-field couplings (interfaces) are indicated by parasitic *C*s (important in, for instance, cross talk in high-impedance clock circuits), and *H*-field couplings by parasitic *M*s (mutual inductance) or *L*s (self inductance).

It is obvious that a knowledge of these matters is of importance in the design of printed-circuit board layouts. Many current CAD programs were written before the EMC Directive was formulated, so that, in order to comply with EMC guide lines, many critical tracks (usually about half of the total) must be laid manually by the designer.

Low and high frequency

Network theory enables the designer to approximate physical reality with models by replacing the *E*- and *H*-fields by impedances. It must be borne in mind, however, that the familiar low-frequency approximation is permitted only if the length, ℓ , of the current loop is small with respect to the wavelength $\lambda = 3 \cdot 10^8 f^{-1}$. In words, the low-frequency approximation is valid for small systems only, that is, systems that satisfy the rule of thumb $\ell \leq \lambda/10$. Even then, as has already been hinted at, a low-frequency analysis will already lose much of its value if the effects of the *E*- and *H*-fields are not, or insufficiently, specified in the network elements (for instance, because it was assumed that there are no fields around or between the connecting wires).

In the case of a large electrical system ($\ell \geq \lambda/10$), that is, a high-frequency system, the designer must apply transmission line theory (characteristic impedance, reflections, standing waves, and so on).

Designing current loops

The electric field strength around a current-carrying circuit (read: small magnetic dipole) is directly proportional to the area of the loop in which the conductive or capacitive displacement currents flow. The maximum radiated field, E_m , at a distance r from a small current loop through which a trapezoidal current flows (see Fig. 8), is estimated from:

$$E_m = 2Z_0 S / \pi r c^2 f_0 i_m / t_r \quad [\text{V m}^{-1}]$$

where Z_0 is the radiation resistance in

air (377Ω), S is the area of the current loop, c is the speed of propagation of electromagnetic waves ($3 \cdot 10^8 \text{ m s}^{-1}$), f_0 is the frequency of the trapezoidal current, i_m is the pulse magnitude, and t_r is the first transition duration (rise time). The expression applies to a distant-field situation, which assumes that the observer distance, $r > \lambda / 2\pi$.

The wavelength $\lambda = 3 \cdot 10^8 / f$ is thus a yardstick of whether the approximation formula may or may not be used. It is important to note that λ is not the fundamental frequency, but the harmonic nearest to $1/\pi t$ Hz. This is because the electric field strength reaches its highest value with harmonics around this spectral cut-off point.

That the area, S , in the above expression must include the entire loop is made clear by considering a Schmitt trigger oscillator (see Fig. 9), which is based on a Type 74HCT132 NAND gate. The oscillator frequency can be varied with P_1 over the range 1–10 MHz.

Capacitor C_1 and low-pass filter L_1 – C_2 bound the emission area in the direction of the power supply. Because of L_1 , C_1 , and C_2 , the spectrum of the supply current (to the left of L_1) consists of low-frequency components that do not contribute to the radiation.

Because of the load on the gate, R_1 – C_L , two current loops ensue that determine the radiation. The first, indicated in Fig. 10 by i_a , carries the sum of the currents through R_L , the charging current of C_L , and the switching current of the IC. The second mesh current, i_b , is characterized by the displacement current that arises as a result of C_L discharging at the instant the output of IC_{1b} goes low.

The current waveforms, i_1 – i_3 , mea-

sured with a current probe are shown sequentially in Fig. 11. Note that i_3 is negligibly small, whence $i_4 \approx i_3$. Note also that the amplitude of the currents (and thus the strength of the radiated field) is determined by C_L and not by R_L . In practice, C_L consists of the sum of the wiring capacitance, and the input capacitance of the digital circuit.

Characteristic values for the IC are: $t = 3 \text{ ns}$, $i_m = 40 \text{ mA}$ and $S = 25 \text{ cm}^2$. Substituting these values in the radiation formula, it is possible to estimate the maximum field to be expected at a distance of 10 m from the oscillator. From this, it appears that the radiation limit of $30 \mu\text{V m}^{-1}$ is already reached at an oscillator fre-

quency of 3.3 MHz. The harmonics responsible for the limit to be exceeded lie above $1/\pi t$, that is, 106 MHz, or from the 33rd harmonic up ($1/\pi t f_0$).

To keep the radiation from current loops within bounds, a well thought out PCB design is imperative. Particularly effective is a board with a reference plane or reference grid. On such a board, the main part of the return current flows underneath the supply line (in agreement with the minimum-flux principle, this is the route of least impedance). A further benefit is that this also gives the smallest possible area of the current loop. All these measures reduce the radiation. On single-sided boards and double-sided

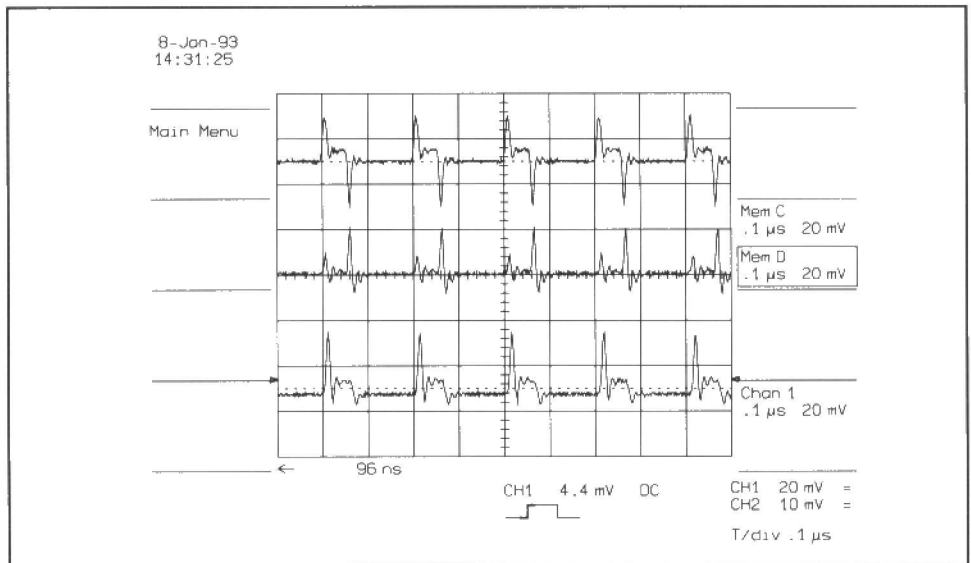


Fig. 11. The output current of the IC, 1, consists of the charging and discharge current of C_L and the current through R_L . The current in the earth conductor, 2, consists of the discharge current of C_L and the switching current of the IC itself. The current in the large loop is equal to currents 1 and 2.

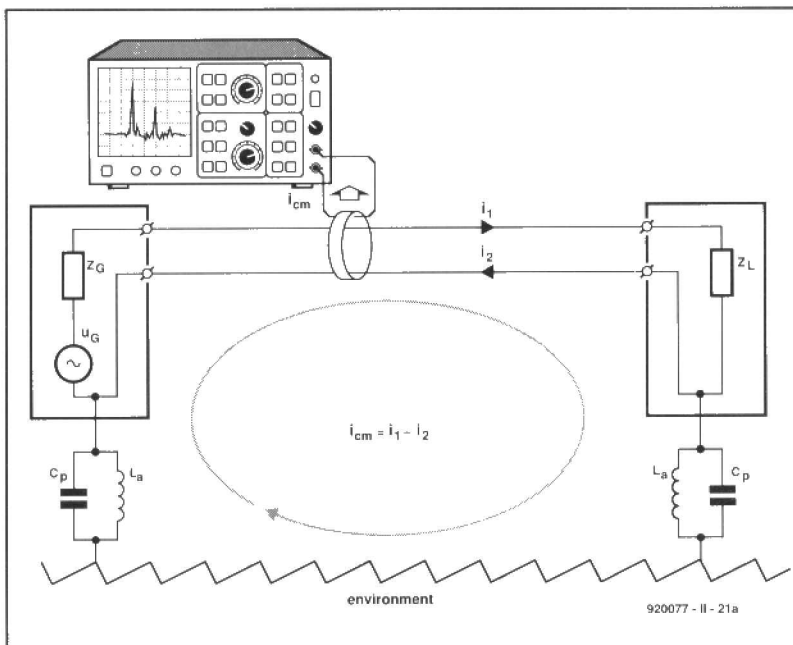


Fig. 12. Common-mode currents occur as the result of a coupling between the circuit and its environment. They may be measured with an HF tong-test ammeter and a spectrum analyser. The coupling is represented here by parasitic capacitances C_p and earth connections L_a .

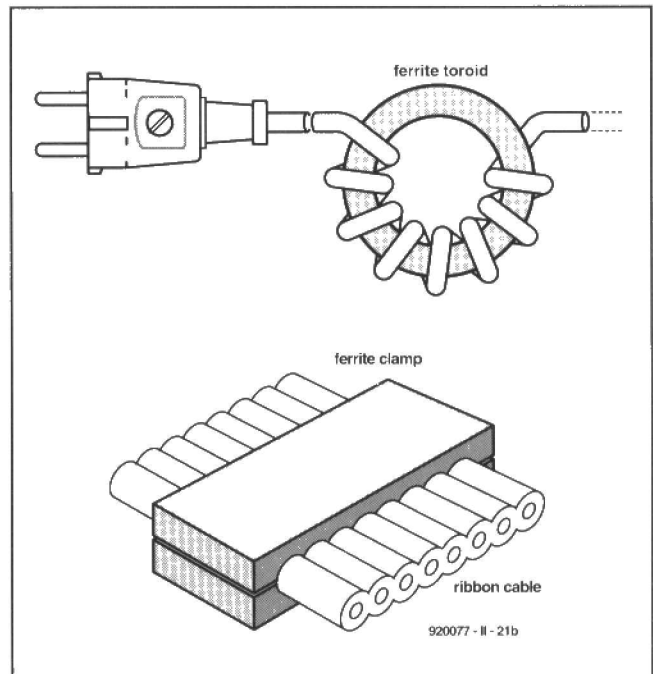


Fig. 13. Radiation may be reduced by ferrite materials like a clamp around a flat cable or the mains cable wound around a ferrite toroid.

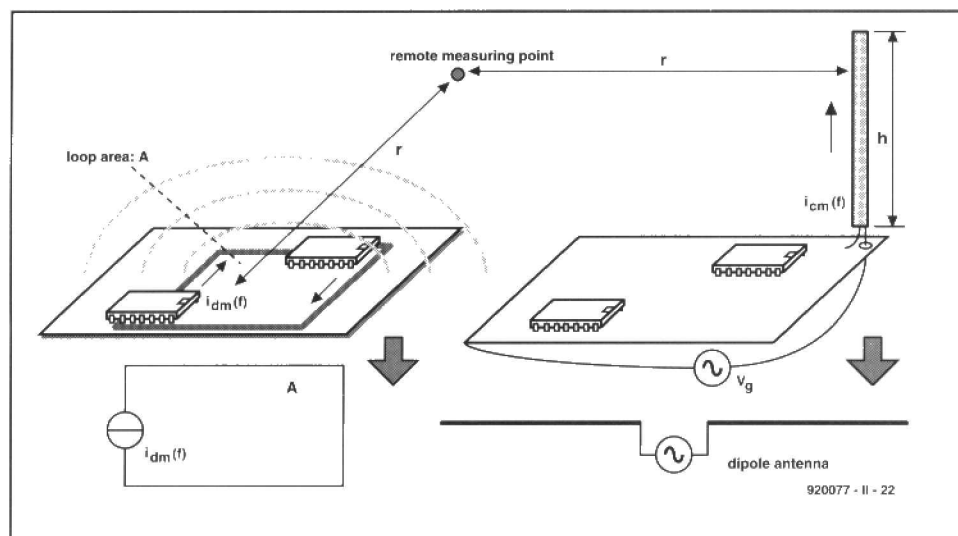


Fig. 14. Energy transfer by radiation. Differential mode radiation (left) is a result of the (wanted) current through an electrically small loop. Common-mode radiation (right) results from an (unwanted) antenna current through the cables.

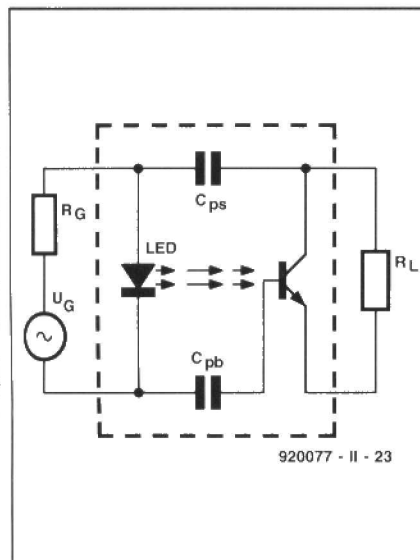


Fig. 15. Parasitic capacitances C_{pb} and C_{ps} cause the conversion in the optoisolator of CM signals into DM signals.

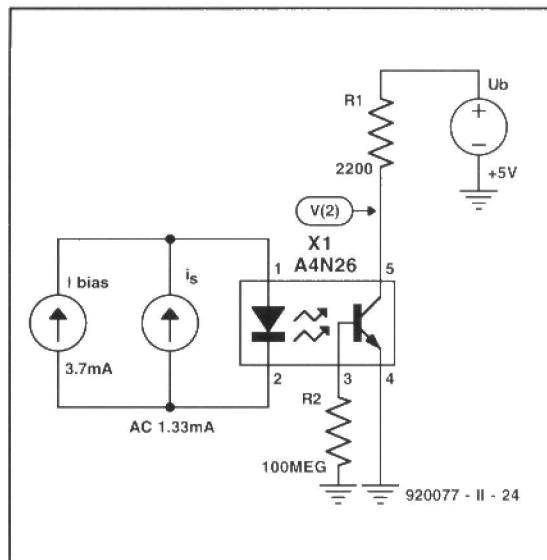


Fig. 16. Pspice model of the electrically isolated data connection in Fig. 15.

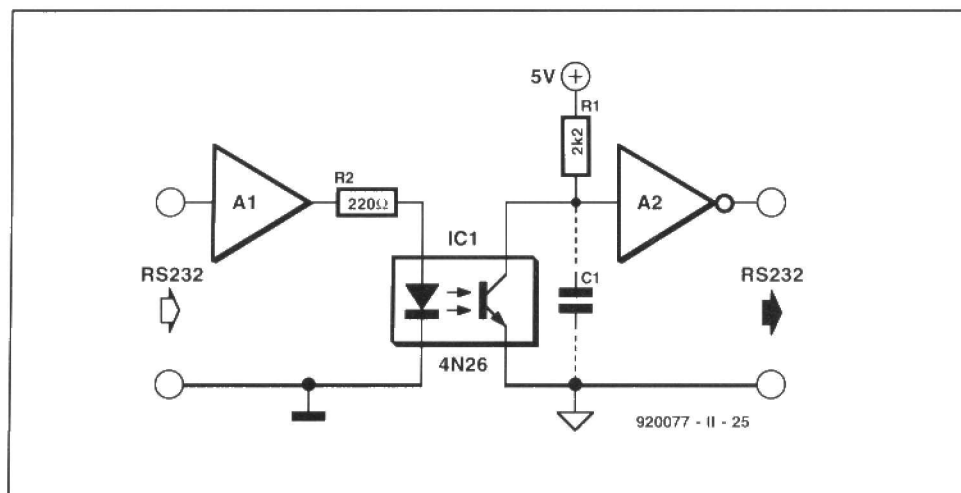


Fig. 17. Basic circuit of an electrically isolated data connection.

ones without a reference grid, the current-loop areas may be kept small by keeping the distance between the supply and return conductors small.

Also, it is advisable never to use faster logic circuits than is necessary: a higher t_r will after all cause a lower E_m . Furthermore, it is clear from the radiation formula that the clock frequency should be as low as possible. The phenomenon that E_m is directly proportional to the clock is a consequence of the fact that the amplitude of the harmonic near to $1/\pi t$ is directly proportional to f_0 . Since the electric-field strength is directly proportional to the amplitude of the current, it is also directly proportional to f_0 .

Beware of common-mode currents

A current loop always maintains a coupling with its surroundings, either by conduction or by radiation. 'Surroundings' include objects such as a metal table top, a central heating radiator, an earthing point, and so on. It all depends on which coupling predominates at a given frequency. Owing to the coupling to the surroundings, common-mode currents, also called asymmetrical currents, arise—see Fig. 12. Unfortunately, common-mode currents often flow through conductors (supply cables), whose dimension is of the same order as the wavelength: for instance, $106 \text{ MHz} = 2.8 \text{ m}$. This means that in electronic systems whose dimensions are much smaller than the wavelength of the signals, the cables connected to the system radiate more than the tracks on the PCB. Therefore, **the radiation of most products is determined by the magnitude of the high-frequency common-mode currents flowing in the cables.**

The CM currents may be measured with an HF tong-test ammeter and a spectrum analyser. In the design stages this test and the rule of thumb $I_{CM} < 5 \mu\text{A}$ gives a good idea of whether the radiation will be higher or lower than the legal limit of $30 \mu\text{V m}^{-1}$. If, in the prototype, the measured CM current through one of the cables (mains lead, cable to printer, signal cables) is greater than $5 \mu\text{A}$, the final product will almost certainly exceed the maximum permissible radiation.

The radiation can be reduced by inserting a high CM impedance in the current path. For example, a ferrite clamp may be placed around a flatcable as shown in Fig. 13. The same drawing shows how the CM currents in a mains lead may be reduced by winding the lead through a ferrite toroid.

Figure 14 shows two other ways via which interference may be transferred through radiation.

Design example

An optoisolator can often be used to put

some of the rules stated into practice. It is an analogue device that is frequently used with digital hardware. In such cases, the optoisolator is controlled digitally, so that, at least from a functional point of view, its output is also digital.

A suitable optoisolator for use in EMC designs is shown in Fig. 15. As usual in such a device, the signal transfer is effected by light. Capacitors C_{pb} and C_{ps} show, however, that there is another, spurious coupling between input and output. The effect of these parasitic capacitances has been investigated with a simulation program, Pspice. A setup with which this program can be used is shown in Fig. 16. This model is derived from the electrically isolated data connection in Fig. 17.

In Fig. 16, the optoisolator has been set to its linear operating range with a direct current of 3.7 mA. This value has been determined empirically and ensures that a direct voltage, whose level is equal to half the supply voltage, is present at the output. To enable the differential mode to differential mode transfer, $u_{out}/i_s = V(2)/i_s$, to be computed, an alternating current source, providing 1.33 mA, has been added at the input. With Pspice this source can be frequency-swept and the amplitude characteristic shown in Fig. 18 calculated. The most important datum to be gleaned from the characteristic is that the bandwidth for the wanted signal transfer is about 25 kHz.

In practice, the electrically isolated data connection will be affected by the common mode source of interference across the optoisolator. To study the effect of this, a voltage source, u_{CM} , and two 50- Ω impedances have been added to the model in Fig. 19. Since the optoisolator is not ideal (C_{ps} and C_{pb}), part of u_{CM} will appear at the output. This is awkward, because this interference signal is in series with the output voltage. If the level of the interference is (relatively) high, it is possible that gate A2 (read: wideband amplifier) produces erroneous logic levels during the transition from one to the other. This comes down to insufficient immunity. Note that this transition in EMC literature is called common-mode/dif-

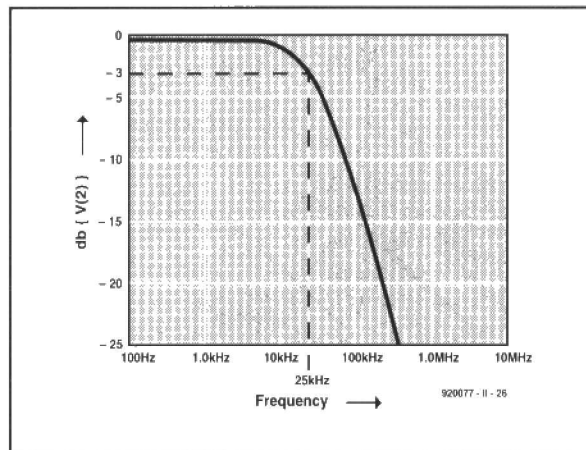


Fig. 18. The simulated DM-DM characteristic according to Fig. 16.

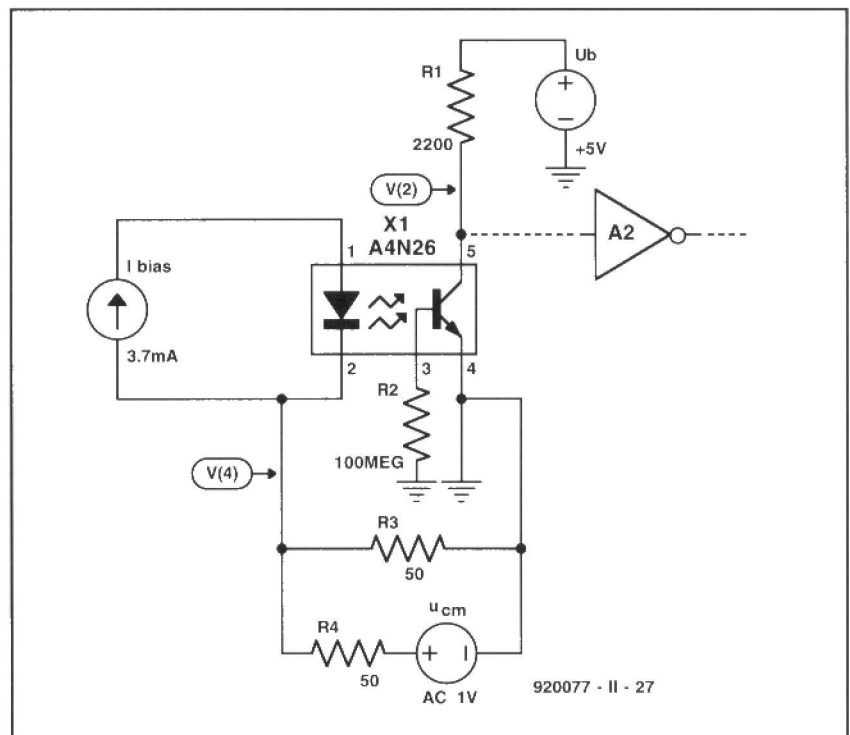


Fig. 19. To compute the CM-DM transfer, voltage source u_{CM} was added to the model in Fig. 16.

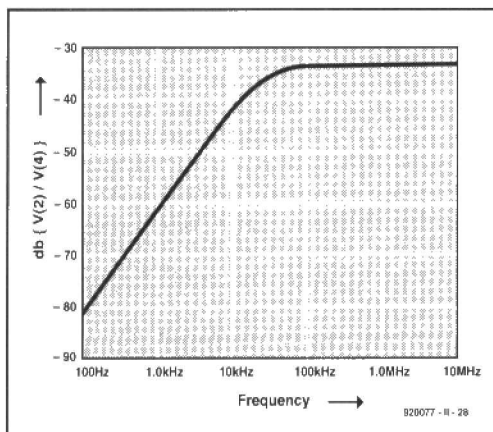


Fig. 20. CM-DM transfer characteristic computed from the setup in Fig. 19.

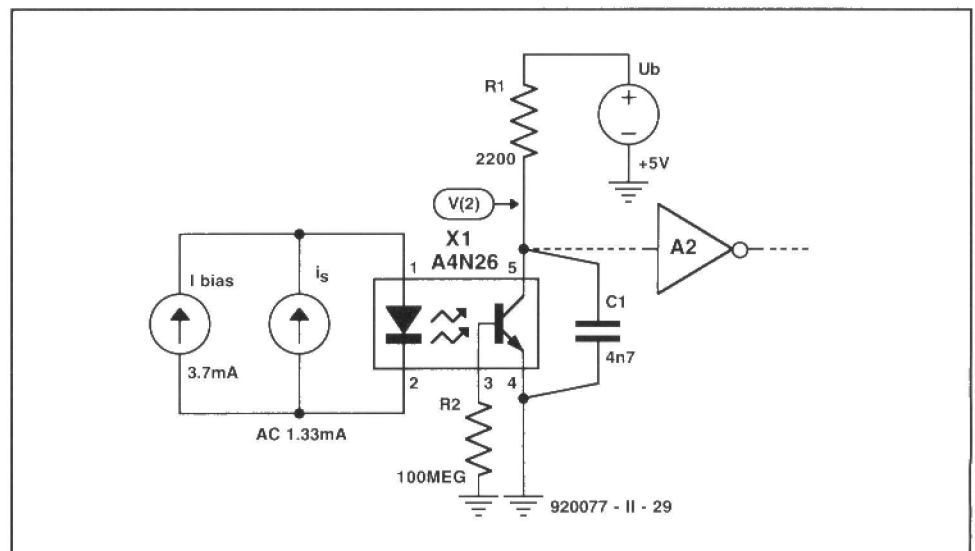


Fig. 21. Capacitor C_1 reduces the DM transfer at high frequencies.

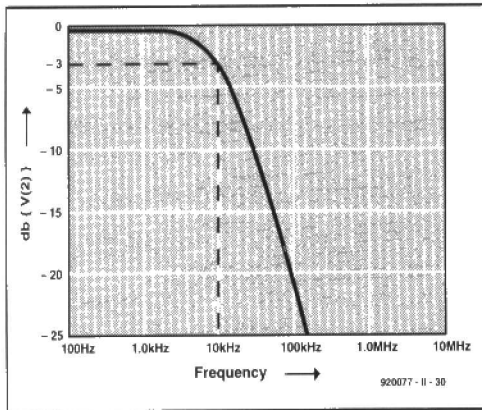


Fig. 22. The DM-DM characteristic for the set-up in Fig. 21.


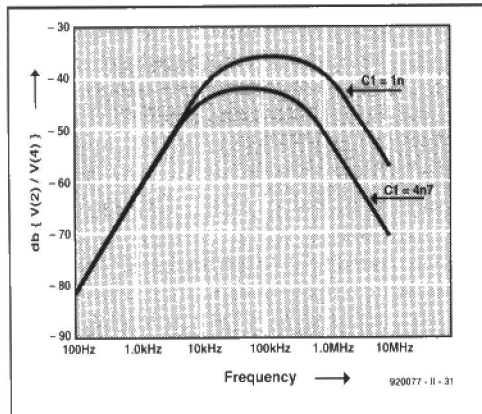


Fig. 23. The CM-DM transfer characteristic for Fig. 21 with different values for C_1 .

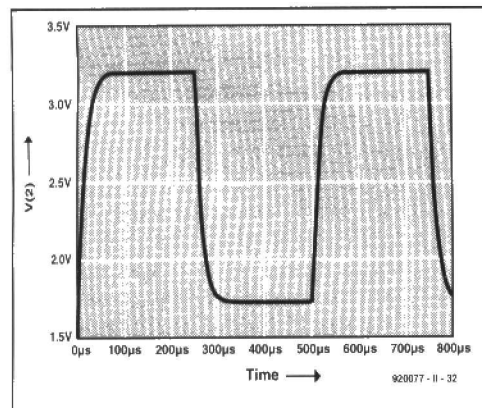

ferential mode (CM-DM) transition.

The quality of an optoisolator, as far as immunity is concerned, is a measure of the degree to which CM signals are suppressed. The characteristic calculated on the basis of the model in Fig. 19 is shown in Fig. 20. This indicates that the suppression of CM signals reduces with rising frequency. Again, this is awkward, because, in practice, u_{CM} contains primarily HF (>1 MHz) components. The characteristic can, however, be improved greatly by reducing the bandwidth of the optoisolator. This is done in Fig. 21 by shunting the switching transistor with a 4.7 nF capacitor. This reduces the bandwidth to about 10 kHz—see Fig. 22; the CM suppression for high frequencies is thereby increased. The CD-DM characteristic for the model in Fig. 21 with shunt capacitors of 1 nF and 4.7 nF is given in Fig. 23. It is clear from the curves that the CM suppression is inversely proportional to the bandwidth.

When the electrically isolated data connection in Fig. 17 operates at a bandwidth (BW) of 10 kHz, the first transition duration (rise time), t_s , of the pulses at the output of the optoisolator is $t_s = 0.35/BW = 35 \mu s$. The maximum input frequency at which a correct digital signal can be measured at the collector of the phototransistor is, by rule of thumb, $BW/5 = 2$ kHz. The output signal simulated with Pspice is shown in Fig. 24; the model is given in Fig. 25. The circuit is thus suitable for use in an RS232 connection with baud rates up to 4000 Bd (which coincides with the frequency limit of 2 kHz). A complete design was published earlier this year*.

*Electrically isolated RS232 interface. *Elektor Electronics*, March 1993.

Fig. 24. Characteristic of the output voltage with a channel bandwidth of 10 kHz and a rectangular (2 kHz) input current.

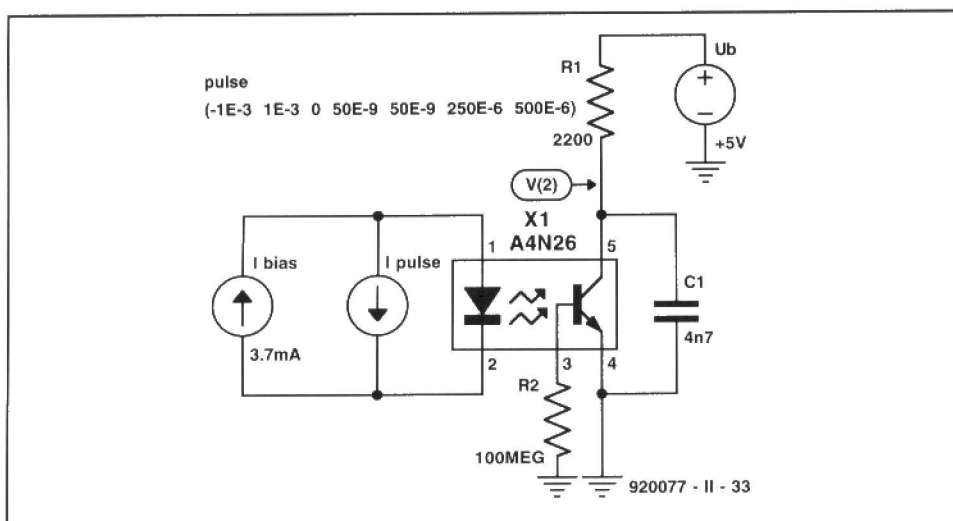


Fig. 25. Model used by Pspice for computing the characteristic in Fig. 24.

Further reading:

Electronic system design: interference and noise control techniques, ISBN 0-13-252 123-7, by J.R. Barnes, Prentice Hall, 1987.

Interference-free electronics: design and applications, ISBN 0-86238-255-6, by S. Benda, Chartwell Bratt, 1991.

Electromagnetic compatibility: Europe, ISBN 0-580-20917-2, British Standards Institution, 1992.

EMC: electromagnetic theory to practical design, ISBN 0-471-82878-X, by P.A. Chatterton & M.A. Holden, Wiley, 1992.

ZZAAP! taming ESD, RFI and EMI, ISBN 0-12-189930-6, by M.B. Corp, Academic, 1990.

Electromagnetic compatibility: bibliography and information pack (2nd Edition), ISBN 0-85296-495-1, by J. Coupland & P. Fountain, IEE Technical Information Unit, 1993.

Grounding for the control of EMI, ISBN 0-932 263-17-8, by H.W. Denny, Don White Consultants, 1989.

Electromagnetic compatibility in radio engineering, ISBN 0-444-99722-9, by W. Rotkiewicz (ed), Elsevier Scientific, 1982.

Electromagnetic compatibility: applied principles of cost-effective control of electromagnetic interference and hazards, ISBN 0-8247-1887-9, by H.M. Schlicke, Marcel Dekker, 1982.

Electromagnetic compatibility handbook, ISBN 0-442-28903-0, by J.L.N. Violette, D.R.J. White & M.F. Violette, Van Nostrand, 1987.

Designers may also note that Rohde & Schwarz's Type ESHS 10 and ESVS 10 test receivers are now available from Livingstone Hire. These instruments meet the measurement requirements of European EMC Standards incl. 55 011 to 55 022, ETS, FCC, VCCI and VDE 0871 to 0879. Full information on these versatile instruments from Livingstone Hire, Livingstone House, Queens Road, Teddington TW11 0LB, England. Telephone (0)81 943 5151; Fax (0)81 977 6431.

CW COMPATIBLE T/R SWITCH

The use of CW (morse) on a high-power transmitter/receiver presents a serious risk of burned antenna (coax) relay contacts or destruction of a GaAs FET preamplifier. Fortunately, that problem can be overcome quite easily at a very small outlay with the circuit described here.

Design by Pedro Wynn, ON4AWQ

ALTHOUGH a number amateur radio magazines have recently carried designs that ensure that antenna relays change before the transmitter is powered, most of these circuits are suitable for 'phone' (voice) transceivers only. Just in case you did not know, early switching of the antenna relay is necessary to protect the expensive and

highly sensitive GaAs FET preamplifier(s) against the huge power produced by the transmitter.

The trouble starts if you want to use a commercial VHF or UHF transceiver for high-power, high-speed CW modes such as Meteor-scatter, Tropo-DX or EME (earth-moon-earth). These modes require high transmitter power levels

and extremely sensitive preamplifiers. Unfortunately, most commercial transceivers have a built-in COR (carrier operated relay), which powers the transmitter the instant the morse key is pressed, not allowing sufficient time for the antenna relay to switch over.

The circuit shown here is connected between the microphone, CW key and the transceiver. The operation of the circuit is quite simple: in 'phone' mode, the antenna relay is energized the instant the PTT switch on the microphone is pressed. The transmitter, however, is switched on a little later by a timer built around Schmitt-trigger NAND gate IC1c. When the PTT switch is released, the reverse takes place: the transmitter is switched off immediately, while the relay is de-energized a little later because of the delaying action of gate IC1d.

When CW is used, the key signals are blocked by wired-AND gate IC1a-T2 until the delay introduced by timer IC1c has elapsed (approx. 200 ms). The circuit around IC1b provides a 'hang' time of about 2 seconds to prevent relay clatter while the transmitter is being keyed. Transistors T4 is a darlington type to enable relays 'outside' the transceiver to be controlled also. If this is not required, the BD675 may be replaced by a BC547. Note that the collector of T5 is supplied via the coil of the Tx/Rx relay in the transceiver. ■

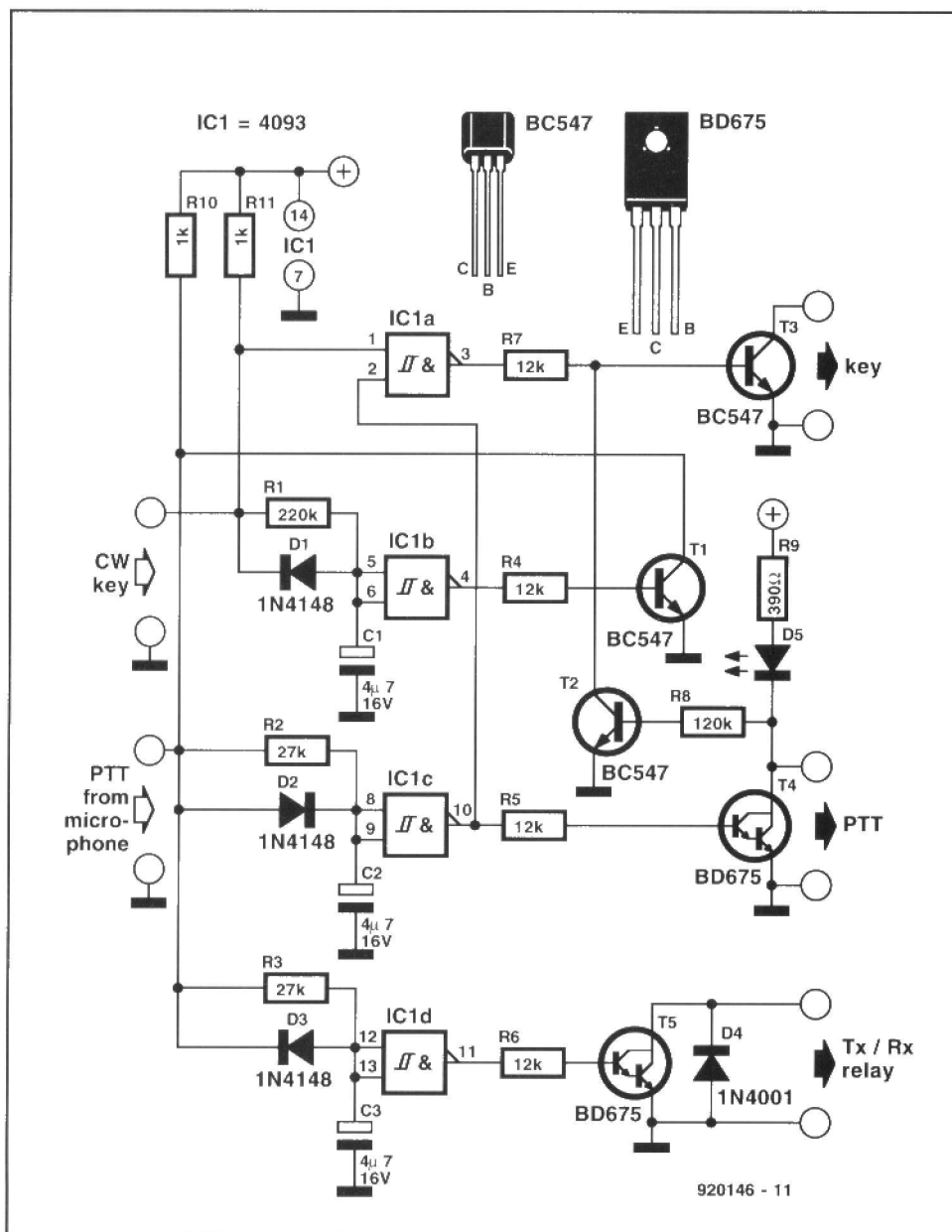


Fig. 1. Circuit diagram of the transmit/receive switch

READERS' CORNER

LETTERS

Dear Editor—In many of your construction projects, we, the readers, are advised to observe due safety precautions. It is, however, and certainly in this part of the world, difficult to find out exactly what these safety precautions are. Are there any books on this subject you can recommend?

K. Laukkanen, Turku, Finland

Safety regulations differ from country to country; in the main they apply to mains operated equipment only. Strangely enough, there are hardly any books on the subject. In the UK, a good general introduction to safety in electrical circuits is 'Regulations for Electrical Installations' published by the Institution of Electrical Engineers.

In general, safety regulations apply when (a) the circuit carries voltages above 40 V; (b) parts of the circuit can become hot; (c) the circuit presents a fire risk; (d) the circuit

may harm the user (for instance, equipment that uses lasers).

In the drawings and text for such equipment, publishers and designers must give the readers enough information to enable them to build a safe equipment without having to consult third parties. Therefore, we refer to the dangers involved in constructing, and working with, equipment specified under (a) to (d) above.

Furthermore, we must indicate for which voltage the equipment is intended and whether it is DC or AC, the power rating of the equipment, and the rating of the fuse and its speed (that is, delayed or fast). The mains transformer should be specified, but unfortunately that is not normally possible because of the varying requirements in different countries. In the UK, the mains cable is invariably a three-core type, but in many countries (and in some commercial equipment) two-core cable is the norm.

Earthing in the UK is automatic because of the three-core mains cable; if two-core cable

is used, double insulation of the transformer or equipment is a legal (and sensible) requirement. The on-off switch (obligatory for equipment that has a power rating of more than 10 W) should always be specified as a mains on-off switch (double pole).

After the mains has been switched off, any high voltages must drop to below 40 V within 2 seconds. It must be clearly seen at the outside of the equipment whether the mains is on; the visual indicator itself must be safe; it should be seated in an approved holder.

The air or the insulation forms the shortest distance between mains-carrying parts and parts that can be touched. Nowhere in the equipment is this distance allowed to be smaller than 6 mm. Constructors are well advised to ensure, wherever possible, that the mains carrying parts are well separated from the remainder of the circuit. It is always advisable to use a mains entry with integrated fuse and on-off switch. If a mains entry is not used, the mains cable must be

EVENTS

IEE AND IEEIE PROGRAMME

- 1 June—Hardware safety standards.
- 1 June—Electromagnetic compatibility for project managers.
- 2 June—Impact of quality on Europe.
- 3 June—Optical switching.
- 3 June—Power electronics and motors for home and garden.
- 7 June—ASICs (Application Specific ICs) in signal processing.
- 7 June—Safety engineering: methods and tools.
- 8–9 June—Electrical installation engineering in Europe.
- 10 June—AMT (Advanced Manufacturing Technology): justifications and update.
- 11 June—Discrete event systems.
- 11 June—Design calculations for small electrical installations.
- 15 June—Satellite services for Eastern Europe.
- 15 June—Fault location.
- 16 June—Mobility in support of personal communications.
- 16 June—Portable appliance testing.
- 17 June—The effect of the Single Market on the specification, manufacture and certification of transmission equipment.
- 18 June—Total quality ISO9000.
- 23 June—Periodic inspection and testing of electrical installations.
- 30 June–14 July—Photographic, computer art and engineering models exhibition.

Further information on these, and many other, events may be obtained from the IEE, Savoy Place, London WC2R 0BL; Telephone 071 240 1871, or from the IEEIE, Savoy Hill

House, Savoy Hill, London WC2R 0BS; Telephone 071 836 3357.

ERA Technology will hold a Management Briefing-Seminar, **Improving Time to Market through Concurrent Engineering**, on 2 June in Solihul. The company will also arrange a Conference and Exhibition on **Integrated Earthing** in June/July.

Details from ERA Technology Ltd, Cleeve Road, Leatherhead KT22 7SA. Telephone (0372) 374 151.

The **British Association for the Advancement of Science** has arranged the following events. **Science Pavilion** at the Urd National Eisteddfod from 31 May to 5 June; **Investing in R&D**, a conference in the City of London, exact date to be announced, and **Science is Great**, an award winning event for primary schools, in Hartlepool from 8 to 11 June.

Further information from the British Association for the Advancement of Science, Fortress House, 23 Savile Row, London W1X 1AB. Telephone 071 494 3326.

All Formats Computer Fairs will be held on 19 June at the Novotel, Hammersmith, London; 20 June at the Brunel Centre, Temple Meads, Bristol; 26 June at Haydock Park Racecourse (M6, J23); 27 June at the National Motorcycle Museum (M42, J6). Further information from Bruce Everiss on (0608) 662 212.

The **Electronic Components & Technology Conference** will be held in Washington, DC

from 1 to 3 June. For further information, phone +1 (803) 963 6621

Eurotherm, a European seminar on the thermal management of electronic systems, will be held at Delft University, the Netherlands on 14–16 June. For further information, phone 081 547 3373.

The Design automation conference, **DAC '93**, will be held in Dallas, Texas, on 14–18 June. For further information, phone +1 (303) 530 4333.

The **Instrumentation Scotland** exhibition, the **Scottish Computer Show**, and the **Vacuum and Semiconductor Processing** Exhibition will be held on from 22 to 24 June at Glasgow. Details from Trident Exhibitions at 0822 614671.

The **Networks** exhibition will be held at the NEC, Birmingham from 29 June to 1 July. Further information from Blenheim Online on 081 742 2828.

DX TELEVISION

A two-monthly column by Keith Hamer and Garry Smith

SEVERAL intense tropospheric openings punctuated the bleakness of February and March. Signals were plentiful in Band III and at UHF, particularly on February 14th when many French, German and Benelux stations emerged at considerable strength.

By comparison, Band I reception was relatively quiet, apart from several sustained sporadic-E openings in the latter half of February. Other Band-I activity was due to meteor-scatter and auroral activity.

Reception reports

Andrew Jackson of Birkenhead has written to say that tropospheric reception conditions were excellent during February. The most productive day was Sunday 14th when most of the 'usual' signals were around plus some new ones. Transmissions received in clear colour included RTBF-1 (Belgium) on channel E57, RTBF-TELE 21 on channel E60, and Canal Plus (France) on channel E63. The 'VOX-Koeln' FuBK test card was received on the 5th and the 13th, and this was also strong. Sporadic-E activity occurred on February 15th at 2037h with prolonged reception from a German ARD-1 transmitter on channel E2.

Andrew has been monitoring the new Irish TV channel allocations from the Kippure transmitter on a daily basis. RTE-1 can be good at times although co-channel interference from the Maghera transmitter does occur. Signals from the Band-I channel B Maghera outlet have also been available during tropospheric activity.

On the 14th, a strange-looking test pattern was present on channel E11 for most of the day and well into the evening. It resembled the FuBK pattern, but had a distinctive central 'window'; there was no identification. This was subsequently identified as 'Canal Plus Belgique' on test from the Leglise transmitter, which once broadcast RTBF-1 programmes.


Davis Asher of Wrexham has only DXed at UHF so far, but plans are afoot to install VHF equipment in the near future. His successes include several Dutch and German outlets, with the reception of almost perfect Teletext from the Nederland-3 network. Unfortunately, Nederland-2 on channel 27 is now blocked by a local relay station. His equipment consists of a 10-element wide-band aerial, aligned East North-East.

This is fed into a home-brew mast-head amplifier with 15-20 dB gain. A Goodmans 20-inch Teletext receiver and Goodmans 2500 VCR completes the set-up.

Stephen Michie of Bristol found that early February was active with sporadic-E on the 2nd from Hungary. Reception consisted of a tennis match and later the PM5544 test pattern with the identification 'MTV-1' at the top, and 'Budapest' in the lower black rectangle. There was enhanced tropospheric reception on at least seven days, with the weekend of the 13/14th being the most active. One German station was transmitting the FuBK test pattern with the inscription 'ARD 1 PROG' and the date and digital clock below the central block. There was an unidentified German signal on channel E36 which was possibly RTL PLUS from Dusseldorf. Stephen found that March was very quiet with only the daily signals from the Goes transmitter, and the occasional reception from Lopik (both outlets are located in the Netherlands).

Iain Menzies of Aberdeen has been monitoring the HF bands to evaluate the MUF (maximum usable frequency) and the reception conditions in general. On 24th February, a station in Michigan reported a MUF of 46 MHz. Sporadic-E signals were noted two days later at 1900h UTC on channel R1, almost totally masked by baby alarms! On the 27th on 28 MHz between 0830h and 1030h UTC, Australia was heard at S9+ with several FM transmissions at over 30 MHz. Unfortunately, the MUF did not reach TV frequencies.

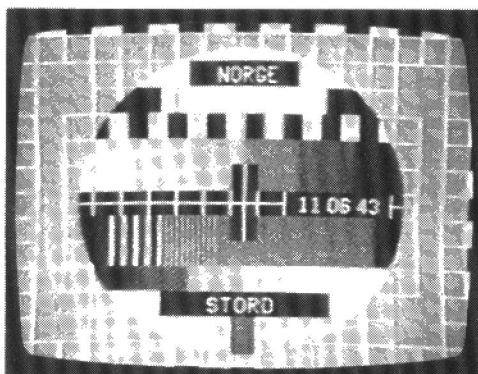During the first five days of March, South African stations reported working as far North as Brittany. On March 11th,



The PM5534 test card from the Stord transmitter (30 kW ERP channel E5) in Norway, received in Derby via Sporadic-E.

an aurora produced GI and G stations with excellent results from the Lerwick beacon. The usual beacon received via auroral activity was not heard. During the same opening, weak unidentified signals were present on TV channels E2 and R1. On 12th March at 1930h UTC the Lerwick beacon was received again via Aurora, but this time there were no TV signals. The MUF has since been extremely poor. Even 28 MHz has been a struggle at times!

According to Simon Hamer of New Radnor in Powys, the weather forecast on Scottish TV is sponsored by *Kwik-Fit*, and not *Legal and General*. Grampian ITV's clock resembles the old TVS one, though blue and white. The identification in red and white on the Danish PM5534 test pattern is, according to Simon, to tie in with their national flag.

Simon has confirmed that RTL-2 is now operational on the Astra 1A satellite, replacing Screensport. RTL-2 is a spin-off from RTL Plus, but more family-oriented and without 'adult' films. The RTL-2 news is called *Action News*. This service is also available on Eutelsat II F1.

Simon has also advised that various BBC Radio broadcasts can now be found on the UK Gold transponder of the Astra 1B, using the Wegener Panda-1® system. The satellite subcarriers transmit the BBC World Service on 7.38 MHz, Radio 4 (long wave version) on 7.56 MHz, Radio 1 on 7.74 MHz and Radio 5 on 7.92 MHz.

Log for February

02.02.93: Norwegian PM 5534 test pattern via meteor scatter propagation on channel E3 at 0815h UTC, plus unidentified signals on channel E2. Sporadic-E signals from Hungary were noted between 1145h and 1330h UTC.

13.02.93: Sporadic-E activity at 1235h on channel E3. The unidentified reception consisted of an historical play.

15.02.93: Strong sporadic-E signals from Germany on channel E2 at 2037h UTC.

18.03.93: A small sporadic-E opening from Denmark on channel E3 at 0730h UTC. Also, meteor scatter activity noted on channel R2 at 0750h.

26.02.93: Unidentified sporadic-E signals on R1 at 1900h.

Tropospheric reception from France, Eire, Belgium, Germany and the Netherlands was noted on the following dates during February: 1st, 4th, 5th, 9th, 10th, 13th, 14th and 15th. In addition, Luxembourg and Denmark were logged on the 14th.

Log for March

09.03.93: SVT-1 (Sweden) on channel E6 and SVT-2 E30 via tropospheric propagation.

11.03.93: Unidentified signals on channels E2 and R1 via auroral activity.

14.03.93: Serbia on channel E3 plus unidentified signals on R2 (meteor scatter).

18.03.93: Sporadic-E reception from Germany on channel E2 and Denmark E3.

20.03.93: Unidentified FuBK test pattern on channel E2 via meteor scatter at 0825h.

The DX-TV logs were kindly supplied by the following enthusiasts: Andrew Jackson (Birkenhead), Simon Hamer (New Radnor), Iain Menzies (Aberdeen) and Stephen Michie (Bristol).

1993 Sporadic-E Season

This is now underway and should last from May to September. An in-depth look at sporadic-E reception was featured in the February 1993 issue of *Elektor Electronics*. To briefly recap, throughout the summer, signals can be received in Band I from transmitters located at distances in excess of 1,100 km. The basic equipment required for reception consists of a tuner covering Band-I channels (48-70 MHz) plus an aerial, such as a dipole with a total length of approximately 2.8 metres.

The modified MP3 converters mentioned in the previous column have all been sold, but several readers have been in contact who purchased the basic unit. Even in their original form they are suitable for sporadic-E work, provided they have Band-I coverage. With the original 5.5-MHz ceramic sound filters fitted, the TV sound from most countries in Western Europe will be heard.

Service information

Portugal: Since its launch in mid-1992, RAP International (RTPi) has been broadcasting for 42 hours per week, taking the best Portuguese programmes from among the four RAP channels (RAP-1 and RAP-2 in Portugal, RAP-Madeira and RAP-Azores). In addition, there are regular news programmes and live football coverage. RTPi also produces a daily news magazine that serves as an interface among the many Portuguese communities throughout the world.

France: Canal Plus is gradually introducing a new scrambling system in an attempt to make pirate decoders unusable. The new scrambling system, called 'Syster', has been developed in Switzerland. It is a technically more sophisticated system than 'Discret 1', which was originally adopted for Canal Plus transmissions. It is hoped that the new system will offer greater security, and will be more difficult to 'hack'.

Belgium: The Canal+ programme is now aired from the Leglise transmitter on channels E11 and E63. A colour test card with a small but distinctive 'window' in the centre has been used for recent tests. No identification is shown.

TV systems

During the recent periods of enhanced tropospheric reception conditions, tuning through the UHF band on a normal TV set may have revealed several foreign stations dotted about the band. Given favourable conditions, some of these would be complete with Teletext information. However, the biggest mystery for the viewer is the absence of sound. This is due to the differences in TV systems adopted by various countries, for example, in the UK and Eire the sound carrier sits at 6 MHz above the vision carrier, whereas in countries such as Belgium and Germany the carrier off-set is only 5.5 MHz. In Eastern Europe and the CIS the spacing is 6.5 MHz.

The FM intercarrier sound system is used by every country throughout the world, apart from France and Monaco where AM sound continues to be used. With the intercarrier system, both the sound and vision IF signals are handled by the vision detector, the resultant beat frequency (the frequency difference) being fed into the sound IF stages which respond to either 5.5, 6.0 or 6.5 MHz signals.

The characteristics that make up a TV system can be divided into five main elements: (1) the number of scan lines; (2) positive or negative vision modulation; (3) FM or AM sound; (4) the sound subcarrier off-set; (5) the colour system. Any combination of these can make up a TV system.

Many different systems were originally adopted in Europe. Even during the early eighties there were at least four different line standards in use: 405 by the UK and Eire; 819 by France and Monaco; 525 by the American forces transmitters, and 625 by other countries. Since the closure of the 405-line system in 1985, only 525-line and 625-line systems exist. Transmissions using 819 lines were phased out a number of years ago.

With the exception of France, Monaco and Luxembourg, negative vision modulation is used worldwide. Positive vision modulation was also used by the UK, Eire and Belgium. If such a transmission is received on a 'normal' set, the pictures tend to resemble a black and white photographic negative, i.e., black areas appear white and vice-versa, when viewed on a UK receiver. The synchronization may also be poor due to the incorrect sense of the video detection.

Amplitude modulation (AM) is used for the sound carrier accompanying positive modulated vision signals. The FM intercarrier system is used elsewhere with four different spacings, depending on the system.

PAL and SECAM colour systems are used throughout Europe. SECAM was adopted by Russia, Eastern-bloc countries and France, while PAL was used elsewhere. Since the recent political changes in Eastern Europe, SECAM is gradually being phased out in favour of the PAL system in some countries. Already the Czech and Slovak republics have initiated this change, and the former East German transmitters have radiated PAL for some time.



The station opening caption of the Dutch third network, photographed by David Glenday in Arbroath.

The 'BRT' header information on the PM5544 test pattern as used by the Flemish-speaking networks now reads 'BRTN'. The lower identification 'TV1' or 'TV2' remains unchanged.

United Kingdom: DAB (Digital Audio Broadcasting) test transmissions are due to start in London this summer (they will commence in France during 1994 with ten local programmes in the Paris area). Frequencies around 60 MHz in Band I and 220 MHz in Band III have been chosen, which could present problems for UK DX-ers. The choice of Band I frequencies again demonstrates the irresponsibility shown by the powers-that-be, because it is likely to cause interference to European TV services during periods of Sporadic-E propagation.

Eire: The channels used for RTE-1 and Network-2 transmissions from Kippure have changed. RET-1 has moved from channel H to E, and Network-2 from channel J to H. Channel J is no longer used. The E and H pair of channels are also used by other Irish transmitters such as Achill, Castletownbere, Clencolumcille, Kilmacthomas and Suir

Valley.

A new RTE-1 transmitter at Maghera is now operating on channel E with 100 kW ERP, and it seems likely to replace the existing channel B outlet. Network-2 is already broadcast from the Maghera site on channel E. A similar move to channel H for RTE-1 seems a possibility for the low-power Glanmire relay which currently radiates the first programme on channel C and Network-2 on channel E.

Finland: MTV, which used to provide programmes for the TV1 and TV2 networks, has transferred its output to the commercial TV3 network, which now covers most of the country. The test card is the FuBK with the 'MTV 3' identification.

The TV1 and TV2 networks have recently undergone a complete face-lift because of this move. TV1 is now described as being modern, international and up-to-date; the TV2 network caters for specialist programmes.

Germany: The MDR-3 network is now using the FuBK colour test pattern with the identification 'MDR 3 Dresden'. VOX TV, who were given two terrestrial channels previously occupied by WEST-3, also radiate the FuBK pattern with the identification 'VOX — Koeln'.

This month's service information was kindly supplied by Gösta van der Linden and the Benelux DX club, Netherlands; Bernd Trutenau, Lithuania; Pertti Salonen, Finland; Reflexion Club, Germany; Roger Bunney, UK; Simon Hamer, UK; André Gille, France. Please send any news about DX-TV in your part of the world to: Keith Hamer, 7 Epping Close, Derby DE3 4HR, England.

80C32 COMPUTER APPLICATION NOTES - 3

X2404 EEPROM interfacing to an 8751

Design by Zoran Stojasavljevic

XICOR's X2404 is a 4096-bit serial Electrically Erasable PROM (EEPROM), internally organized as two pages, each containing 256×8 bits. The X2404 features a serial interface and an I2C compatible software protocol that allows it to be operated via a 2-wire bus. The pinning and internal architecture of the IC are given in Fig. 1. The SCL (serial clock) input is used to clock all data into and out of the device. The serial data pin, SDA, is bidirectional, and used to transfer data into and out of the device. SDA is an open-drain output, and may be wire-ORed with any number of open-drain or open-collector outputs to form a bus. Address input A0 is not used by the X2404, although it must be tied to V_{SS} for proper device operation. Address inputs A1 and A2 are used to set the least-significant two bits of the six-bit slave address assigned to the device. The address inputs are static, and should be tied to logic high or low levels, to give one unique address per device.

The circuit diagram in Fig. 2 shows an example application of the X2404 in a 8751 microcontroller driven racing car computer. The functions of this computer are not our prime concern here, hence the following discussion will concentrate mainly on the way the 8751 and the X2404 are set up to communicate properly. The functions of the four push-buttons are:

- S2: adjust clock;
- S3: display max. rpm during race;
- S4: display max. rpm ever.
- S5: reserved.

The hardware implementation of the X2404 is simplicity itself, being essentially restricted to two lines only. In the application circuit, the X2404 records the highest rpm (revolutions per minute) value of the car engine. This is achieved by reducing the ignition pulses to a suitable level, digitizing (Tx), and feeding them to the P3.2 input of the 8751 microcontroller.

X2404 device operation

The X2404 supports a bidirectional, bus oriented protocol. This protocol defines any device that sends data on to the bus as a transmitter, and the receiving device as a receiver. The device

Following the eight instalment '8051/8032 assembler course' featured in last year's issues of *Elektor Electronics*, this column presents design ideas, programming examples and hardware experiments based on and around the popular 80C32 single-board computer. All descriptions are kept as brief as possible to ensure that a wide variety of subjects can be presented. Apart from the knowledge you have hopefully gathered from the assembly language course, you will need the following to get going with the application notes: an 80C32 SBC (with extension board) running the EMON51 system monitor from EPROM, and a PC running the EASM51 assembler. Both programs are contained on the assembler course diskette, no. 1661. This month Zoran Stojasavljevic tells us all about 8751-to-EEPROM interfacing.

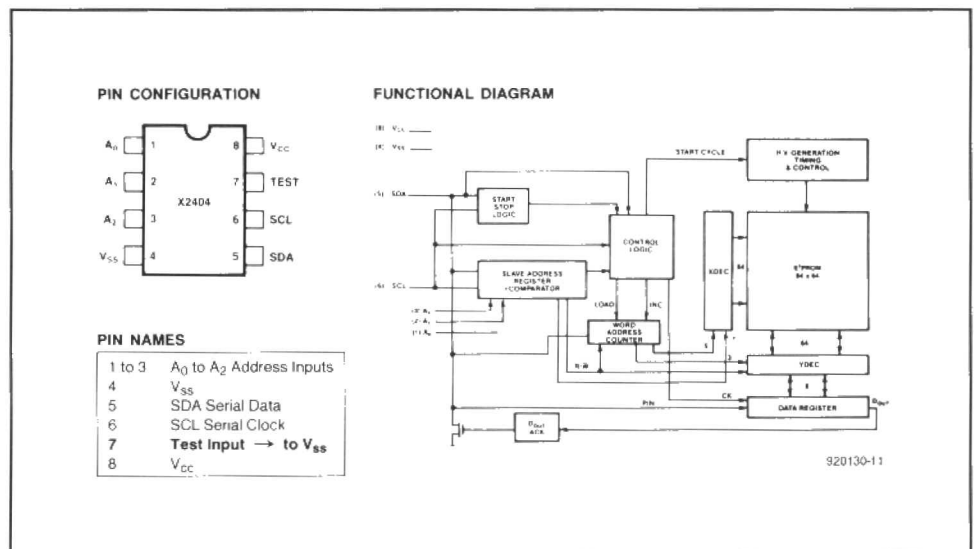


Fig. 1. Pin layout and internal structure of EEPROM X2404.

controlling the data transfer is a master, and the device being controlled is a slave. The master will always initiate data transfers, and provide the clock for both transmit and receive operations. Therefore, the X2404 will be considered a slave in all applications.

Data states on the SDA line can change only when SCL is low. SDA changes during SCL 'high' periods are reserved for indications of start and stop conditions, as illustrated in Fig. 3. All commands are preceded by the start condition, which is a high-to-low transition of SDA when SCL is high. The X2404 continuously monitors the SDA and SCL lines for the start condition, and will not respond to any command until this condition is

satisfied. All communications are terminated by a stop condition, which is a low-to-high transition of SDA when SCL is high. The definitions of the start and stop conditions are illustrated in Fig. 4.

The transmitting device, either a master or a slave, releases the bus after transmitting eight bits. During the ninth clock cycle, the receiver pulls the SDA line low to acknowledge that it received the eight bits of data. The X2404 will always respond with an acknowledge after recognition of a start condition, followed by its slave address. If both the device and a write operation have been selected, the X2404 will respond with an acknowledge on receipt of each subsequent

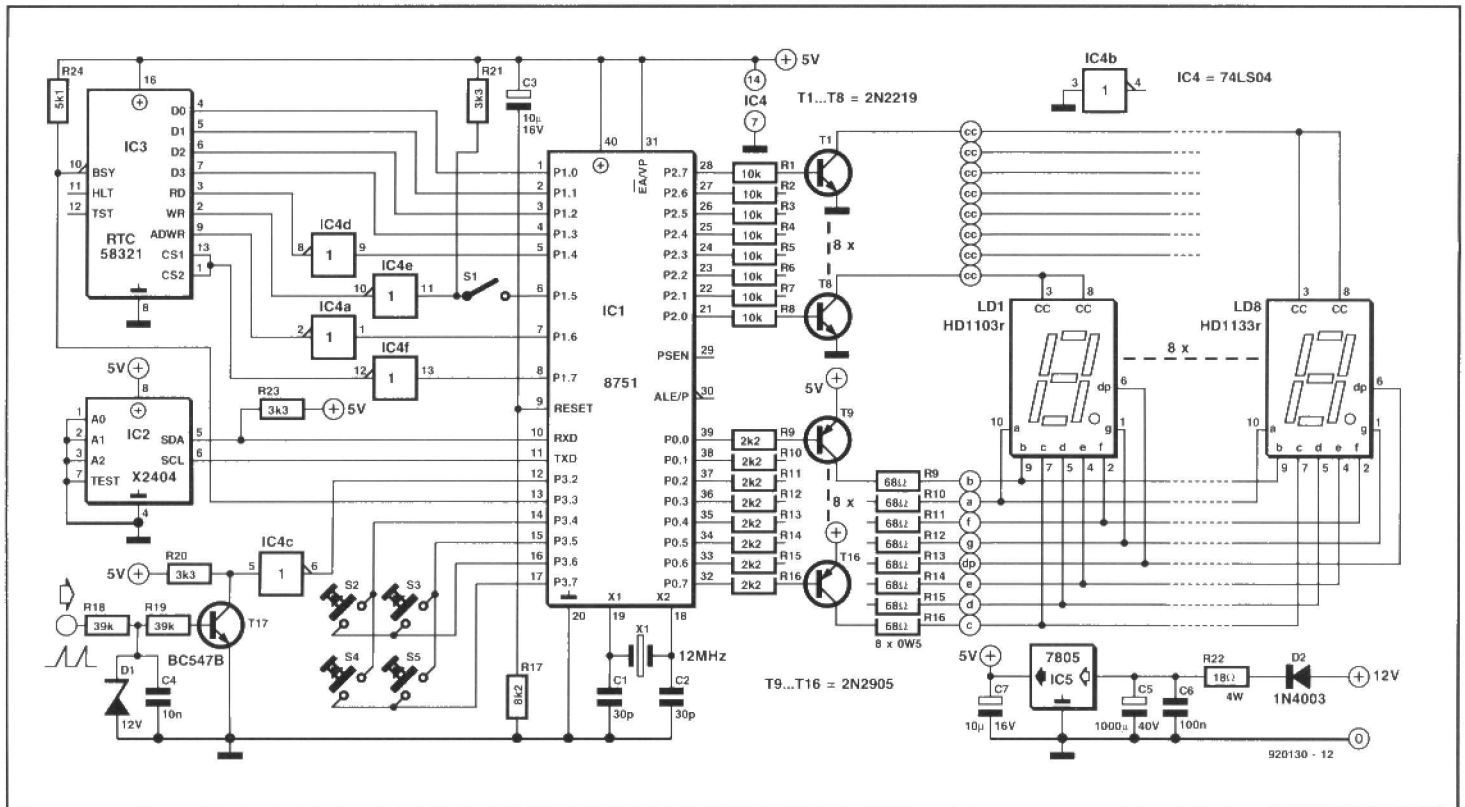


Fig. 2. Application of an X2404 in a car computer based on Intel's 8751 microcontroller. The X2404 serves, among others, to store and retain the highest rpm of the car's engine.

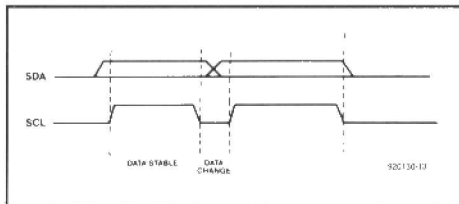


Fig. 3. Clock and data conventions.

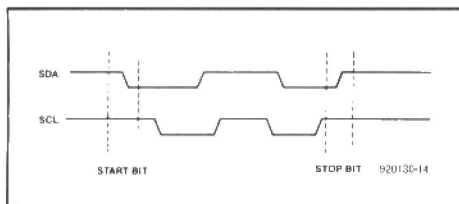


Fig. 4. Definition of start and stop conditions.

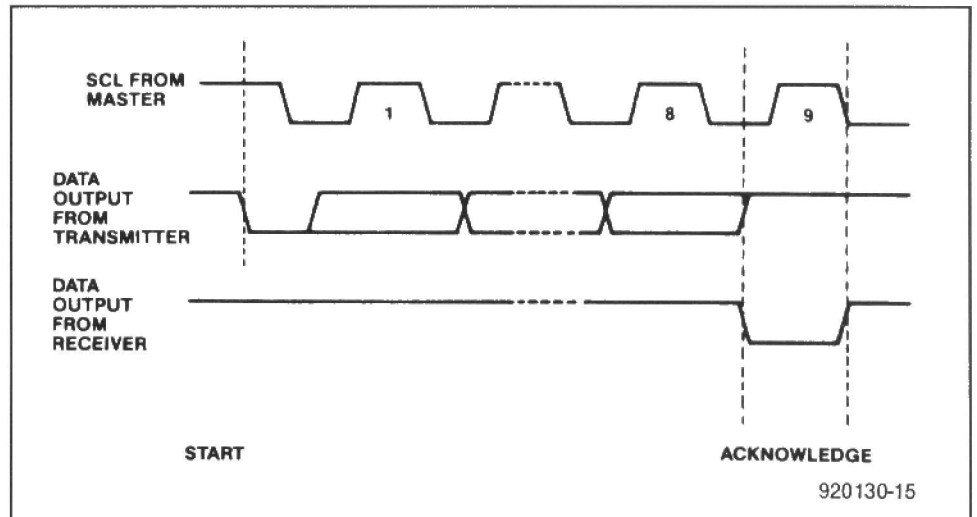


Fig. 5. Response from the receiver.

eight-bit word (Fig. 5). In read mode, the X2404 will transmit eight data bits, release the SDA line, and monitor it for an acknowledge. If an acknowledge is detected and no stop condition is generated by the master, the X2404 will continue to transmit data. If an acknowledge is not detected, the X2404 will terminate further data transmissions, and await the stop condition.

Following a start condition, the bus master must output the address of the slave it is accessing. The most significant four bits of the slave address are the type identifier (see Fig. 6). For the X2404 this is fixed as 1010. The next two bits, A2 and A1, address one of up to four X2404s connected on to the

bus. The next bit, A0, allows the host to toggle between the two 256-word pages contained in the X2404. The last bit in the device address field switches between read (bit=1) and write (bit=0) operations. Following the start condition, the X2404 monitors the SDA bus, comparing the slave address being transmitted with its own address (i.e., four-bit device type and two-bit device number). When the two match, the X2404 generates an acknowledge on the SDA line. Depending on the state of the R/W bit, the device next does a read or a write operation.

Write operations on the X2404 can be divided into two types: byte write and page write. For a byte write opera-

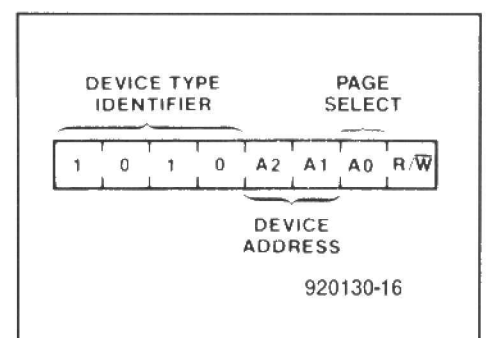


Fig. 6. Address format.

tion (Fig. 7), the X2404 requires a second address field, which forms the word address. This consists of eight

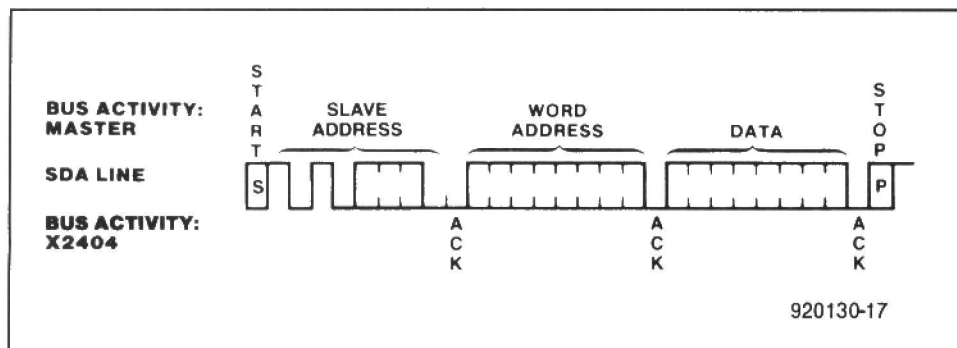


Fig. 7. Byte write operation.

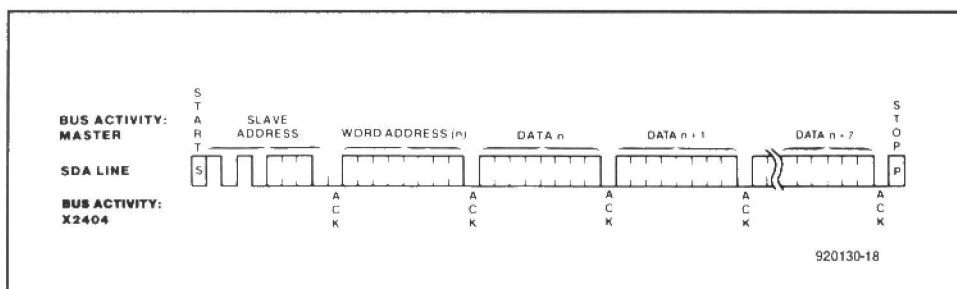


Fig. 8. Page write operation.

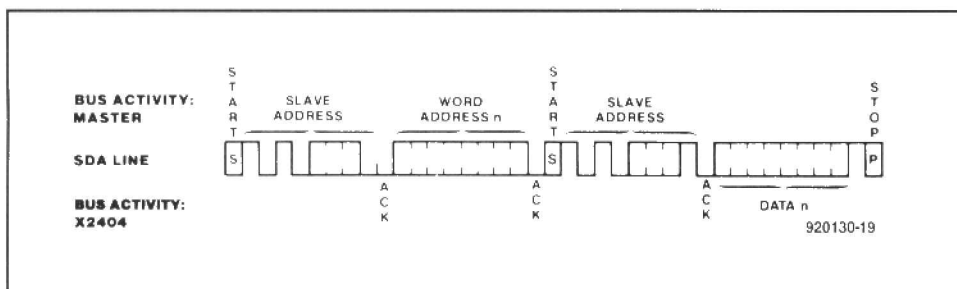


Fig. 9. Random read operation.

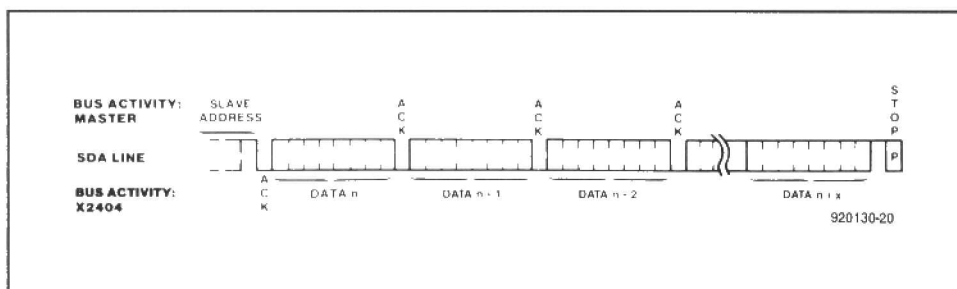


Fig. 10. Sequential read operation.

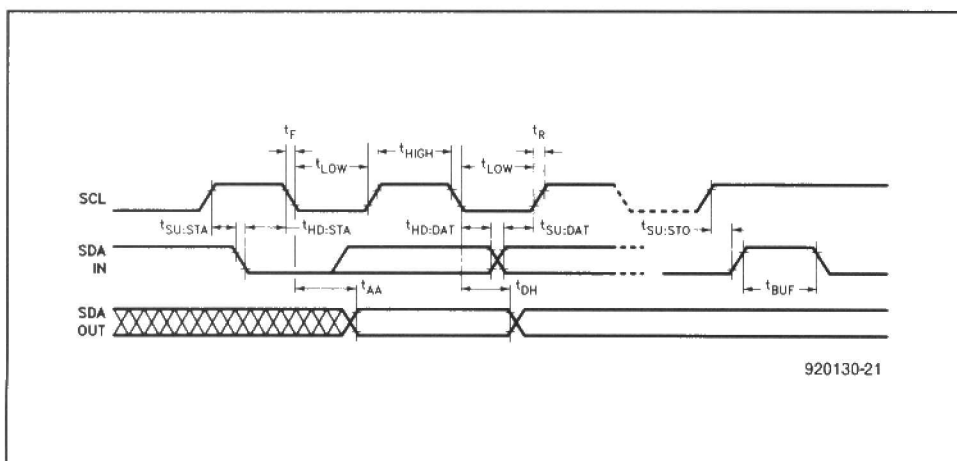


Fig. 11. Control and data line setup times.

bits, and provides access to any one of the 256 words of memory. Upon receipt of the word address, the X2404 responds with an acknowledge, and awaits the next eight bits of data, again responding with an acknowledge. Next, the master terminates the transfer by generating a stop condition, at which time the X2404 starts an internal write cycle to the non-volatile memory. During this write operation, the device disables its inputs, and will not respond to any requests from the master.

Page write operations (Fig. 8) move eight bytes at a time, and are initiated in the same manner as byte write operations. However, instead of terminating the first write cycle after the first data word is transferred, the master can transmit up to seven more words. On receipt of each word, the X2404 will respond with an acknowledge. On receipt of each word, the three low-order address bit are internally increased by one. The high order five bits of the address remain the same. If the master transmits more than eight words before generating the stop condition, the address counter will 'roll over', and the previously stored data will be overwritten. As with the byte write operation, all inputs are disabled until the internal write cycle is completed.

Acknowledge polling can be implemented by making use of the typical 5-ms write cycle time. ACK polling involves issuing the start condition followed by the slave address for a write operation. If the relevant X2404 is still busy with the write operation, it will not return an ACK until this operation is finished, after which the host can proceed with the next read or write operation.

Read operations (Fig. 9) are initiated in the same manner as write operations, with the exception that the R/W bit of the slave address is set to a one. There are three basic read operations: current address read, random read and sequential read.

Random read operations allow the master to access any memory location in a random manner. Prior to issuing the slave address with the R/W bit set to one, the master must perform a 'dummy' write operation. The master issues the start condition, and the slave address followed by the word address it is to read. After the word address acknowledge, the master immediately re-issues the start condition and the slave address with the R/W bit set to one. This will be followed by an acknowledge from the X2404, and then by the 8-bit word. The master does not acknowledge the transfer, but generates a stop condition, so that the X2404 stops transmitting.

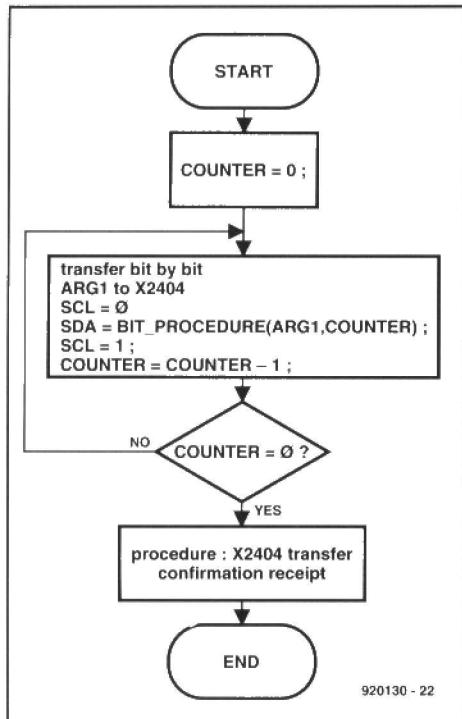


Fig. 12. Flow chart of procedure WRITE_BYTE.

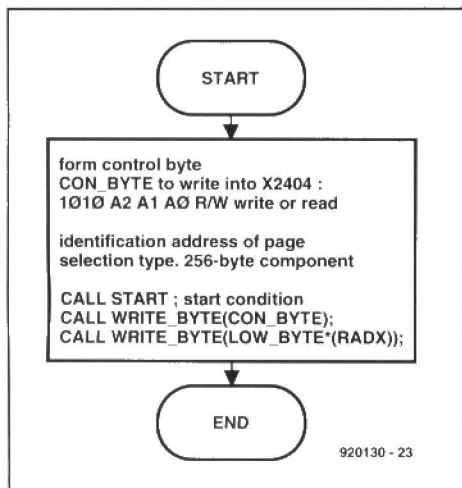


Fig. 13. Flow chart of procedure WRITE_ADDR.

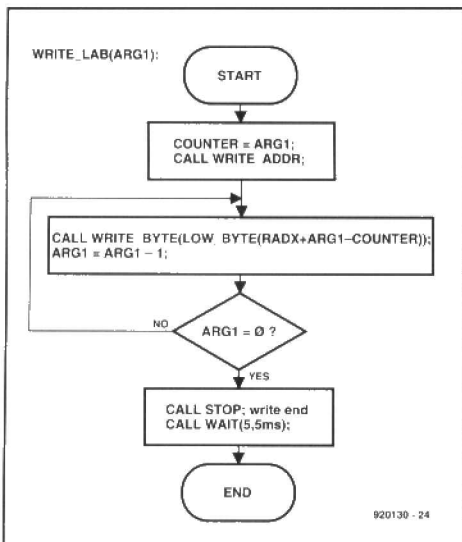


Fig. 14. Flow chart of procedure WRITE LAB.

Sequential read operations can be initiated either as a current address read or a random access read. The first word is transmitted as with the other read modes. However, the master now responds with an acknowledge, indicating that it requires additional data. The X2404 continues to output data for each acknowledge received. The read operation is terminated by the master not responding with an acknowledge, and generating a stop condition.

The data output is sequential, with the data from address N followed by the data from address $N+1$ (Fig. 10). The address counter for read operations increases all eight address bits, allowing the entire memory contents of the current 256-word page to be read serially in one operation. If more than 256 words are read, the counter 'rolls over', and the X2404 continues to output data from the same 256-word page for each acknowledge received.

X2404 control program

The control program written to interface the X2404 to an 8751 is based on the previously discussed device operation and the timing specifications given in Fig. 11. Any transmission to the X2404 requires at least three parameters: (1) the number of bytes to be transferred; (2) the initial EEPROM address to or from which the length data, defined by the first parameter, are transferred; (3) the initial address of the 8751 internal RAM to or from which the length data, defined by the first parameter, are transferred. The following program notations apply:

RADX: Required initial Address for read/write from/to X2404;

RADM: Required initial Address for read/write from/to Microcontroller;

RBN: Required Byte Number for read/write program.

The flow charts in Figs. 12 through 16 illustrate the basic operation of the X2404 control program. The flow charts were used as a starting point for the assembler code written to implement the X2404-to-8751 link. Unfortunately, owing to lack of space, it is not possible to print the assembly listing of the interface program. The program is available on an MS-DOS formatted disk, however, and can be obtained through the Readers Services — the order code is 1891.

Conclusion

The X2404 EEPROM and the software driver developed for it allows an 8051 (or derivate) microcontroller to store a relatively small packet of data that is not lost when the power is switched off. Applications can be found in auto-

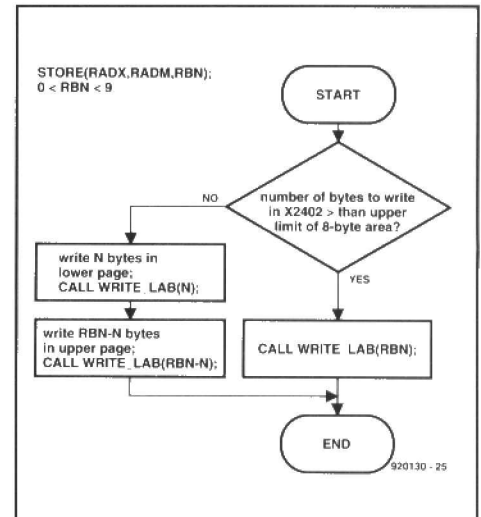


Fig. 15. Flow chart of procedure STORE.

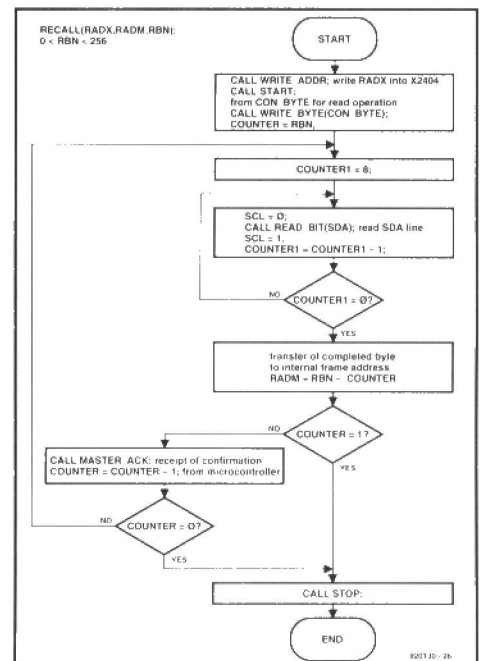


Fig. 17. Flow chart of procedure RECALL.

motive control, test and measurement, and data logging systems. If your application requires more memory space, there are EEPROMs in the X24xx family with a larger capacity, for instance, the X24C16 with a capacity of 2 kBytes, organized as eight pages of 256 bytes each. The software driver described here requires only small changes for use with a variety of serial EEPROMs. ■

Literature:

1. Data Book, Xicor. Xicor Inc., 851 Buckeye Court, Milpitas, California 95035. Telephone (408) 432-8888. Fax: (408) 432-0640.
2. Embedded Controller Handbook, Intel Corp.

Note:

Figures 1, and 3 through 11, and extracts from X2404 datasheets reproduced by courtesy of Xicor, Inc.

PRODUCT OVERVIEW

JUNE 1993

ELEKTOR ELECTRONICS

A number of projects carried in *Elektor Electronics* are supported by ready-made printed-circuit boards (PCBs), self-adhesive front panel foils, ROMs, EPROMs, PALs, GALs, microcontrollers and diskettes, which may be ordered through our Readers Services using the order form printed every month opposite the Readers Services page.

The list printed here is complementary to the shorter one opposite the Readers Services page elsewhere in this issue. This two-page overview of all currently available products is regularly updated and appears in the March, June, September and December issues of *Elektor Electronics*.

Items marked with a dot (●) following the product number are in limited supply only, and their availability can not be guaranteed by the time your order is received.

Items not listed here or on this month's Readers Services page are not available.

The artwork for making PCBs which are not available ready-made through the Readers Services may be found in the relevant article (from March 1990 onwards).

Prices and item descriptions subject to change. Prices can be confirmed on request at the time of ordering. Sterling (£) prices are inclusive of VAT at 17.5%.

PRINTED-CIRCUIT BOARDS

1986

APRIL 1986
Portable mixer 86012-1 ● 6.25 12.50

MAY 1986
Printer buffer 85114-1 ● 13.80 27.60
85114-2 ● 5.95 11.90

JUNE 1986
Rain gauge 86068 ● 4.25 8.50

SEPTEMBER 1986
RTTY interface 86019 ● 8.95 17.90
Universal peripheral equipment 86090-1 ● 9.35 18.70

OCTOBER 1986
IDU for satellite TV reception 86082-1 ● 14.80 29.60
Computerscope 86083 ● 28.90 57.80
9968-5 2.40 4.80

NOVEMBER 1986
Top-of-the-range preamplifier 86111-3A 8.10 16.20
86111-1 12.20 24.40

DECEMBER 1986
Temperature probe for DMM 86022 ● 1.25 2.50

1987

JANUARY 1987
Top-of-the-range preamplifier 86111-2 ● 26.45 52.90

FEBRUARY 1987
Electron ROM card 86089 ● 6.70 13.40

MARCH 1987
MSX EPROMmer 87002 ● 11.15 22.30

APRIL 1987
Facsimile interface 87038 ● 10.40 20.80

MAY 1987
MIDI signal distribution 87012 ● 8.70 17.40

OCTOBER 1987
Low-noise microphone preamplifier 87058 ● 4.05 8.10

NOVEMBER 1987
SSB receiver for 80m and 20m 87051 ● 17.35 34.70
BASIC computer 87192 23.80 47.60
Dimmer for inductive loads 87181 ● 7.05 14.10

1988

JANUARY 1988
Stereo limiter 87168 ● 8.50 17.00

FEBRUARY 1988
Infra-red headphones 87640 ● 7.20 14.40

MARCH 1988
Computer-controlled

PRINTED-CIRCUIT BOARDS

slide fader 87259 ● 18.80 37.60
Low-noise preamplifier for FM receivers 880041 ● 7.65 15.30
Signal divider for satellite TV receivers 880067 ● 5.90 11.80

APRIL 1988
Fuzz unit for guitars 87255 ● 7.65 15.30
Active loudspeaker system 880030 ● 8.80 17.60

MAY 1988
Plotter 87167 ● 13.50 27.00

JUNE 1988
Wideband active aerial for SW receivers 880043-1 ● 7.05 14.10
880043-2 ● 5.60 11.20

JULY/AUGUST 1988
I/O extension card for IBM PCs 880038 33.60 67.20
Frequency read-out for SW receivers 880039 ● 21.60 43.20

OCTOBER 1988
Centronics interface for slide fader 880111 ● 9.10 18.20
Preamplifier for purists 880132-1 ● 6.95 13.90
880132-2 ● 14.40 28.80
Peripheral modules for BASIC computer 880159 ● 5.90 11.80

NOVEMBER 1988
Bus interface for hi-res LCD screens 880074 ● 19.70 39.40
LFA-150 — a fast power amplifier 880092-1 ● 9.95 19.90
880092-2 ● 9.20 18.40
Harmonic enhancer 880167 ● 7.40 14.80
Portable MIDI keyboard 880168 ● 9.20 18.40

DECEMBER 1988
LFA-150 — a fast power amplifier 880092-3 ● 7.50 15.00
CVBS-to-TTL adaptor 880098 ● 5.70 11.40
Colour test pattern generator 880130 ● 15.65 31.30
Autonomous I/O controller 880184 ● 18.00 36.00
Pitch control for CD players 880165 ● 13.50 27.00

1989

JANUARY 1989
Fax interface for Atari ST and Archimedes 880109 8.65 17.30
MIDI control unit 880178-1 10.65 21.30
880178-2 7.80 15.60

Low-budget capacitance meter UPBS-1 2.30 4.60

FEBRUARY 1989
Digital Model Train 87291-1 4.95 9.90
Touch key organ 886077 11.80 23.60
VHF receiver 886127 8.75 17.50

MARCH 1989
Power line modem 880189 7.15 14.30
Centronics buffer 890007-1 23.05 46.10
890007-2 2.55 5.10
890007-3 9.80 19.60

APRIL 1989
Digital Model Train 87291-2/3 5.05 10.10
Function generator UPBS-1 2.30 4.60

PRINTED-CIRCUIT BOARDS

Triplet 890013-1 7.80 15.60
890013-2 8.00 16.00
Multi-point IR control 890019-1 4.05 8.10
890019-2 4.75 9.50

MAY 1989
RDS decoder 880209 ● 5.30 10.60
Digital Model Train (4) 87291-4 6.15 12.30
Analogue multimeter 890035 14.70 29.40
DTMF system decoder 890060 7.65 15.30
Sine-wave converter UPBS-1 2.30 4.60
S-VHS-to-RGB converter ELV project

JUNE 1989
8-digit frequency meter 880128 13.50 27.00
Echo unit 880043-2 ● 5.60 11.20

JULY/AUGUST 1989
MIDI keyboard interface decoder board 890105-1 8.25 16.50
Tracking tester ELV project
Floppy disk monitor 890078 5.00 10.00
Function generator UPBS-1 2.30 4.60

SEPTEMBER 1989
Digital Model Train 87291-6 7.85 15.70
Stereo viewer 890044 6.55 13.10
Centronics monitor 890123 6.45 12.90
Resonance meter 886071 4.60 9.20

OCTOBER 1989
Logic analyser with Atari ST 890126 6.15 12.30
CD error detector 890131 7.05 14.10
RGB-to-CVBS converter ELV project

NOVEMBER 1989
Digital Model Train (8) 87291-5 51.10 102.20

DECEMBER 1989
Digital Model Train 87291-7 10.30 20.60
EPROM simulator 890166 11.75 23.50
Hard disk monitor 890186 12.95 25.90
IC tester ELV project
LF/HF signal tracer 890183 9.40 18.80
Solid-state preamp 890170-1* 13.80 27.60
890170-3* 10.60 21.20

1990

JANUARY 1990
Video mixer (1) 87304-1 32.00 64.00
Mini EPROM programmer 890164 8.25 16.50
All solid-state preamplifier 890170-2* 18.50 37.00
Simple AC milli-voltmeter 900004 ● 7.65 15.30
1 GHz frequency meter card for PCs 894110 25.55 51.10

*The four PCBs required for the preamplifier (2 × 890170-1; 1 × 890170-2 and 1 × 890170-3) are available as a package, ref. 890170-9, at a discounted price of £48.15 (US\$96.30).

FEBRUARY 1990
Initialisation aid for printers 900007 16.75 33.50
Digital Model Train (11) 87291-8 5.30 10.60
Reflex MW AM receiver UPBS-1 2.30 4.60
Video mixer (2) 87304-2 19.10 38.20
Capacitance meter 900012 ● 8.50 17.00

PROJECTS

MARCH 1990
Audio/video modulator ELV project
Digital model train (12) 87291-9 4.10 8.20
IC monitor 896140 8.80 17.60
Power line monitor 900025 ● 5.60 11.20
Video mixer (3) 87304-3 41.70 83.40

APRIL 1990
BBD sound effects unit 900010 ● 9.10 18.20
Digital model train (13) 87291-10 4.70 9.40
Q meter 900031 ● 7.05 14.10
RS-232 splitter 900017-1 8.50 17.00
900017-2 5.30 10.60
Wiring allocation tester ELV project

MAY 1990
Acoustic temperature monitor UPBS-1 2.30 4.60
Budget sweep/function generator 900040 ● 8.25 16.50
Centronics ADC/DAC 900037D 17.90 35.80
PC servicing card ELV project
Transistor characteristic plotting 900058 5.60 11.20

JUNE 1990
Electronic load simulator 900042 ● 14.10 28.20
MIDI master keyboard Doepfer Elektronik
Mini EPROM viewer 900030 21.15 42.30
Power zener diode UPBS-1 2.30 4.60
Remotely controlled stroboscope ELV project

JULY/AUGUST 1990
Battery tester ELV project
Compact 10A power supply 900045 13.50 27.00
Intermediate projects UPBS-1 2.30 4.60
Mini FM transmitter* 896118 5.00 10.00
Sound demodulator for satellite-TV receivers 900057 4.40 8.80
Audio power indicator 904004 ● 4.40 8.80
Four-monitor driver for PCs 904067 ● 6.15 12.30
* can not be supplied to readers in the UK

SEPTEMBER 1990
High-current h_{FE} tester 900078 ● 6.45 12.90
Infra-red remote control 904085/86 7.95 15.90
Sound generator ELV project

OCTOBER 1990
 μ P-controlled telephone exchange 900081 21.15 42.30
S-VHS/CVBS-to-RGB converter 900055 ● 14.40 28.80

NOVEMBER 1990
400-watt laboratory PSU 900082 ● 12.95 25.90
Active mini subwoofer 900122-1 ● 7.05 14.10
Dubbing mixer EV7000 ELV project
Medium-power audio amplifier 900098 10.60 21.20
Programmer for the 8751 900100 8.25 16.50
PT100 thermometer 900106 ● 5.90 11.80

DECEMBER 1990
Active mini subwoofer 900122-2 ● 6.15 12.30
MilliOhmmeter 910004 ● 5.90 11.80
Phase check for audio systems 900114-1/2 ● 9.40 18.80
PC-controlled Video-text decoder (1) ELV project
Signal suppressor for all-solid state preamp 904024 ● 4.40 8.80

1991

JANUARY 1991
Logic analyser (1):
- Busboard 900094-4 ● 10.60 21.20
PC controlled Video-text decoder (2) ELV project
SWR meter 900013 3.55 7.10

FEBRUARY 1991
Logic analyser (2):
- RAM board 900094-2 ● 18.50 37.00
- Probe board 900094-3 ● 5.00 10.00
Multifunction measurement card for PCs 900124-1 28.20 56.40
MIDI-to-CV interface Doepfer Elektronik
RDS decoder:
- demodulator board 880209 ● 5.30 10.60
- processor board 900060 ● 7.65 15.30

MARCH 1991
The complete preamplifier:
- input board 890169-1 26.10 52.20
- main board 890169-2 39.35 78.70
Electronic exposure timer 900041 ● 10.85 21.70
PC-controlled weather station (1) 900124-3 4.40 8.80
2-m band converter 900006-1 5.00 10.00

APRIL 1991
Logic analyser (3):
- control board 900094-5 ● 18.50 37.00
MIDI programme changer 900138 ● 6.75 13.50
8-bit I/O for Atari 910005 12.35 24.70

Project	No.	Price (£)	Price (US\$)
6-m band transverter	910010	11.45	22.90
Wattmeter:			
- meter board	910011-1	6.45	12.90
- display board	910011-2	4.10	8.20
Moving-coil (MC) preamplifier	910016 ●	10.60	21.20
Dimmer for halogen lights:			
- transmitter	910032-1 ●	4.10	8.20
- receiver	910032-2 ●	4.40	8.80

PC-controlled semi-conductor tester	ELV project		
MAY 1991			
80C32/8052 Computer	910042	12.05	24.10
Battery tester	906056	4.10	8.20
Laser (1)	ELV project		
Moving-magnet (MM) preamplifier	900111 ●	6.75	13.50
Universal I/O interface for IBM PCs	910046	10.85	21.70

JUNE 1991			
Universal battery charger	900134	9.40	18.80
Logic analyser - 4			
- power supply board	900094-7 ●	8.80	17.60
- Atari interface	900094-6 ●	12.65	25.30
- IBM interface	900094-1 ●	14.40	28.80
Digital phase meter (set of 3 PCBs)	910045-1/2/3	26.15	52.30
Light transceiver	UPBS-1	2.30	4.60
Variable AC PSU	900104 ●	6.15	12.30
Light switch w. TV IR r/c	910048	5.60	11.20
RTC for Atari ST	910006	6.15	12.30
Stepper motor board - 1:			
- PC insertion card	910054-1	29.10	58.20

JULY/AUGUST 1991			
Multifunction I/O for PCs	910029	24.40	48.80
B/W video digitizer	910053	22.60	45.20
Stepper motor board - 2:			
- power driver board	910054-2	28.50	57.00
Laser - 3	ELV project		
LED voltmeter	914005 ●	5.60	11.20
Wien bridge	914007 ●	4.10	8.20
Angled bus extension card for PCs	914030 ●	12.05	24.10
Sync separator	914077 ●	4.40	8.80

SEPTEMBER 1991			
Peak indicator for loud-speakers	ELV project		
Timecode interface for slide control:			
- main board	910055	24.40	48.80
- display board	87291-9a	4.10	8.20
Asymm-symm converter	910072	5.60	11.20

OCTOBER 1991			
PC-controlled weather station (2)	900124-2	3.80	7.60
Digital function generator			
- main board	910077-1	21.75	43.50
- display board	910077-2	12.65	25.30
Audio spectrum shift encoder/decoder	910105	10.35	20.70

NOVEMBER 1991			
Relay card for universal I/O interface	910038	12.95	25.90
Dissipation limiter	910071	4.40	8.80
Digital function generator			
- sine converter	910077-3	15.00	30.00
- R/T converter	910077-4	12.35	24.70
Class-A power amplifier (1):			
880092-1	9.95	19.90	
880092-2	9.05	18.10	
Timer for CH systems	UPBS-2	3.80	7.60

DECEMBER 1991			
Class-A power amplifier (2):			
880092-3	7.50	15.00	
880092-4	7.60	15.20	
Economy power supply	910111 ●	9.40	18.80
µP programmable filters	910125	6.75	13.50
Amiga mouse/joystick switch	914078	4.10	8.20
Safe solid-state relay	914008 ●	3.80	7.60
Slave mains on/off control Mark-2	914072 ●	6.45	12.90
Wideband antenna amplifier	ELV project		

1992

JANUARY 1992			
CD player	910146	8.25	16.50
Fast precise thermometer	910081	8.50	17.00
Low-frequency counter			
- input board	910149-1	5.00	10.00
- display board	910149-2	6.45	12.90
Mini Z80 system	910060	10.60	21.20
Prototyping board for IBM PCs	910049	21.15	42.30
Universal RC5 code infra-red receiver	910137	4.70	9.40
PC-controlled weather station (3)	900124-5	10.00	20.00

FEBRUARY 1992			
Audio/video switching unit	910130	11.75	23.50
I ² C interface for PCs	910131-1	14.40	28.80
Measurement amplifier	910144	13.50	27.00
Mini square wave generator	910151	5.30	10.60

Project	No.	Price (£)	Price (US\$)
RAM extension for mini Z80 system	910073	2.35	4.70
Switch-mode power supply	920001	4.40	8.80

MARCH 1992			
8751 emulator	920019	12.05	24.10
A-D/D-A and I/O for I ² C bus	910131-2	6.15	12.30
AF drive indicator	920016	5.60	11.20
Centronics line booster	910133	5.90	11.80
FM tuner (tuner board)	920005	21.15	42.30
LC meter	920012	8.80	17.60
MIDI optical link	920014	6.15	12.30

APRIL 1992			
80C32 SBC extension	910109	13.50	27.00
2-metre FM receiver	910134	10.30	20.60
Comb generator	920003	8.50	17.00
AD232 converter	920010	12.35	24.70
Automatic NiCd charger	UPBS-1	2.30	4.60
LCD for L-C meter	920018	4.70	9.40
Multi-ohm meter adaptor	920020	4.40	8.80

MAY 1992			
1.3-GHz prescaler	914059	5.00	10.00
Compact mains supply	920021	7.35	14.70
FM tuner - 3 (PSU)	920005-2	8.80	17.60
GAL programmer	920030	11.15	22.30
NICAM decoder	920035	15.00	30.00

JUNE 1992			
4-Megabyte printer buffer	910110	18.80	37.60
Audio-video processor - 2	ELV project		
I ² C display	920004	4.70	9.40
FM tuner - 4:			
- mode control board	920005-3	5.60	11.20
- synthesizer board	920005-5	10.85	21.70
Guitar tuner	920033	10.00	20.00
Multi-purpose Z80 card	920002	20.25	40.50

JULY 1992			
12VDC to 240VAC inverter			
- main board	920039-1	11.15	22.30
- power board	920039-2	6.45	12.90
Audio DAC - 1	920063-1	8.50	17.00

Optocoupler for universal PC I/O bus	910040	12.95	25.90
Audio-video processor - 3	ELV project		
FM tuner - 5:			
- keyboard/display	920005-4	14.40	28.80
- S-meter	920005-6	3.80	7.60
RS232 quick tester	920037	5.00	10.00

<i>Small projects:</i>			
Water pump control for solar power system	924007	7.35	14.70
Simple power supply	924024	5.00	10.00
Wideband active telescopic antenna	924102	3.25	6.50

SEPTEMBER 1992			
EPROM emulator - II	910082	10.00	20.00
Audio/video processor - 4	ELV project		
Audio DAC - 2	920063-2	18.80	37.60

OCTOBER 1992			
Audio DAC - 3	920063-3	26.45	52.90
Mains sequencer	920013	17.35	34.70
Wideband active antenna	924101	3.25	6.50
RDS demodulator	880209 ●	5.30	10.60

NOVEMBER 1992			
Printer sharing unit	920011	14.70	29.40
Sound sampler for Amiga	920074	6.75	13.50
Difference thermometer	920078	5.30	10.60
Low-power TTL-to-RS232 interface	920127	3.55	7.10

DECEMBER 1992			
Digital audio/visual system (incl. EPROM 6171)	920022-1	34.10	68.20
1.2 GHz multifunction frequency meter (incl. EPROM 6141)	920095-1	29.40	58.80
Output amplifier for ribbon loudspeakers	920135-1	19.40	38.80
	920135-2	7.95	15.90
Peak-delta NiCd charger	920147	4.10	8.20
IDC-to-box header adaptor	924049	6.45	12.90
Mini keyboard for Z80	924047	12.35	24.70
80C552 µP system	924071	20.00	40.00
Mains power-on delay	924055	6.45	12.90

For January to June 1993 items see page 70 of this issue.

ROMS — EPROMS — PALS — GALS — MICROCONTROLLERS

Article/Project	Issue	Order code	Description	Price (£)	Price (US\$)
<i>For pre-1989 project EPROMs see the December 1992 Product Overview or contact our Dorchester office</i>					
Multifunction measurement card for PCs	2/91	561	1 × 16L8	10.30	20.60
MIDI control unit	1/89	570	1 × 27C64	11.75	23.50
The digital model train series	5/72	572	1 × 2764	11.75	23.50
Darkroom clock	5/83	583	1 × 27128	10.85	21.70
Video mixer	3/90	5861	1 × 2764	11.75	23.50
Four-sensor sunshine recorder	6/90	5921	1 × 27128	11.75	23.50
µP-controlled telephone exchange	10/90	5941	1 × 27128	15.30	30.60
RDS decoder	2/91	5951	1 × 2764	15.30	30.60
MIDI programme changer	4/91	5961	1 × 2764	15.30	30.60
Logic analyser (series)			see under DISKETTES below		
Logic analyser (IBM interface)	6/91	5971	1 × PAL 16L8	8.25	16.50
MIDI-to-CV interface	2/91	5981	1 × 2764	15.30	30.60
Multifunction I/O card for PCs	7/8/91	5991	1 × PAL 16L8	8.25	16.50
Amiga mouse/joystick switch	12/91	6001	1 × GAL 16V8	8.25	16.50
Stepper motor board	6/91	6011	1 × PAL 16L8	8.25	16.50
8751 emulator (incl. system disk 5.25 in.)	3/92	6051	1 × 27C64	29.40	58.80
EMON51 (incl. course disk 1661)	(series)	6061	1 × 27256	20.00	40.00
Connect 4	12/91	6081	1 × 2764	15.30	30.60
EMON51 (incl. course disk 1681)	(series)	6091	1 × 27256	20.00	40.00
FM tuner	7/92	6101	1 × 27C256	20.00	40.00
Multi-purpose Z80 card: GAL set	6/92	6111	2 × GAL 16V8	11.15	22.30
Multi-purpose Z80 card: BIOS	6/92	6121	1 × 27128	15.30	30.60
TV test pattern generator (80C32 SBC)	3/93	6151	1 × 27256	15.30	30.60
1.2 GHz multifunction frequency meter	12/92	6141	1 × 27C256	11.45	22.90
Digital audio/visual system	12/92	6171	1 × 27C256	10.30	20.60
Digital audio/visual system (software package)	2/93	6181	EPROM, GALs and disk	30.50	61.00
PAL test pattern generator	1/93	6211	1 × GAL 20V8	9.40	18.80
Watt-hour meter	2/93	6241	1 × 27256	10.00	20.00
8751 programmer	11/90	7061	1 × 8751	46.40	92.80

DISKETTES

Article/Project	Issue	Order code	Disk size	Price (£)	Price (US\$)
<i>For pre-1990 project diskettes see the December 1992 Product Overview or contact our Dorchester office</i>					
Digital model train (series)	109		5.25-inch	6.75	13.50
FAX interface for IBM PCs	6/90	119	5.25-inch (2 x)	8.25	16.50
EPROM emulator II	9/91	129	5.25-inch	6.75	13.50
RS-232 splitter	4/90	1411	5.25-inch	6.75	13.50
Centronics ADC/DAC	5/90	1421	5.25-inch	6.75	13.50
Transistor characteristic plotting (Atari ST) (for monochrome systems only)	5/90	1431	3.5-inch	7.65	15.30
ROM-copy for BASIC computer	9/90	1441	5.25-inch	7.65	15.30
Multifunction measurement card (MMC) for PCs	2/91	1461	5.25-inch	7.65	15.30
8751 programmer	11/90	1471	5.25-inch	7.65	15.30
PT100 thermometer	11/90	1481	5.25-inch	7.65	15.30
Logic analyser: IBM software & GAL IC	7/8/91	1491	5.25-inch	19.40	38.80
Logic analyser: Atari software & GAL IC	7/8/91	1501	3.5-inch	19.40	38.80
Plotter driver (D. Sijtsma)	9/91	1541	5.25-inch	11.15	22.30
PC-controlled weather station (3)	1/92	1641	5.25-inch	7.65	15.30
8-bit I/O interface for Atari ST	4/91	1571	3.5-inch	7.65	15.30
Tektronix/Intel file converter	4/91	1581	5.25-inch	7.65	15.30
B/W video digitizer for Archimedes	7/8/91	1591	3.5-inch	11.15	22.30
Timecode interface for slide controller	9/91	1611	5.25-inch	7.65	15.30
Real-time clock for Atari ST	6/91	1621	3.5-inch	7.65	15.30
24-bit colour extension for video digitizer	11/91	1631	3.5-inch	11.15	22.30
8051/8032 assembler course (IBM version)	(series)	1661	5.25-inch	7.65	15.30
A-D/D-A and I/O for I ² C bus	3/92	1671	5.25-inch	7.65	15.30
8051/8032 assembler course (Atari version)	series	1681	3.5-inch	7.65	15.30
AD232 converter	4/92	1691	5.25-inch	7.65	15.30
GAL programmer (upgrade: June 1993)	5/92 & 6/93	1701	5.25-inch (3 x)	11.15	22.30
Multi-purpose Z80 card	6/92	1711	5.25-inch	7.65	15.30
Pascal routines for MMC for PCs	10/92	1751	5.25 inch	9.70	19.40
Speech/sound memory	12/92	1771	5.25 inch	7.65	15.30
Infra-red receiver and DTMF decoder for 80C32 single-board computer	3 & 4/93	1791	5.35-inch	7.50	15.00
I ² C opto/relay card	2/93	1821	5.25 inch	7.65	15.30
Video digitizer for PCs	4/93	1823	5.25 inch	14.50	29.00
Philips preamplifier	5/93	1861	5.25 inch	8.50	17.00
GAL programmer (excl. Opal Jr. disks)	6/93	1881	5.25 inch	10.75	21.50

SELF-ADHESIVE FRONT PANEL FOIL

READERS SERVICES

Except in the USA and Canada, all orders, except for subscriptions and past issues (for which see below), must be sent BY POST to our Dorchester office using the appropriate form opposite. Please note that we can not deal with PERSONAL CALLERS, as no stock is carried at the editorial and administrative office.

Readers in the USA and Canada should send orders, except for subscriptions (for which see below), to Old Colony Sound Lab, Peterborough, whose full address is given on the order form opposite. All US\$ prices are postpaid to customers in the fifty states except for books. Please add \$2.00 for the first book and 75¢ for each additional book ordered. Canadians please add US\$4.50 for the first book, and 75¢ for each additional one. Canadians may expect Canadian duty charges on shipments of any items except books.

All other customers must add postage and packing charges for orders up to £25.00 as follows: UK and Eire £1.75; surface mail outside UK £2.25; Europe (airmail) £2.75; outside Europe (airmail) £3.50. For orders over £25.00, but not exceeding £100.00, these p&p charges should be doubled. For orders over £100.00 in value, p&p charges will be advised.

SUBSCRIPTIONS & PAST ISSUES

Subscriptions and past issues, if available, should be ordered from **Worldwide Subscription Service Ltd, Unit 4, Gibbs Reed Farm, Pashley Road, TICEHURST TN5 7HE, England**. For subscriptions, use order form opposite. Prices of past issues, including postage for single copies are £2.50 (UK and Eire); £2.80 (surface mail outside UK); £3.00 (air mail Europe); and £3.75 (airmail outside Europe).

PAST ARTICLES

Photocopies of articles from January 1978 onwards can be provided, postage paid, at £1.75 (UK and Eire), £1.90 (surface mail outside UK), £2.25 (airmail Europe), or £2.50 (airmail outside Europe). In case an article is split into instalments, these prices are applicable **per instalment**. Photocopies may be ordered from our editorial and administrative offices.

COMPONENTS

Components for projects appearing in *Elektor Electronics* are usually available from appropriate advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. It should be noted that the source(s) given is (are) not exclusive — other suppliers may also be able to help.

BOOKS

The following books are currently available; these may be ordered from certain bookshops, Old Colony Sound Lab (USA and Canadian readers only), or direct from our Dorchester office.

301 Circuits.....	£8.95.....	\$12.50
302 Circuits.....	£8.95.....	\$12.50
303 Circuits.....	£9.95.....	\$15.90
304 Circuits.....	£10.95.....	\$19.95
Microprocessor Data Book.....	£9.95.....	\$17.90
Data Sheet Book 2.....	£8.95.....	\$16.50
Data Book 3: Peripheral Chips.....	£9.95.....	\$17.95
Data Book 4: Peripheral Chips.....	£9.95.....	\$17.95
Data Book 5: Application Notes.....	£9.95.....	\$17.95

SHELF BOX

Elektor Electronics shelf box.....	£2.95.....	\$6.00
------------------------------------	------------	--------

FRONT PANELS

PROJECT	No.	Price (£)	Price (US\$)
Timecode interface	910055-F	8.80	17.60
Digital function generator	910077-F	10.60	21.20
4-Megabyte printer buffer	910110-F	11.45	22.90
Economy PSU	910111-F	10.60	21.20
CD Player	910146-F	12.05	24.10
Measurement amplifier	910144-F	8.80	17.60
FM tuner	920005-F	13.20	26.40
4MB printer buffer card	920009-F	8.25	16.50

PROJECT	No.	Price (£)	Price (US\$)
LC meter	920012-F	11.45	22.90
Guitar tuner	920033-F	8.80	17.60
NICAM decoder	920035-F	8.25	16.50
12VDC to 240VAC inverter	920038-F	16.15	32.30
Audio DAC	920063-F	10.00	20.00
Dig. audio/visual system	920022-F1	10.00	20.00
	920022-F2	19.40	38.80
	920022-F3	28.80	57.60
1.2 GHz multifunction frequency meter	920095-F	13.80	27.60
U2400B NiCd battery charger	920098-F	8.75	17.50
Workbench PSU	930033-F	17.00	34.00
Inexpensive phase meter	930046-F	17.25	34.50

EPROMS / PALS / MICROCONTROLLERS

Multifunction measurement card for PCs (1 × PAL16L8)	561	10.30	20.60
Video mixer (1 × 2764)	5861	11.75	23.50
RDS decoder (1 × 2764)	5951	15.30	30.60
MIDI programme changer (1 × 2764)	5961	15.30	30.60
Logic analyser (IBM interface) (1 × PAL 16L8)	5971	8.25	16.50
MIDI-to-CV interface	5981	15.30	30.60
Multifunction I/O for PCs (1 × PAL 16L8)	5991	8.25	16.50
Amiga mouse/joystick switch (1 × GAL 16V8)	6001	8.25	16.50
Stepper motor board - 1 (1 × PAL 16L8)	6011	8.25	16.50
4-Megabyte printer buffer (1 × 2764)	6041	15.30	30.60
8751 emulator			
incl. system disk (MSDOS)	6051	29.40	58.80
Connect 4 (1 × 27C64)	6081	15.30	30.60
EMON51 (8051 assembler course) (1 × 27256 + disk 1661)	6061	20.00	40.00
EMON51 (8051 assembler course) (1 × 27256 + disk 1681)	6091	20.00	40.00
Multi-purpose Z80 card:			
FM tuner (1 × 27C256)	6101	20.00	40.00
Multi-purpose Z80 card:			
GAL set (2 × GAL 16V8)	6111	11.15	22.30
Multi-purpose Z80 card:			
BIOS (1 × EPROM 27128)	6121	15.30	30.60
1.2 GHz multifunction frequency meter (1 × 27C256)	6141	11.45	22.90
Digital audio/visual system (1 × 27C256)	6171	10.30	20.60
TV test pattern generator (1 × 27256)	6151	13.00	26.00
DiAV system. Package: 1 × 27512; 2 × GAL; 1 × floppy disk (MSDOS)	6181	30.50	61.00
PAL test pattern generator (1 × GAL 20V8-25)	6211	9.40	18.60
Watt-hour meter (1 × 27256)	6241	10.00	20.00
8751 programmer (1 × 8751)	7061	46.40	92.80

DISKETTES

Multifunction measurement card (MMC) for PCs	1461	7.65	15.30
8751 programmer	1471	7.65	15.30
PT100 thermometer	1481	7.65	15.30
Logic analyser: IBM software on disk, incl. GAL	1491	19.40	38.80
Logic analyser: Atari software on disk (3.5"), incl. GAL	1501	19.40	38.80
Plotter driver (D. Sijtsma)	1541	11.15	22.30
I/O interface for Atari	1571	7.65	15.30
Tek/Intel file converter	1581	7.65	15.30
B/W video digitizer	1591	11.15	22.30
Timecode interface	1611	7.65	15.30
RTC for Atari ST	1621	7.65	15.30
24-bit colour extension for video digitizer	1631	11.15	22.30
PC controlled weather station - 3 (supersedes disks 1551 and 1561)	1641	7.65	15.30
8051/8032 Assembler course (IBM version)	1661	7.65	15.30
8051/8032 Assembler			

PROJECT	No.	Price (£)	Price (US\$)
course (Atari version) (3.5")	1681	7.65	15.30
AD232 converter	1691	7.65	15.30
GAL programmer (3 disks; upgrade: June 1993)	1701	11.15	22.30
Multi-purpose Z80 card	1711	7.65	15.30
EPROM emulator II	129	6.75	13.50
Pascal library for MMC	1751	9.70	19.40
Speech/sound memory	1771	7.65	15.30
IR receiver and DTMF decoder for 80C32 SBC	1791	9.00	18.00
I2C opto/relay card	1821	7.65	15.30
Video digitizer for PCs	1831	14.50	29.00
Philips preamplifier	1861	8.50	17.00
GAL programmer (excl. Opal Jr. disks)	1881	10.75	21.50

PRINTED CIRCUIT BOARDS

Printed circuit boards whose number is followed by a + sign are only available in combination with the associated software item, and can **not** be supplied separately. The indicated price includes the software.

JANUARY 1993

PAL test pattern generator (incl. GAL 6211)	920129+	15.30	30.60
Dual video amplifier/splitter	920153	Not available	
Cross-over point detector	920165	Not available	
Multi-core cable tester			
- matrix board	926079	17.05	34.10
- slave unit	926084	6.20	12.40
- master unit	926085	8.25	16.50

FEBRUARY 1993

U2400B NiCd battery charger	920098	8.75	17.50
Digital audio enhancer	920169	14.25	28.50
I2C opto/relay card	930004	11.00	22.00
Watt-hour meter (PCBs -1 and -2, and EPROM 6241)	920148+	37.25	74.50

MARCH 1993

Linear sound pressure meter	930006	7.00	14.00
Electrically isolated RS232 interface	920138	10.25	20.50
80C32 DTMF decoder	920070	Not available	

APRIL 1993

Audio power meter	930018	10.25	20.50
27MHz AM/FM transmitter	920121	Not available	
Video digitizer for PCs (incl. disk 1831)	930007+	37.00	74.00
Infrared receiver for 80C32 single-board computer (incl. disk 1791)	920149+	14.50	29.00
4MB printer buffer card	920009	27.50	55.00

MAY 1993

FM stereo signal generator	920155	23.00	46.00
VHF/UHF receiver	926001	19.00	38.00
Philips preamplifier	930003	7.50	15.00
Workbench PSU	930033	21.50	43.00

JUNE 1993

Spectrum VU meter	920151	13.00	26.00
GAL programmer upgrade	930060	4.50	9.00
Digital frequency readout for VHF/UHF receiver	926001-2	11.50	23.00
Inexpensive phase meter			
- main board	930046	9.00	18.00
- meter board	920018	4.75	9.50

SERIOUS SOUND SERIOUS SAVING

HIGH QUALITY PROFESSIONAL 100W POWER AMPLIFIER KIT – **SAVE £30**

★ Ideal for Instrument Amplification ★ Stage Foldback ★ Small Venue P.A. ★ Studio Monitor Amplifier



1992/3 Catalogue Price **£159.95**

NOW ONLY [H]

£129.95

Order Code **LT11M**

This superb amplifier kit brings together five of the best and most popular 'Audio Building Blocks', to produce an amplifier of unrivalled sound quality at the price. The Power Output Stage is an excellent 150W MOSFET design which is currently Maplin's Best Selling Audio Kit. It is complemented by the excellent performance of the SSM2016 Differential Preamplifier which has also featured in Maplin's 'Top 20' kits. The superb audio stages are supported by a High Quality Power Supply Unit, sophisticated Monitoring Circuitry and a Thermal Protection System. Housed in a rugged 19in. rack mounting case, this outstanding amplifier is designed for longevity, purity of sound reproduction and ease of integration with other professional equipment.

The kit contains everything you need to build this superb amplifier and is supplied complete with comprehensive constructional information.

Features:

- ★ Standard 19in. 2U Rack Mounting Case
- ★ 100W RMS Power Output
- ★ Balanced Line Input
- ★ Loudspeaker Protection
- ★ Switch-on Mute
- ★ Thermal Protection

Typical Specification:

Rated Load Impedance: 4 to 8Ω

Maximum Power Output:

4Ω 105W RMS

8Ω 90W RMS

THD @ 75W (1kHz): 0.02%

Frequency Response: 10Hz to 40kHz, -1dB

For a friendly welcome and the best of service, visit your local Maplin store: **BIRMINGHAM**; Sutton New Road, Erdington. **BRIGHTON**; 65 London Road. **BRISTOL**; 302 Gloucester Road. **CARDIFF**; 29-31 City Road. **CHATHAM**; 2 Luton Road. **COVENTRY**; 12 Bishop Street. **EDINBURGH**; 126 Dalry Road. **GLASGOW**; 264-266 Great Western Road. **ILFORD**; 302-304 Green Lane. **LEEDS**; Carpet World Building, 3 Regent Street. **LEICESTER**; Office World Building, Burton Street. **LONDON**; 146-148 Burnt Oak Broadway, Edgware. 107-113 Stanstead Road, Forest Hill. 120-122 King Street, Hammersmith. **MANCHESTER**; 8 Oxford Road. **NEWCASTLE-UPON-TYNE**; Unit 4, Allison Court, The Metro Centre, Gateshead. **NOTTINGHAM**; 86-88 Lower Parliament Street. **PORTSMOUTH**; 98-100 Kingston Road. **READING**; 129-131 Oxford Road. **SHEFFIELD**; 413 Langsett Road, Hillsborough. **SOUTHAMPTON**; 46-48 Bevois Valley Road. **SOUTHEND-ON-SEA**; 282-284 London Road, Westcliff. Plus a NEW STORE opening soon in **MIDDLESBROUGH**. Phone 0702 552911 for further details. Subject to availability. Price subject to change. Price inclusive of VAT. [H] indicates a carriage charge of £5.50.

Maplin

ELECTRONICS

CREDIT CARD HOTLINE

0702 554161

Mail Order to: P.O. Box 3, Rayleigh, Essex SS6 8LR